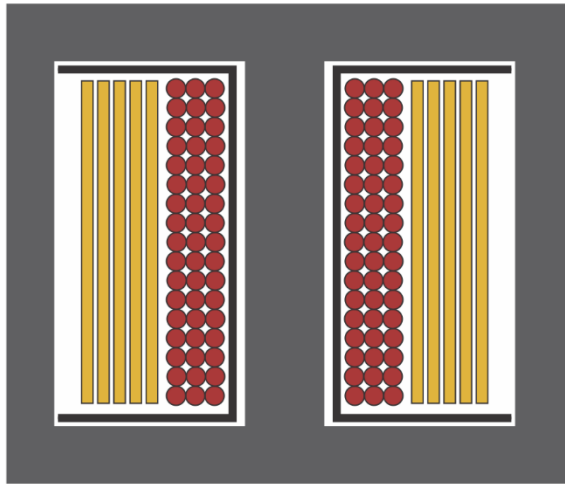


Circuit Modeling of Winding Loss for Inductors and Transformers

Dr. Ray Ridley

ridleyengineering.com

Why do we Need Proximity Loss Analysis?



Primary Winding 0.097 Ohm

51 Turns

3 Layers of 17 Turns 20 awg wire

0.9 mm diameter


$$\text{Loss} = 1.985^2 \times 0.097 = \boxed{0.38 \text{ W}}$$

Secondary Winding 1.46 mOhm

5 Turns

5 Layers of 10 mil foil (0.26 mm)
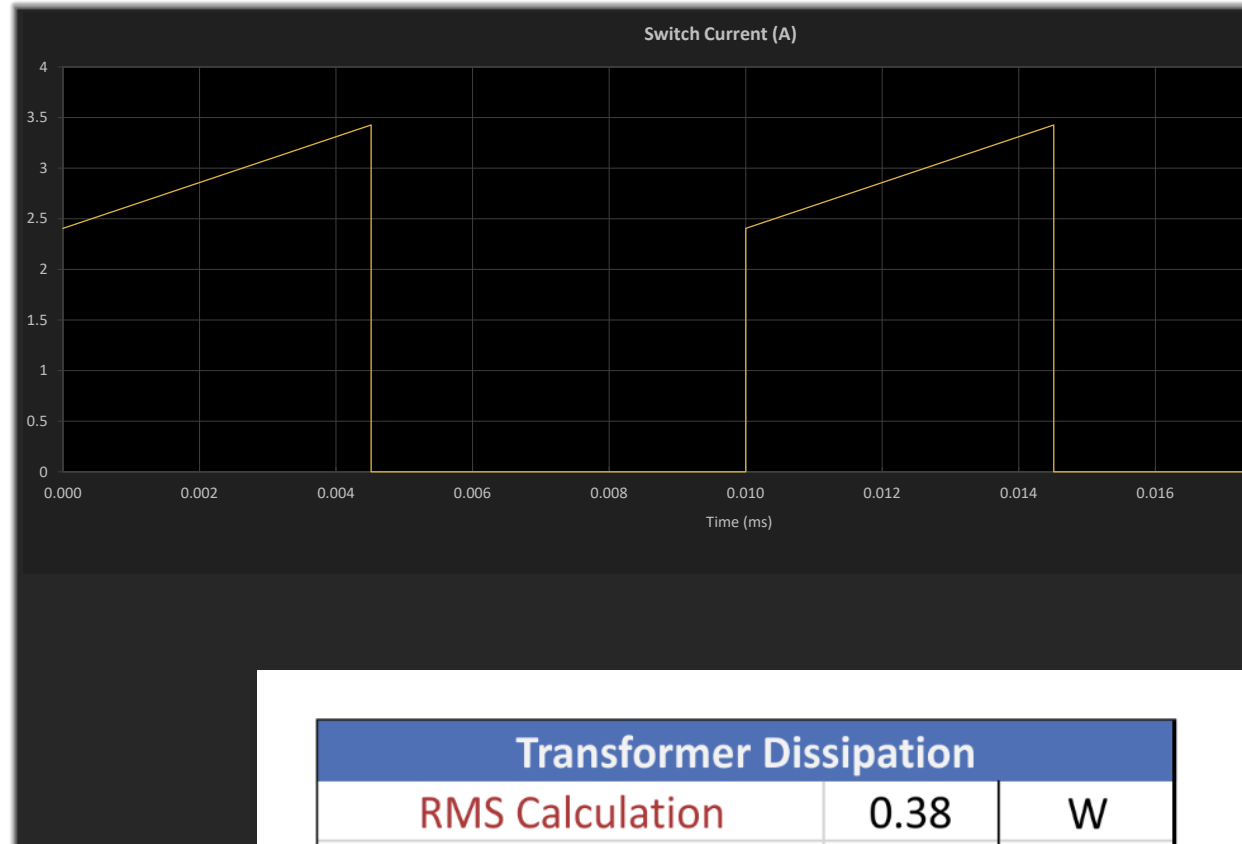
$$\text{Loss} = 21.73^2 \times 0.00146 = \boxed{0.69 \text{ W}}$$




Transformer Dissipation		
RMS Calculation	0.38	W
Proximity Fundamental	5.54	W
LTspice Simulation	8.46	W
RMS Calculation	0.69	W
Proximity Fundamental	6.02	W
LTspice Simulation	6.27	W

Proximity Loss - the Hard Way

Step 1


Define the Winding Structure

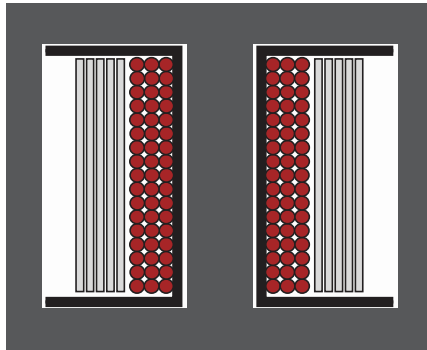

Find n , R_{dc} and L


Step 2

Simulate Waveforms

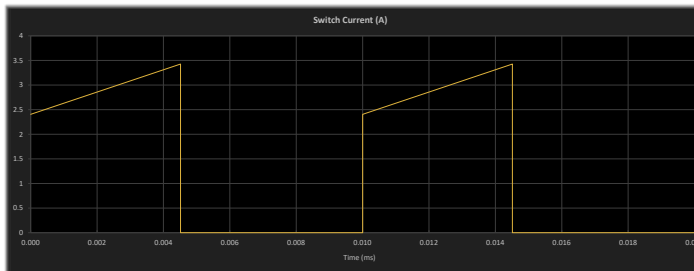


Step 4

Dowell's Eqs for AC Resistance

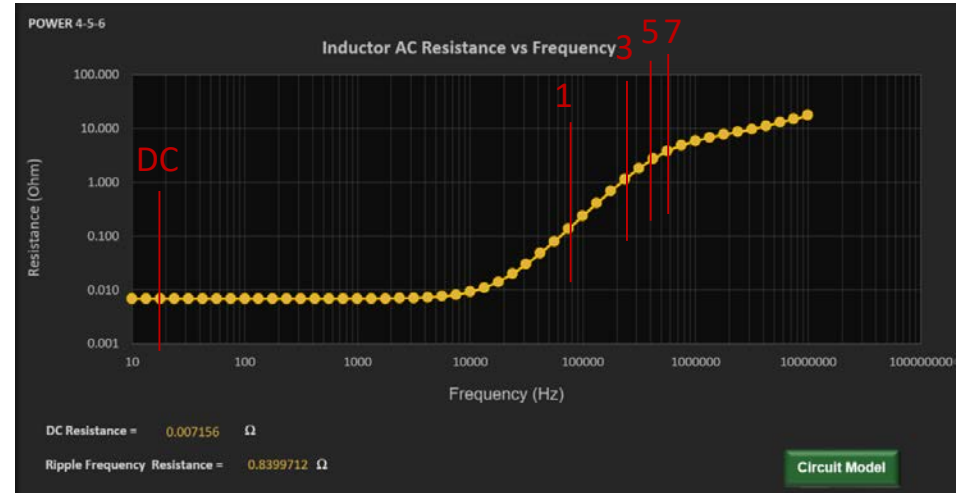

Step 3

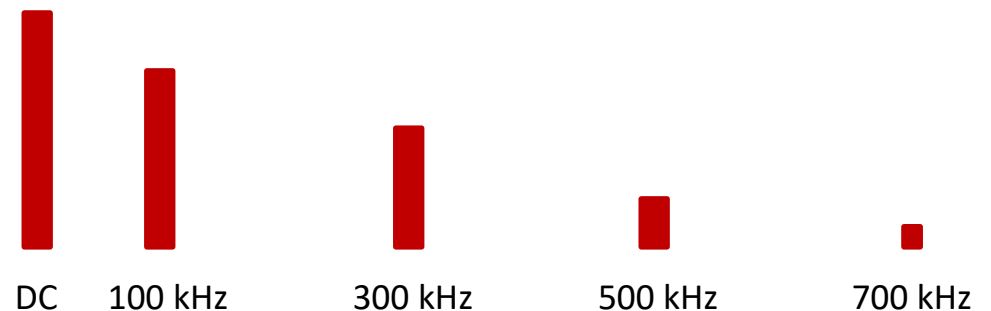
Extract Harmonic Content – solve $I^2 R_{ac}$ for each



Proximity Loss - the Modern Way

Step 1


Define the Winding Structure

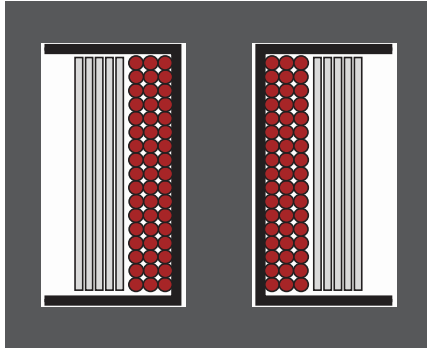

Find n , R_{dc} and L

Step 3


Circuit Model to Match Predictions

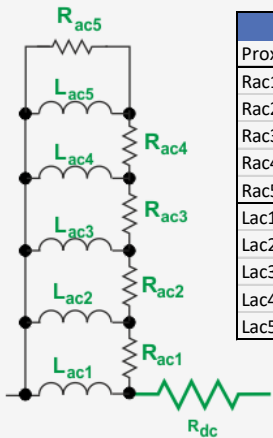

Transformer Primary Winding Proximity Model		
Proximity model active?	1	1=yes
Rac1	1.32	mΩ
Rac2	234.43	mΩ
Rac3	2938.35	mΩ
Rac4	6590.55	mΩ
Rac5	21402.18	mΩ
Lac1	41.39685	uH
Lac2	41.0829	uH
Lac3	29.89081	uH
Lac4	8.84732	uH
Lac5	2.55406	uH


Step 2

Sweep Dowell's Eqs for AC Resistance

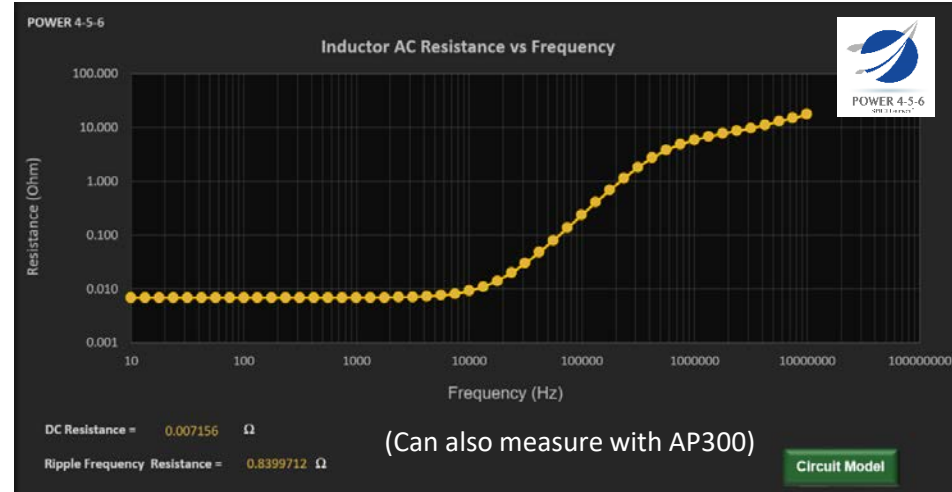

Step 4

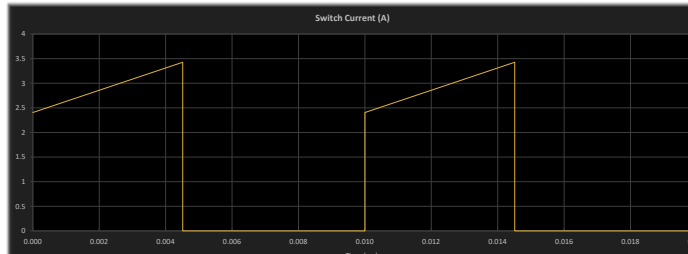
Simulate Waveforms - all Proximity Loss is Time Domain



Magnetics Winding Loss


Design Example

Proximity Loss Example

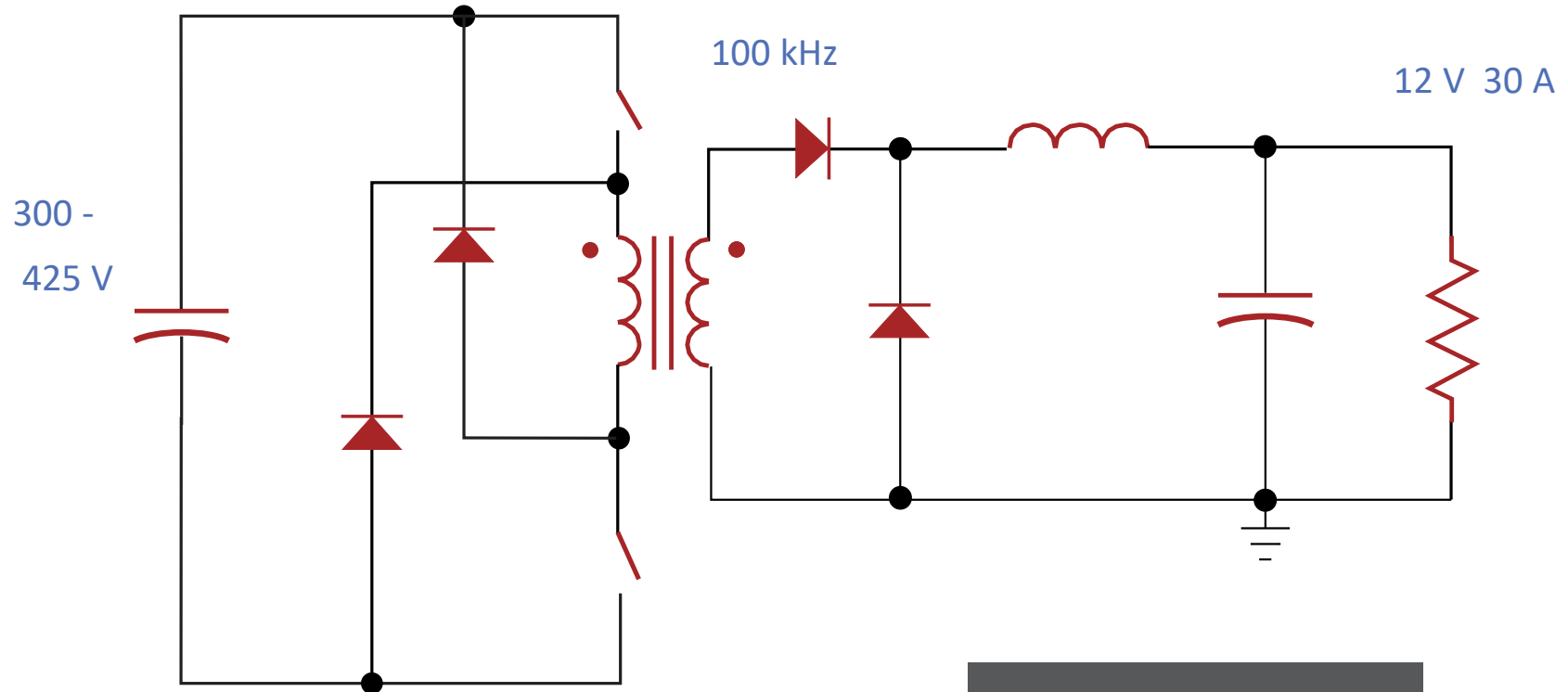


Primary 51 turns 20 awg 3 layers

Secondary 5 turns 10 mil foil

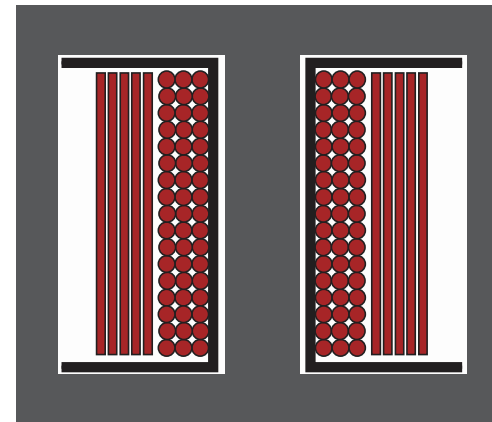

Primary Proximity Loss

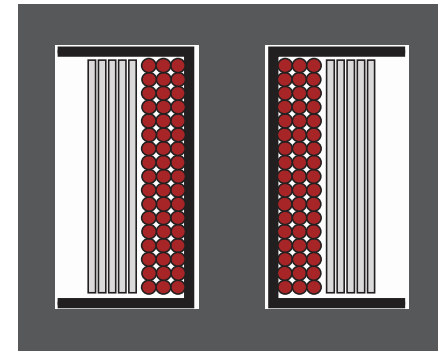

$$P_d = b_w \sum_{i=1}^n l_i \frac{1}{h_i \eta_i \sigma} H_i^2 \left[(1 + \alpha_i^2) G_{1_i} - 4\alpha_i G_{2_i} \right]$$

The H field is calculated from

$$H_i = \frac{N_i I_i}{b_w} \quad b_w = \text{winding width}$$

Complex functions are needed to calculate the losses :

$$G_{1_i} = \Delta_i \frac{\sinh 2\Delta_i + \sin 2\Delta_i}{\cosh 2\Delta_i - \cos 2\Delta_i}$$


$$G_{2_i} = \Delta_i \frac{\sinh \Delta_i \cos \Delta_i + \cosh \Delta_i \sin \Delta_i}{\cosh 2\Delta_i - \cos 2\Delta_i}$$

The ratio of the winding layer height to skin depth is

$$\Delta_i = \frac{h_{cu_i}}{\delta} \quad \text{skin depth } \delta = \sqrt{\frac{2}{\omega \mu_o \sigma \eta}}$$

$$\sigma = \text{conductivity} \quad \mu_o = 4\pi \times 10^{-7} \quad \eta = \text{porosity}$$

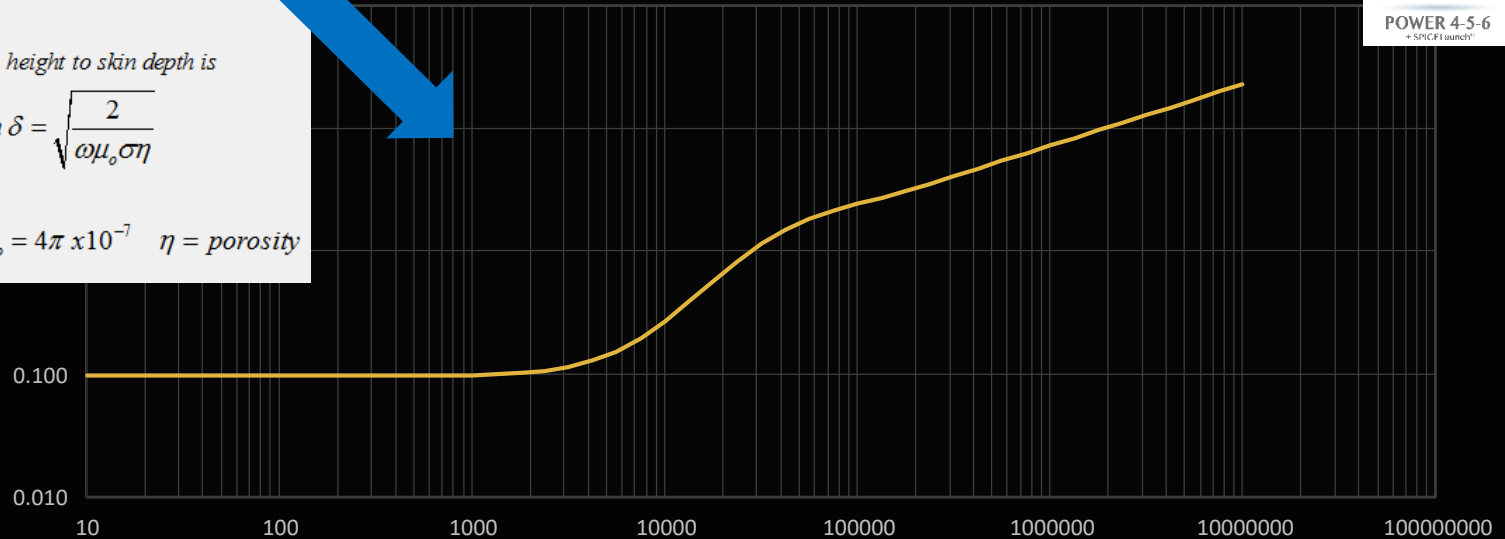Transformer Primary AC Resistance vs Frequency



DC Resistance = 0.09657 Ohm


Ripple Frequency Resistance = 2.4239 Ohm

Primary Proximity Loss




Resistance (Ohm)

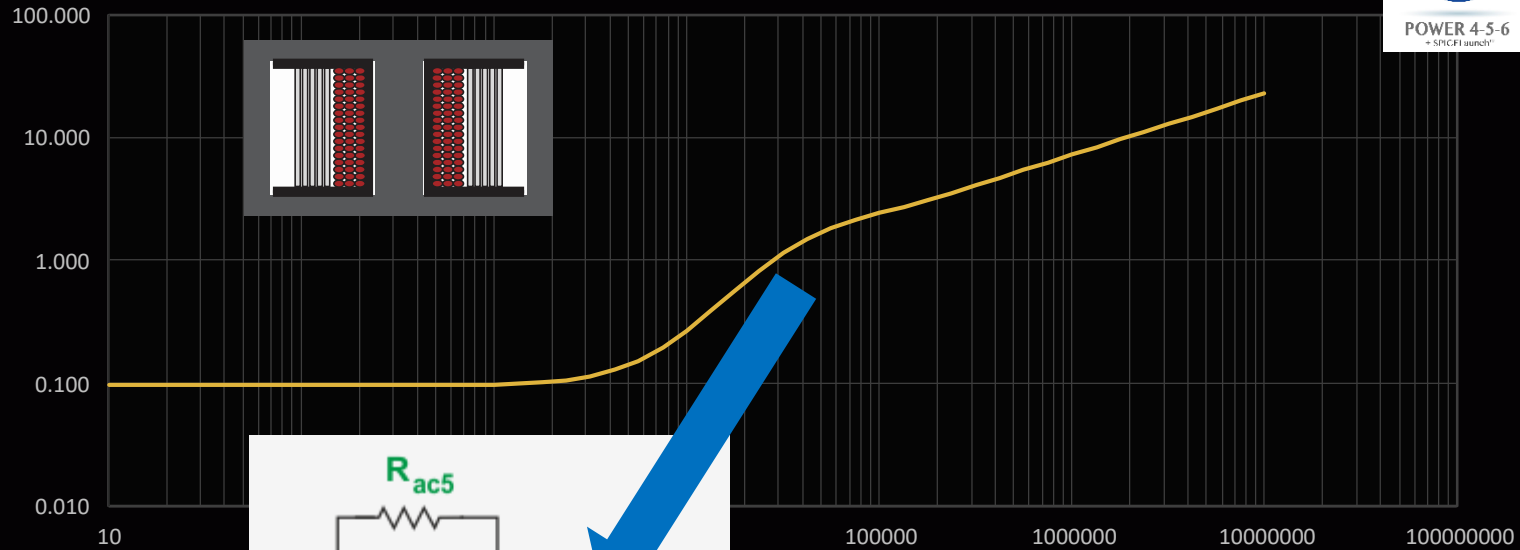Transformer Primary AC Resistance vs Frequency






DC Resistance =
Ripple Frequency



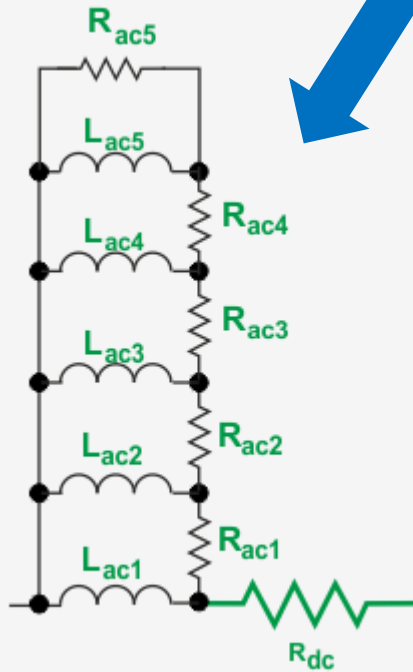


Transformer Primary Winding Proximity Model		
Proximity model active?	1	1=yes
Rac1	1.32	mΩ
Rac2	234.43	mΩ
Rac3	2938.35	mΩ
Rac4	6590.55	mΩ
Rac5	21402.18	mΩ
Lac1	41.39685	uH
Lac2	41.0829	uH
Lac3	29.89081	uH
Lac4	8.84732	uH
Lac5	2.55406	uH

Primary Proximity Loss

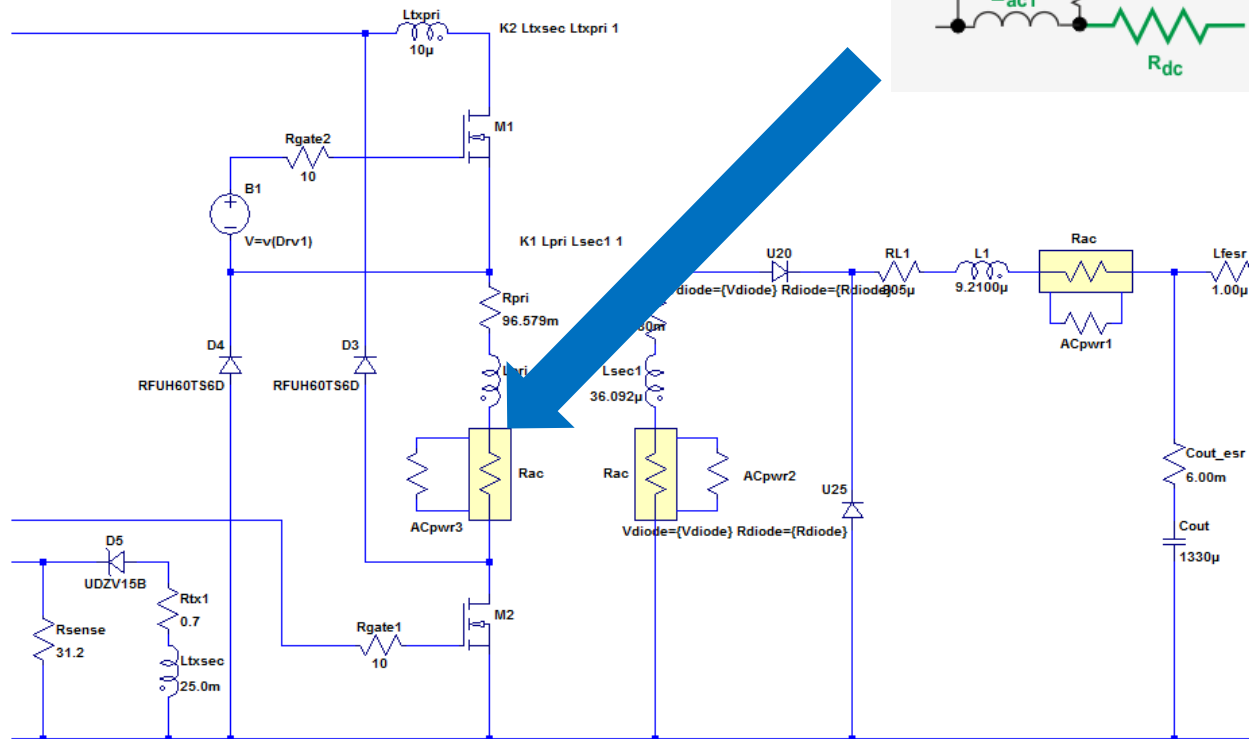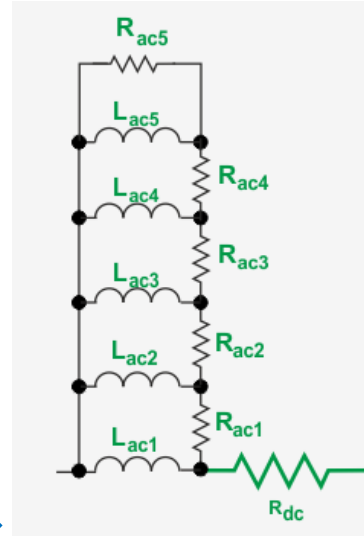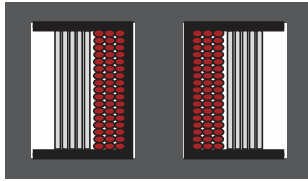

Primary Proximity Loss

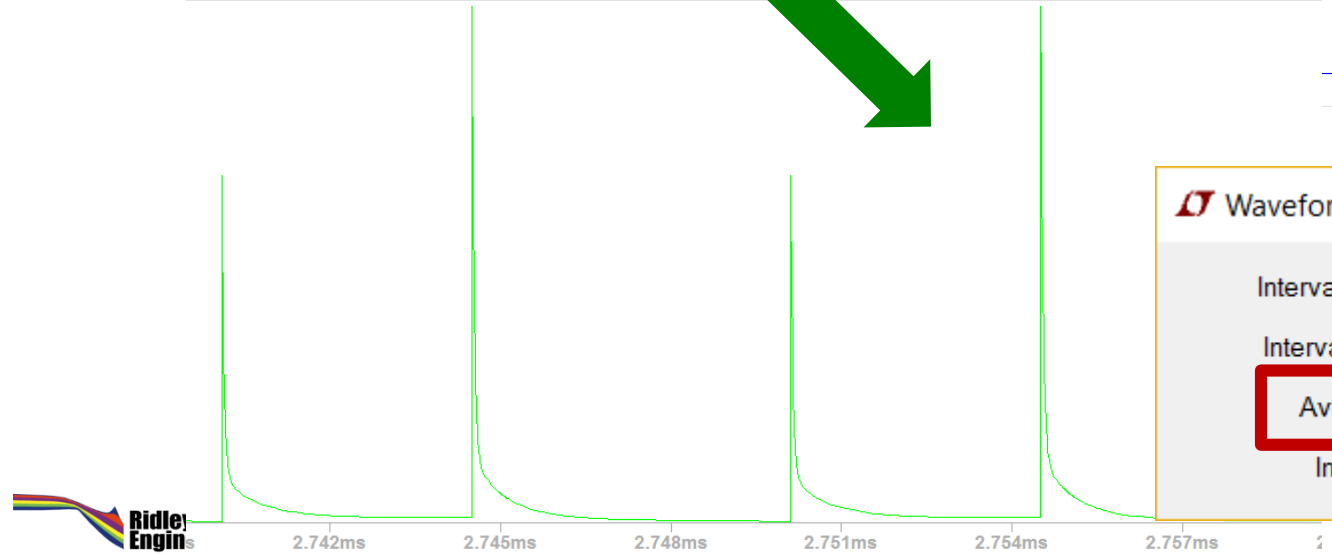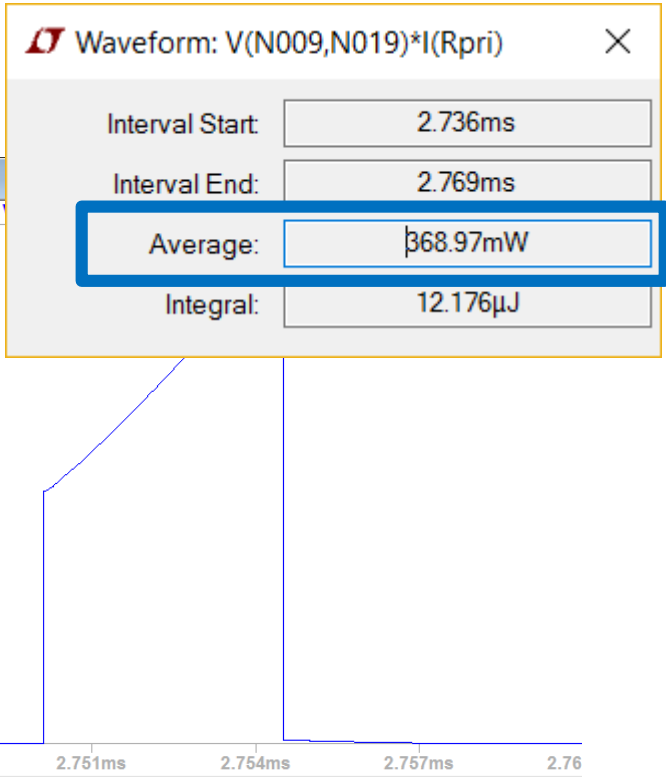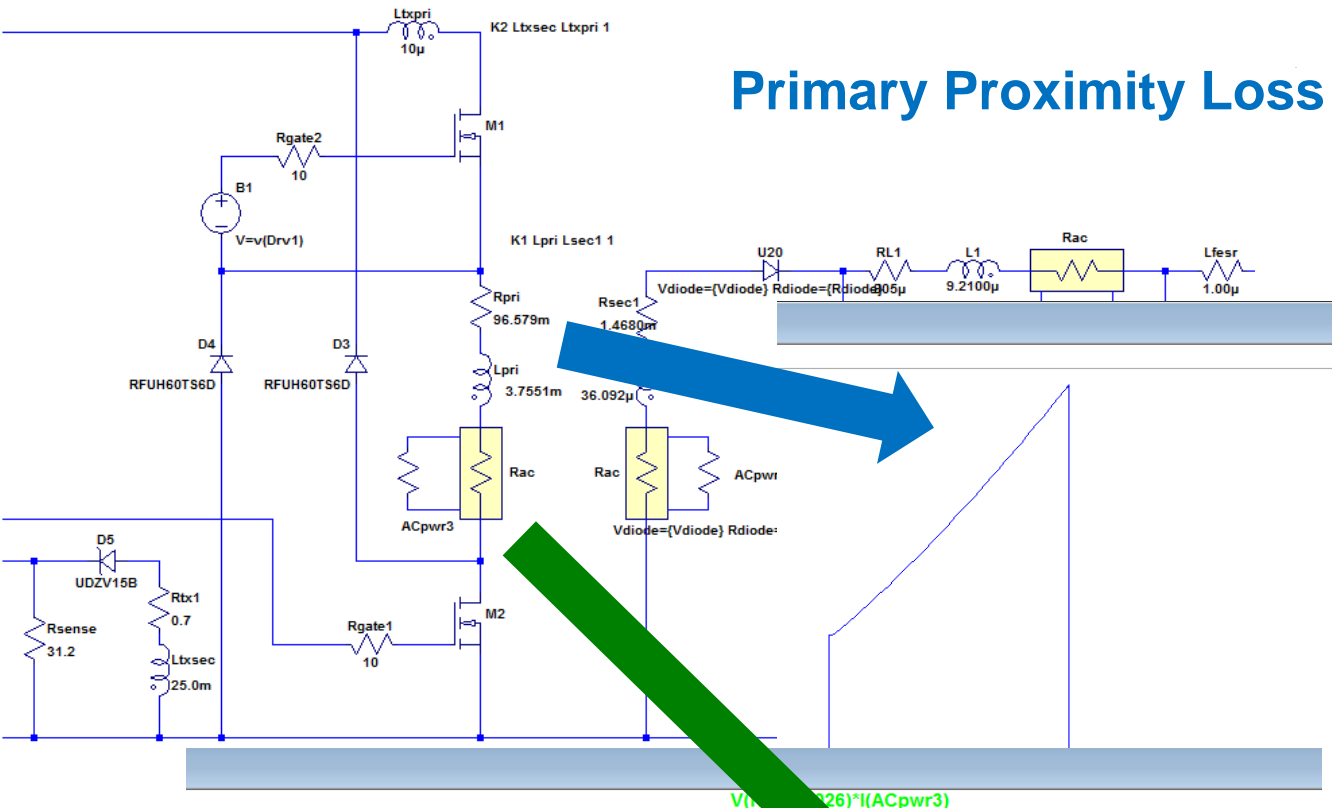

Secondary Proximity Loss (5 mil Foil)

$$P_d = b_w \sum_{i=1}^n l_i \frac{1}{h_i \eta_i \sigma} H_i^2 [(1 + \alpha_i^2) G_1 - 4 \alpha_i G_2]$$

The H field is calculated from

$$H_i = \frac{N_i I_i}{b_w} \quad b_w = \text{winding width}$$

Complex functions are needed to calculate the losses :


$$G_1 = \Delta_i \frac{\sinh 2\Delta_i + \sin 2\Delta_i}{\cosh 2\Delta_i - \cos 2\Delta_i}$$

$$G_2 = \Delta_i \frac{\sinh \Delta_i \cos \Delta_i + \cosh \Delta_i \sin \Delta_i}{\cosh 2\Delta_i - \cos 2\Delta_i}$$


The ratio of the winding layer height to skin depth is

$$\Delta_i = \frac{h_{cu}}{\delta} \quad \text{skin depth } \delta = \sqrt{\frac{2}{\omega \mu_o \sigma \eta}}$$

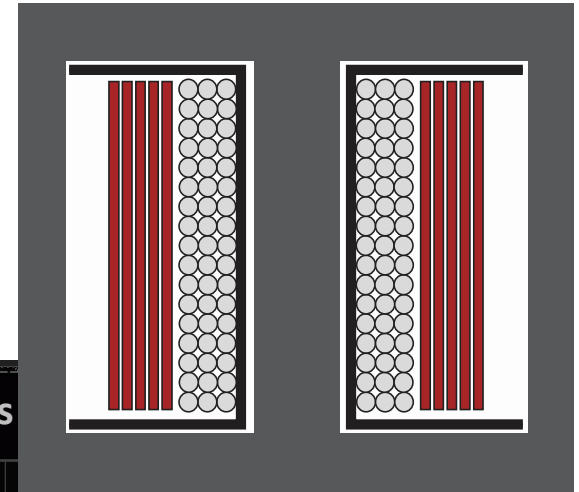$\sigma = \text{conductivity}$ $\mu_o = 4\pi \times 10^{-7}$ $\eta = \text{porosity}$




Transformer Secondary AC Resistance vs

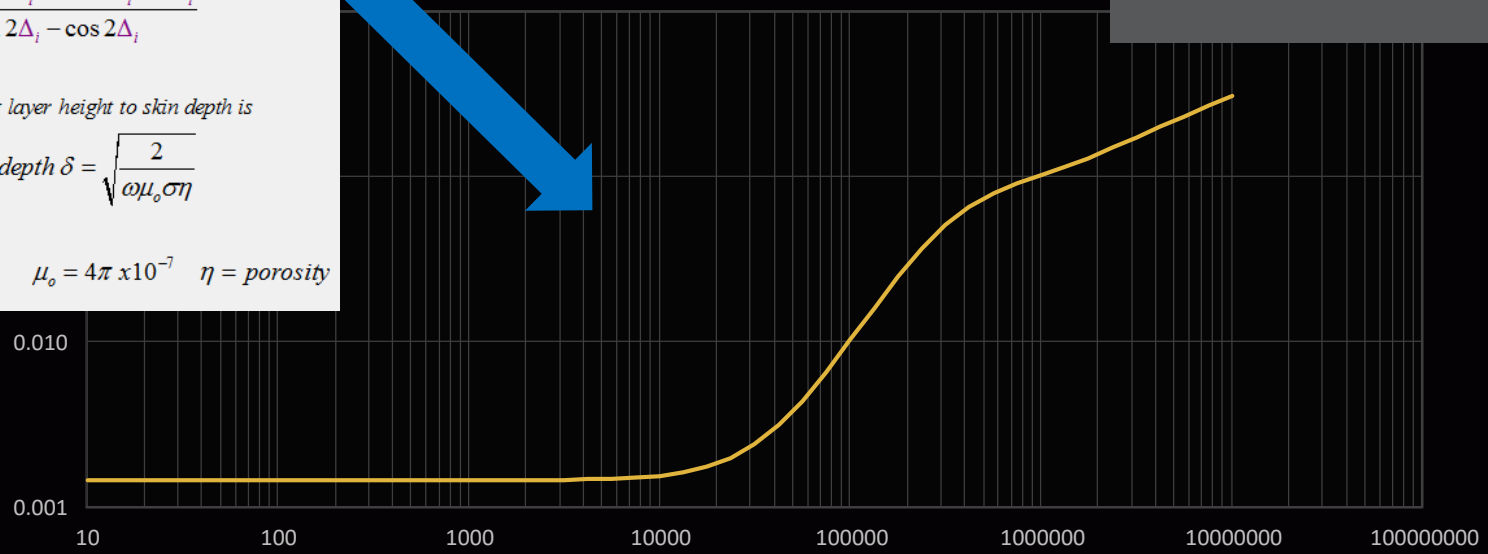

DC Resistance = 0.0014569 Ohm

Ripple Frequency Resistance = 0.0102 Ohm

Secondary Proximity Loss Simulation

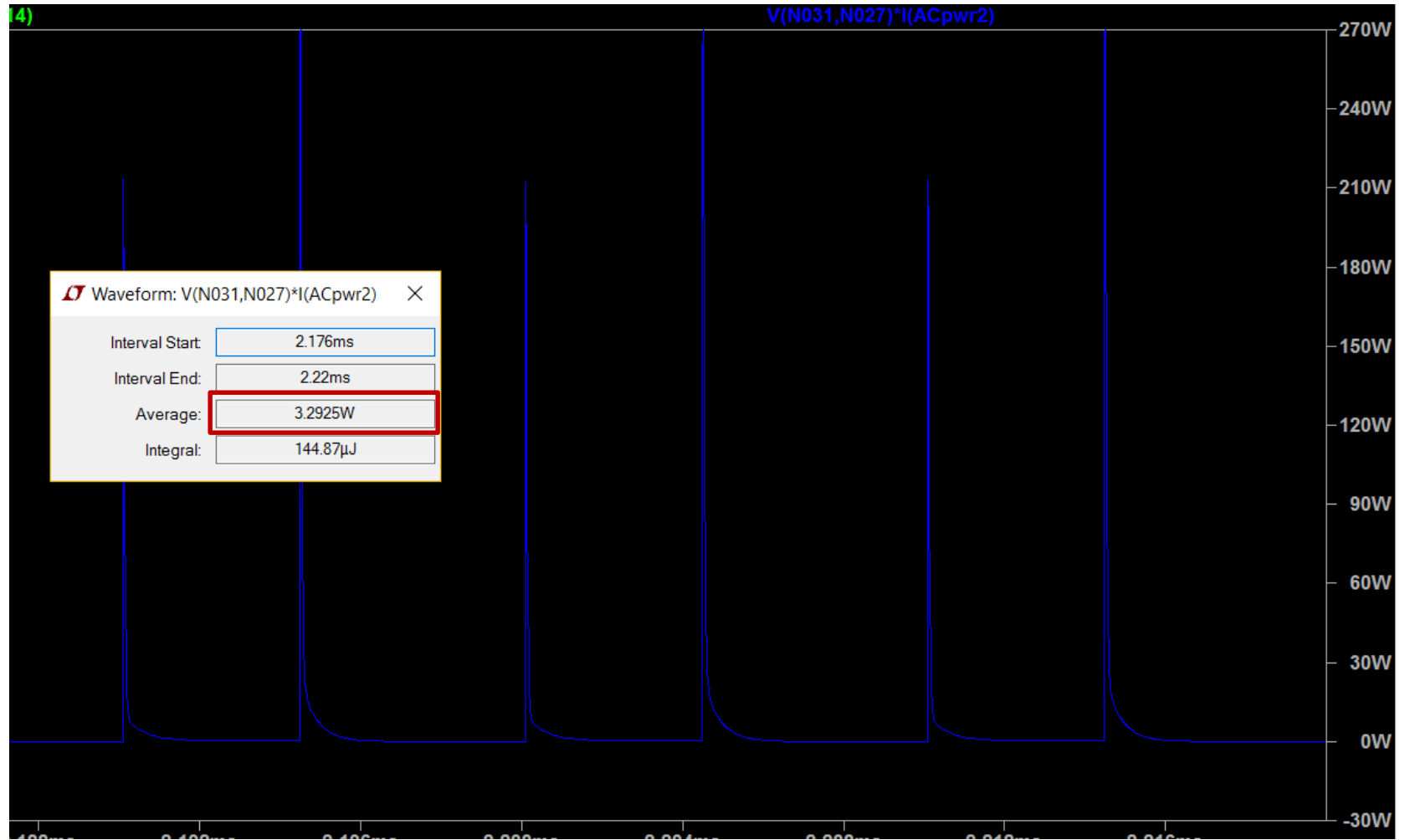

Ridley Engineering Contacts

Power Supply Design Center Discussion Group

Advanced discussion group for power electronics engineers.

facebook.com/groups/ridleyengineering/

Power Supply Design Center Papers and Videos

Educational material with a very practical approach
ridleyengineering.com/design-center-ridley-engineering.html

Power 4-5-6 with SpiceLaunch Advanced Software

Automated power supply design software
Proximity models and Ltspice generation
ridleyengineering.com/software-ridley/power-4-5-6/power-4-5-6-ridley.html

Power Supply Workshops Training for working engineers

Four days of hands-on magnetics and control design.
ridleyengineering.com/education/analog-lab-workshop/intro.html