



# If Your Standby Power Is Too High, Your Power Converter Will Not Sell

David Chen, Energy Management Industry Session, APEC 2020

# What is Standby Power?

- **Standby power is the power used by electronics and appliances when not performing their main function**
  - ▶ Can be a significant portion of the overall energy use of a device
- **Energy efficiency standards set standby power limits**
  - ▶ All new federal efficiency standards are required to include standby power
  - ▶ Horizontal standby regulation in EU is under revision and targeting stricter limits
- **As a power supply designer, what can one do?**
  - ▶ Aim is to optimize efficiency to maximize available power within the prescribed limits
  - ▶ Example: 15 W dual-output power supply design to meet emerging EU standby regulation

# European Commission Has Different Levels of Requirements



## ■ Ecodesign Directive

- ▶ Regulatory framework in the EU to reduce the environmental impact of products throughout their entire lifecycles

## ■ Energy Labelling

- ▶ Policy instrument used to influence consumer behavior toward conservation



## ■ Code of Conduct

- ▶ Sets out the basic principles to be followed by all parties involved in power supplies operating in Europe with respect to energy efficient equipment
- ▶ Voluntary

# Ecodesign and Labelling Under Revision

Product	ENER Lot	Status in the EuP process
PCs and servers	3	Regulation in force 2013. Revision ongoing.
Televisions and electronic displays	5	Revision ongoing.
Standby and off-mode losses	6	Revision ongoing. Consultation Forum 20 Dec 2017
Battery chargers and external power supplies	7	Regulation in force 2009. Revision ongoing.
Linear, CFL, and HID lamps and ballasts	8-9	Regulation in force 2009. Revision ongoing.
Ventilation fans	11	Revision ongoing.
Electric pumps	11	Revision ongoing. Consultation Forum 8 Dec 2017
Domestic refrigerators and freezers	13	Revision ongoing. Consultation Forum 6 Dec 2017
Domestic washing machines	14	Revision ongoing. Consultation Forum 18 Dec 2017
Domestic dishwashers	14	Revision ongoing. Consultation Forum 19 Dec 2017
Household tumble driers	16	Regulation in force 2012. Revision ongoing.
Vacuum cleaners	17	Regulation in force 2013. Revision ongoing.
Directional lighting	19	Revision ongoing. Consultation Forum 7 Dec 2017
Domestic lighting (general lighting equipment)	19	Revision ongoing. Consultation Forum 7 Dec 2017
Networked standby losses	26	Revision ongoing. Consultation Forum 20 Dec 2017

<https://www.ecee.org/ecodesign/>

# Ecodesign Regulations for Standby/Off-Mode

## ■ Impact assessment finalized

- ▶ Review study on standby published in April 2017; consultation forum held in December 2017
- ▶ Status of adoption pending

## ■ Regulation (EC) No 1275/2008 is under revision

- ▶ Horizontal requirement → applies across all energy-using product categories

## ■ Proposed changes

- ▶ Standby/off-mode requirement reduced to 0.3 W from 0.5 W
- ▶ Network standby requirement reduced to 2 W from 3 W
  - WiFi load is always on (~1 W) plus other functions (screen, camera, etc.)
  - Example: Smart Speaker OEMs targeting <2 W input power with 1.5 W system load in standby

## ■ Timeline

- ▶ Entry into force likely delayed to end of 2020


# 15 W Dual-output Power Supply Design Example

---

# Specification

Description	Symbol	Min	Typ.	Max	Units	Comment
<b>Input</b>						
Voltage	$V_{IN}$	85	115/230	277	VAC	2 Wire – no P.E.
Frequency	$f_{LINE}$	47	50/60	63	Hz	
No-load Input Power				45	mW	230 VAC Input.
<b>Output</b>						
Output Voltage 1	$V_{OUT1}$		5		V	±5% PCB Connector Side.
Output Current 1	$I_{OUT1}$		1.2		A	
Output Ripple Voltage 1	$V_{RIPPLE1}$			150	mVpp	Measured at the PCB Connector.
Output Voltage 2	$V_{OUT2}$		12		V	±10% PCB Connector Side.
Output Current 2	$I_{OUT2}$	0.02	0.75		A	
Output Ripple Voltage 2	$V_{RIPPLE2}$			200	mVpp	Measured at the PCB Connector.
Continuous Output Power	$P_{OUT}$			15	W	
<b>Efficiency</b>						
Average 25%, 50%, 75%, and 100%	$\eta_{AVE[BRD]}$	80			%	115 and 230 VAC Input
<b>Environmental</b>						
Conducted EMI		CISPR22B / EN55022B Load floating				Resistive Load, 6 dB Margin.
Safety		IEC950 / UL1950 Class II				Designed to Meet.
Differential Line Surge		1			kV	230 VAC Input
Ambient Temperature	$T_{AMB}$	0		40	°C	Free Convection, Sea Level in Sealed Enclosure.




# Schematic

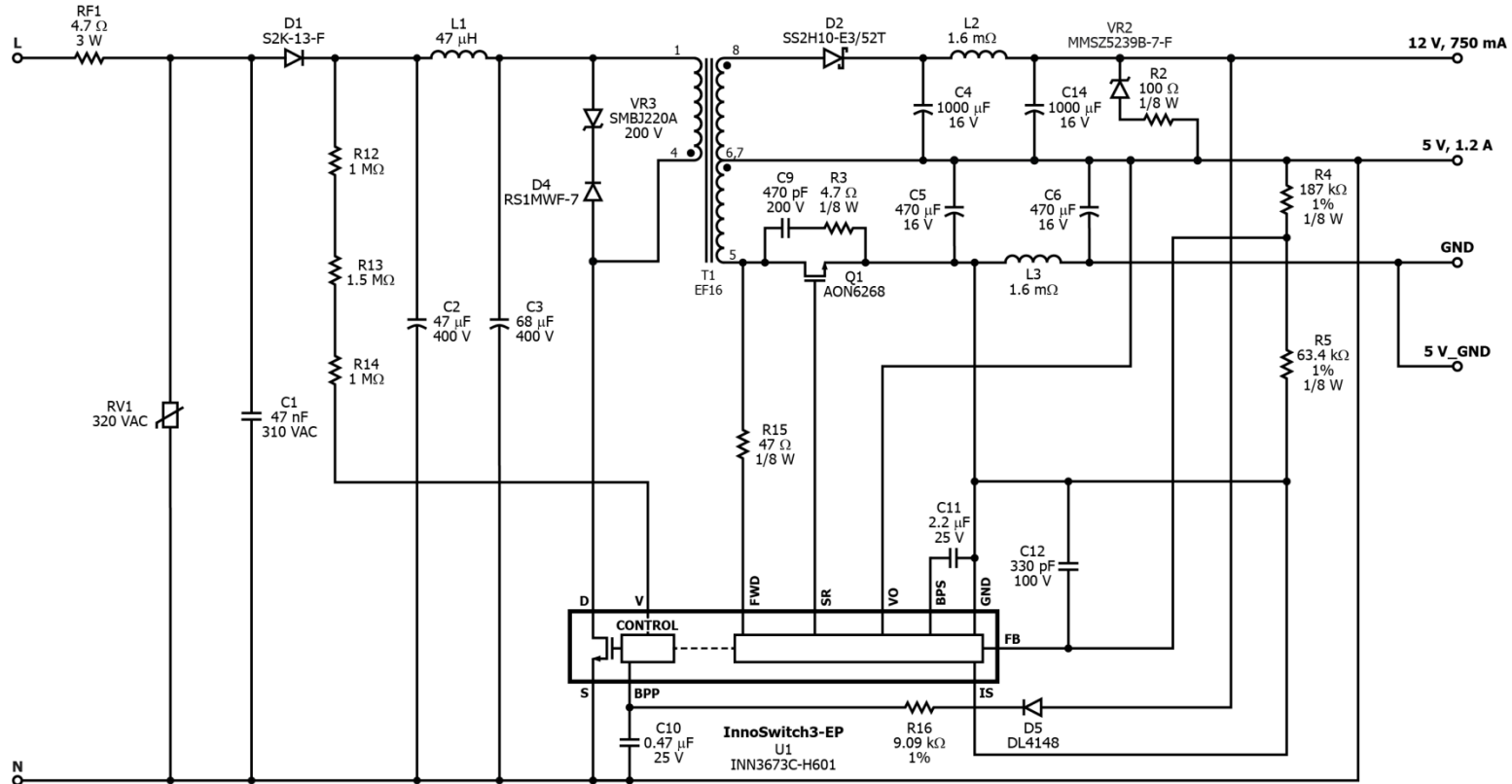

PI-8846-101618



# Open Frame Design

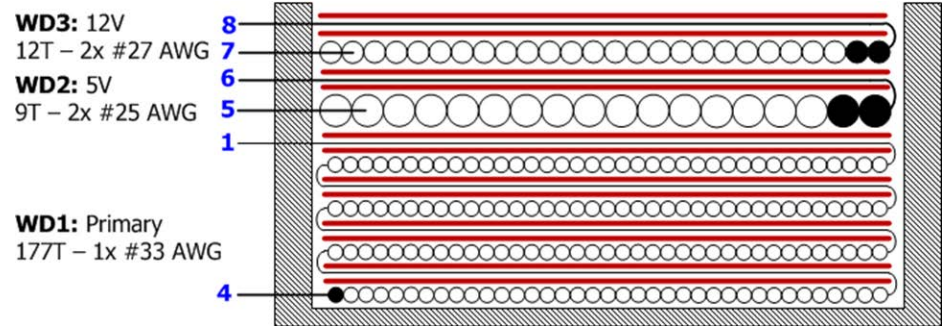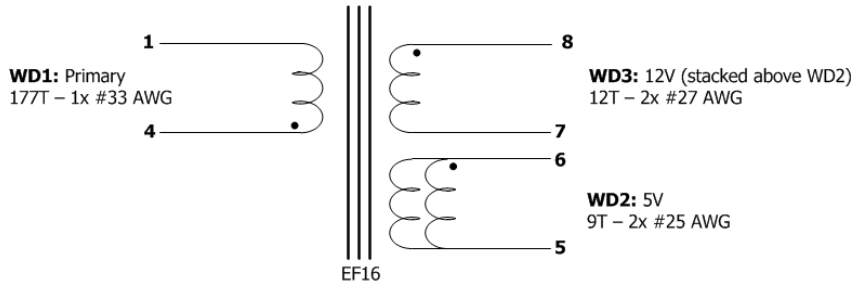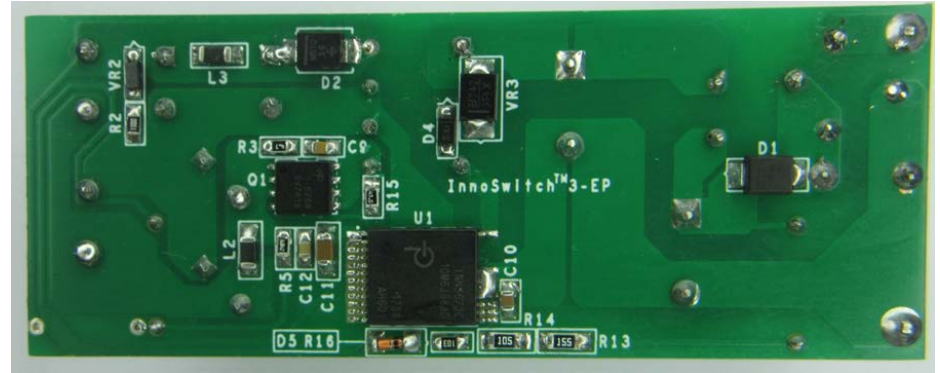

# Standby Efficiency Optimization

## 1. Primary clamp

- ▶ RCD clamp vs. Zener clamp

## 2. Transformer

- ▶ VOR, winding technique, core material

## 3. 5 V output

- ▶ Output capacitors, RC snubber

## 4. BP bias circuit

## 5. Input section

## 6. 5 V output rectifier

# Primary Clamp Design

- **To minimize losses, tune the primary clamp such that  $V_{DS(max)}$  of the primary MOSFET is 85-90% of rated breakdown voltage ( $BV_{DSS}$ )**
  - ▶ Measure at the highest AC input voltage
- **Choosing between a Zener clamp and an RCD clamp**
  - ▶ Both implementations can be used given that the above criterion is met
  - ▶ With Zener clamp, the voltage rating of the Zener (TVS) diodes have big voltage steps (e.g. 180 V, 200 V, 220 V, 250 V, 300 V, 350 V)
  - ▶ With RCD clamp, the components can be more easily tuned to meet derating target


# Transformer – VOR Optimization

- Adjusting the reflected voltage (VOR) of the transformer has a direct effect on efficiency
- Decreasing VOR increases efficiency
  - ▶ Lower VOR yields lower secondary-peak, RMS and average currents
    - Reduces conduction loss in the output diodes
  - ▶ Lower VOR increases the peak inverse voltage (PIV) – limited by diode de-rating

Section	Iteration	Reflected Voltage	Improvement per step	300 mW Standby Efficiency	5 V Output Diode PIV (rated 60 V)
Transformer	0	VOR = 90 V		75.98%	46.29
	1	VOR = 85 V	↑ 0.40%	76.38%	46.40
	2	VOR = 80 V	↑ 0.35%	76.73%	50.08
	3	VOR = 75 V	↑ 0.06%	76.79%	58.14

Design approach: start with conservative VOR and iterate design reducing VOR until diode voltage margin is minimized
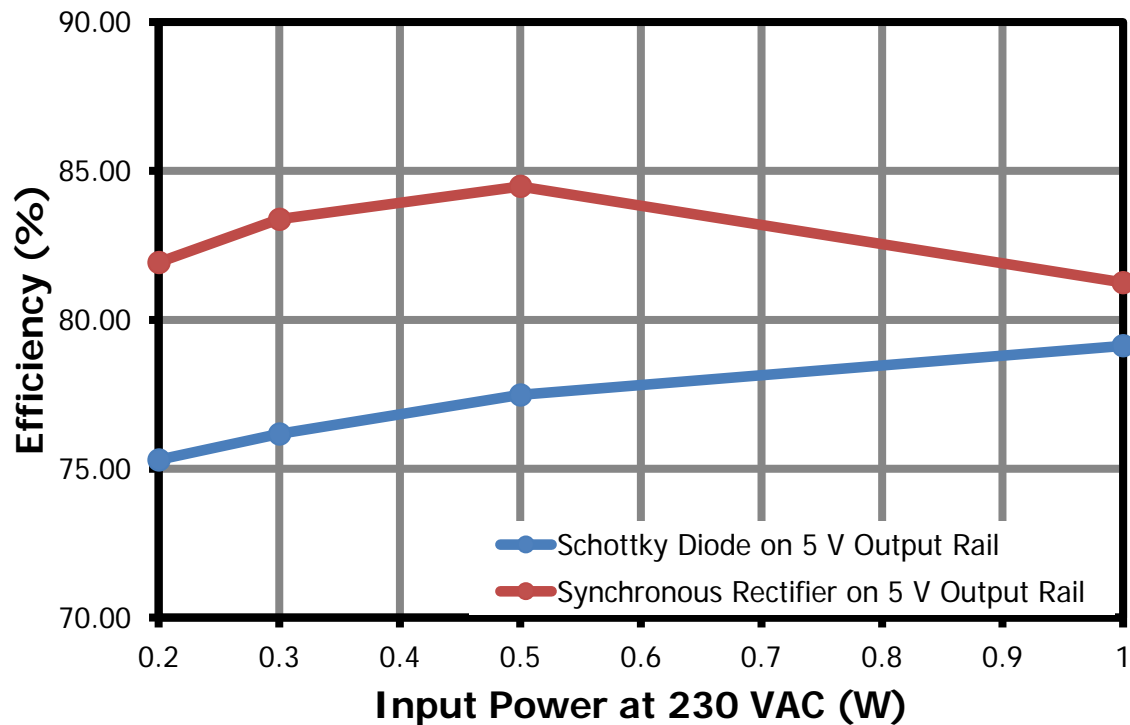
# Increasing Standby Efficiency with Synchronous Rectification on 5 V Output



# Standby Power Improvement



					<b>60.30%</b>
Primary Clamp	Primary Snubber	RCD Clamp R1=200 k $\Omega$ , C8=470 pF D4=S1ML (trr=1.8 us), R11=20 $\Omega$	Zener Clamp VR1=SMBJ200A D4=RS1MWF (trr=500 ns)	↑ 9.26%	<b>69.56%</b>
Transformer	VOR	VOR = 110 V	VOR = 100 V	↑ 4.12%	<b>73.67%</b>
	Core Material	N27 ( $A_L = 950$ nH, $\mu_e = 1410$ )	N87 ( $A_L = 1000$ nH, $\mu_e = 1490$ )	↑ 0.19%	<b>73.87%</b>
5 V Output	5 V Output Capacitor	C5 = 470 $\mu$ F 16 V E-cap Low ESR = 53 m $\Omega$	C5 = 470 $\mu$ F 16 V Polymer Cap Low ESR = 10 m $\Omega$	↑ 0.47%	<b>74.33%</b>
	5 V Output Rectifier RC Snubber	C9 = 1500 pF R13 = 10 $\Omega$	C9 = 470 pF R13 = 4.7 $\Omega$	↑ 0.30%	<b>74.63%</b>
BP Pin	BP Bias Resistor	R16 = 18 k $\Omega$ (IBP = 195 $\mu$ A)	R16 = 9.09 k $\Omega$ (IBP = 230 $\mu$ A)	↑ 0.82%	<b>75.45%</b>
Input Section	Input Choke Filter	L1 = 1000 $\mu$ H 0.28 A DCR = 2.37 $\Omega$	L1 = 47 $\mu$ H 1.6 A DCR = 0.14 $\Omega$	↑ 0.72%	<b>76.17%</b>
5 V Output	5 V Output Rectifier	D3 = STPS5L60S 60 V 5 A SMC	Q1 = AON6268 60 V 44A 6.3 m $\Omega$	↑ 7.21%	<b>83.38%</b>

# Standby Power Optimization Design Challenges

Section	Item	Challenge
Primary clamp	Zener Clamp	Verify the primary MOSFET voltage derating and EMI margin
Transformer	Lower VOR	Verify the maximum peak reverse voltage across output diode in worst case
	Core material	Higher transformer cost
5 V output capacitor	Low ESR capacitor	Lower ripple but higher cost
5 V output diode rectification	RC Snubber	Verify the output diode voltage derating and radiated EMI
BP pin	Proper supply current (230 $\mu$ A to 250 $\mu$ A)	Insufficient external supply current may cause IC self-supply
Feedback circuit	High value feedback divider resistor	Verify noise immunity and regulation/ripple
Input choke	Lower DC resistance differential choke	Verify the surge performance and ensure safe voltage margins across the input bulk cap, primary MOSFET and output rectifier; validate conducted EMI
5 V SR rectification	SR FET used for 5 V output	Higher cost
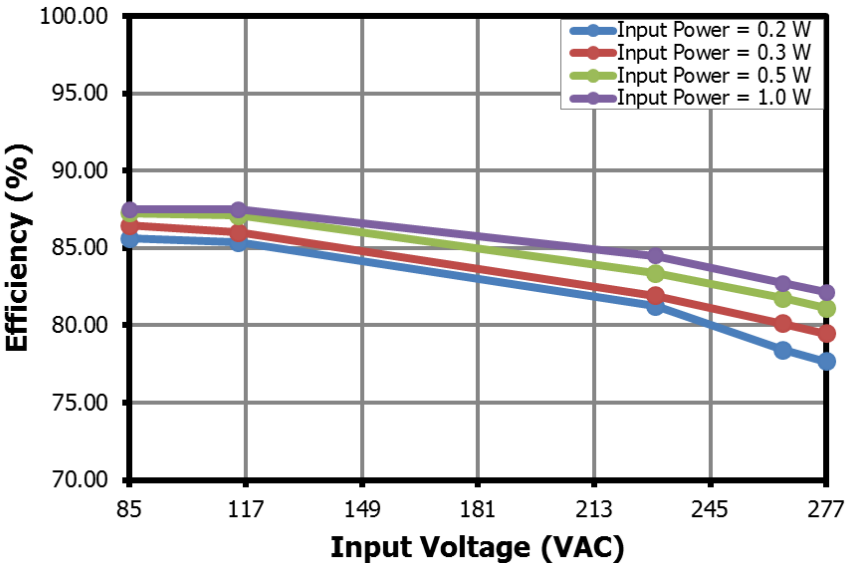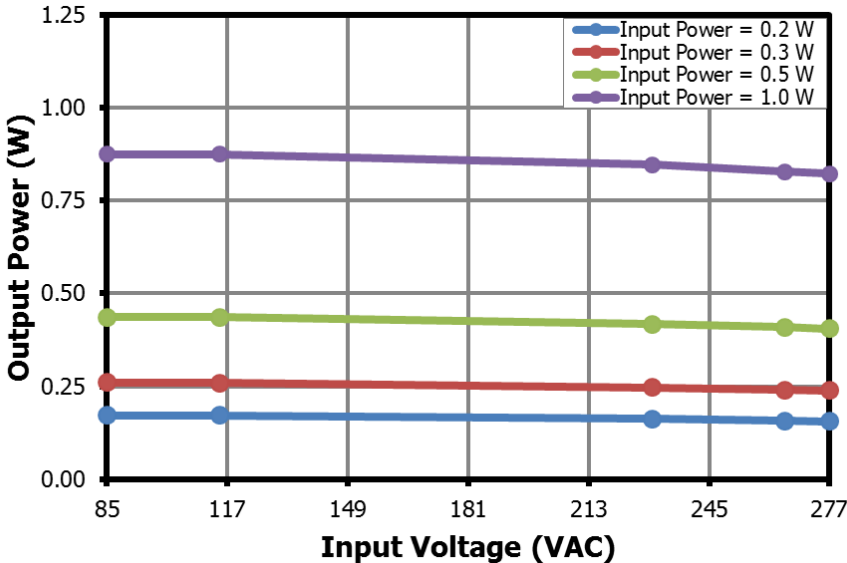
# Available Power and Efficiency in Standby Mode

- Test Condition: Soak at full load for 5 minutes and decrease load to standby mode for 5 minutes for each line step





# Summary

## ■ Standby power matters!

- ▶ Global impact of standby power consumption – ~1% of global CO2 emissions \*
- ▶ Typically 5-10% of residential electricity use in developed countries \*
- ▶ Standby power growing as more appliances incorporate standby functions, especially connectivity

## ■ Power supply design optimization enables compliance to standby regulations worldwide


\* <https://standby.lbl.gov/faq/>

# power integrations™

power.com




# Improving Standby Efficiency

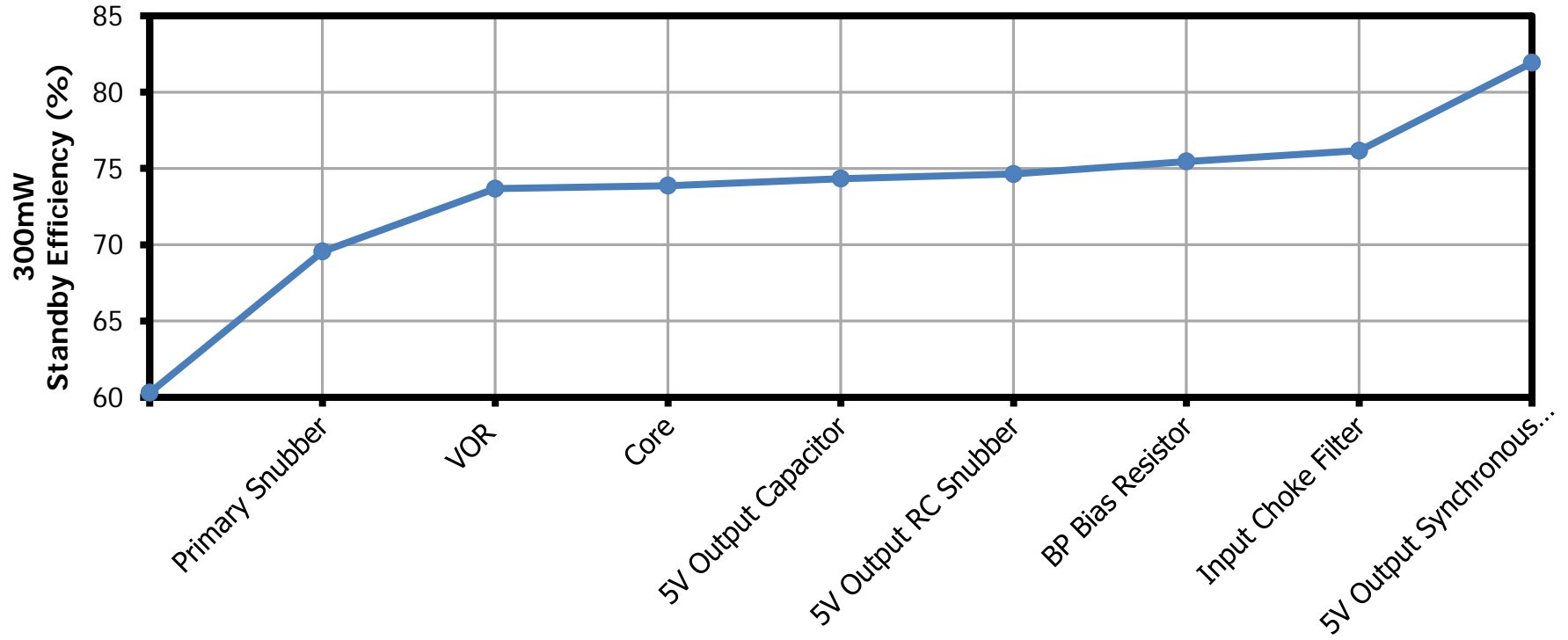

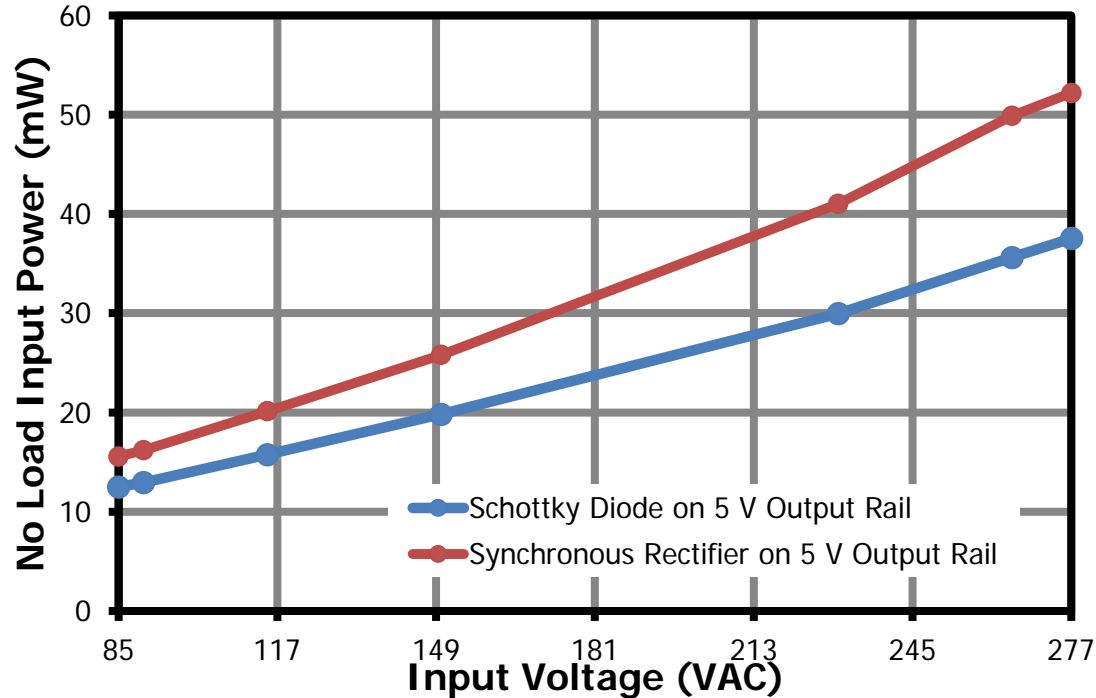
# Lower No-load Input Power Can Be Achieved By Using Diode Rectifier on 5 V Output

- Soak for 15 minutes and 3 minutes integration time for each line/step




# Load Regulation

## ■ 5 V output at 230 VAC input

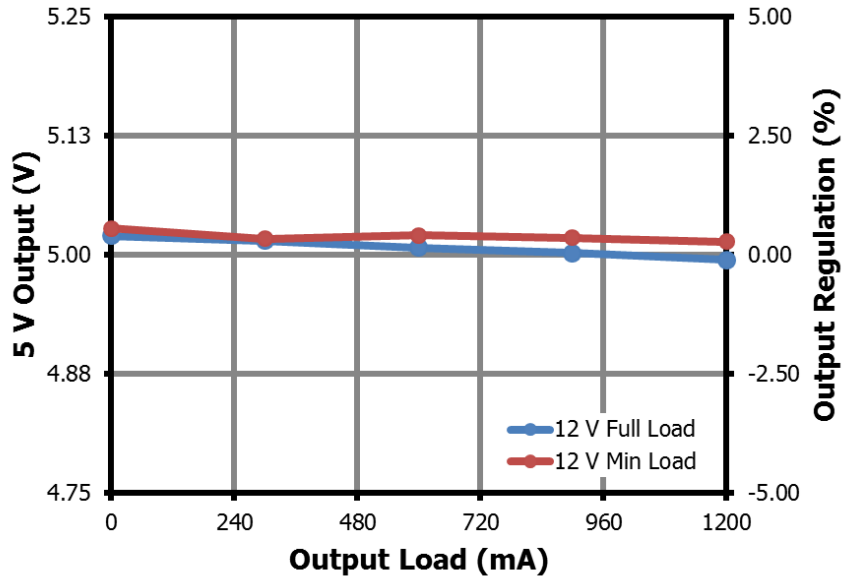

## ■ 12 V output at 230 VAC input

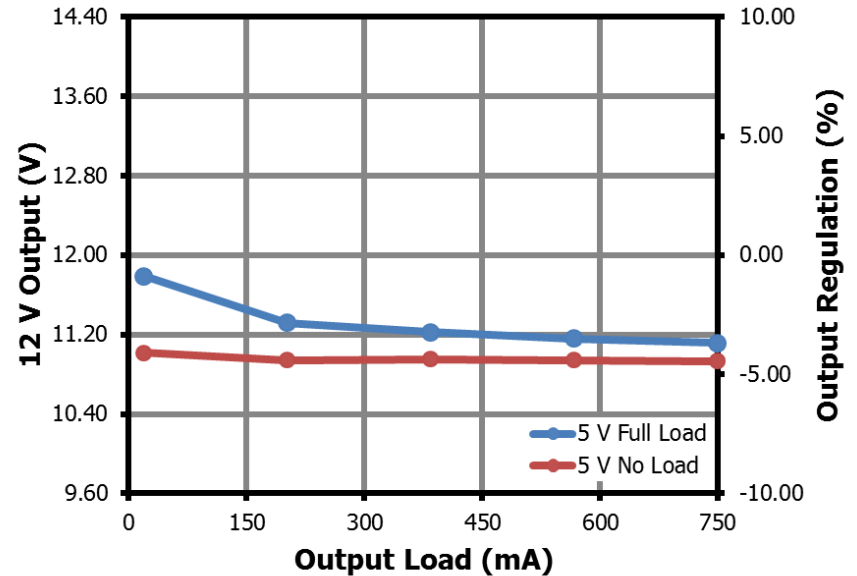

# Stress Analysis


Input Voltage	Operation	Output Load	Primary FET VDS		5 V Output Diode PIV		12 V Output Diode PIV	
			725 (V)	Derating	60 (V)	Derating	100 (V)	Derating
277 VAC	Normal Running	5 V/1.2 A 12 V/0.75 A	658	90.8%	36.8	61.4%	47.5	47.5%
		5 V/NL, 12 V/NL	627	86.5%	33.0	54.9%	48.4	48.4%
	Startup	5 V/1.2 A 12 V/0.75 A	656	90.5%	41.6	69.3%	74.0	74.0%
		5 V/NL, 12 V/NL	656	90.5%	38.6	64.3%	57.0	57.0%

# Conducted EMI Verification

## Can be effected by:-

- ▶ Transformer construction
- ▶ Input bulk capacitor ESR
- ▶ Differential inductor in  $\pi$  filter
- ▶ RC snubber
- ▶ PCB layout


Differential mode dominates

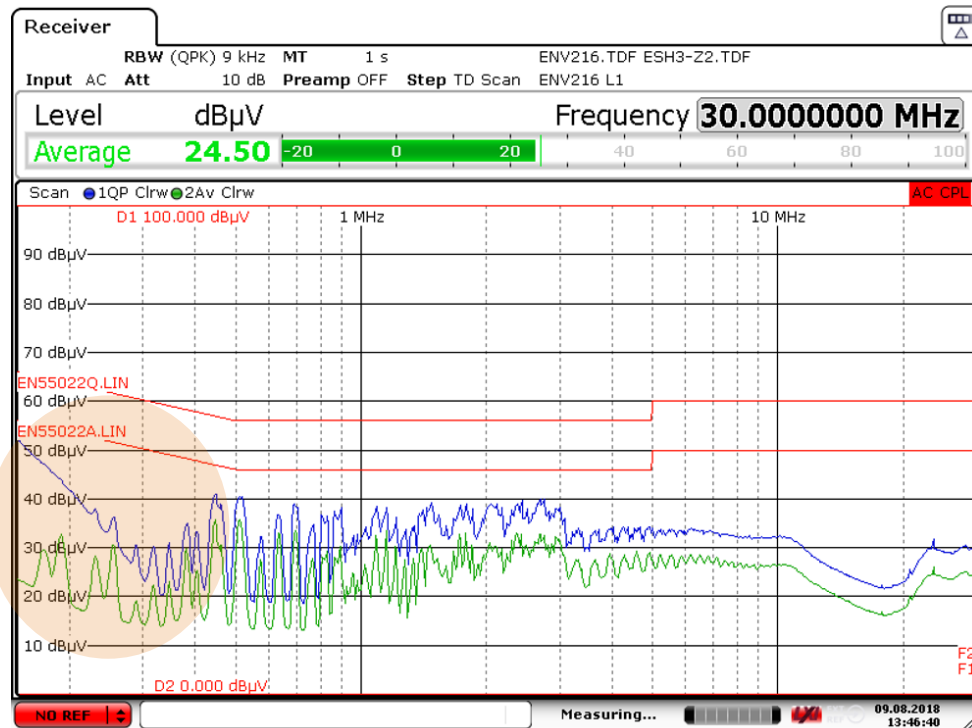

Date: 9.AUG.2018 13:46:40
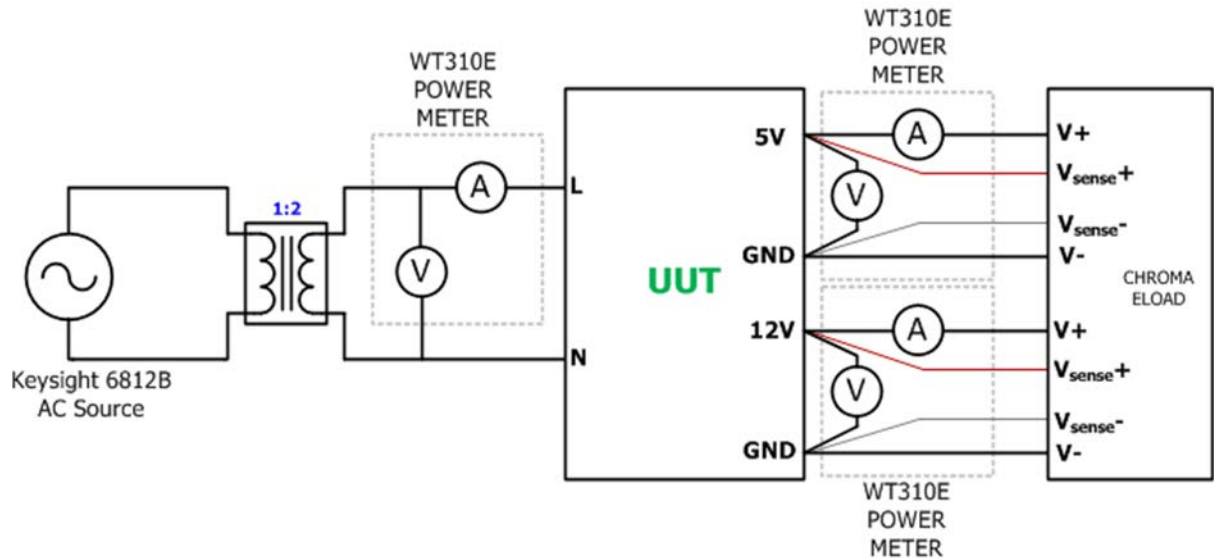
# Measurement Setup

- Applicable for standby efficiency and average efficiency measurement
- Input and output power meter settings
  - ▶ Line filter: OFF
  - ▶ Frequency filter: OFF
  - ▶ Sync: Volt
  - ▶ Averaging: ON
    - Linear, 32 points
  - ▶ Range
    - Voltage: AUTO
    - Current: AUTO





# Measurement Setup

## ■ Standby power measurement

- ▶ Set desired input AC voltage and apply full load across the 5 V and 12 V output
  - Soak time at full load: 240 seconds (4 minutes)
- ▶ Reduce load to meet desired standby input power (300 mW, 250 mW, 500 mW)
  - Soak time at standby load: 240 seconds (4 minutes)
- ▶ Record input/output voltage, current, and power measurements

## ■ Average efficiency measurement

- ▶ Soak time: 120 seconds
- ▶ Delay per line: 120 seconds
- ▶ Delay per load step: 120 seconds
- ▶ Reduction of load: 100%, 75%, 50% , 25%, 10%

# Input/output Conditions For Standby Efficiency Optimization

- **Input voltage: 230 VAC**
- **Input power: 300 mW**
- **Output load**
  - ▶ Increase 5 V load until target input power is reached
  - ▶ Assumes no-load on 12 V output