



GaN Integration Enables Next Generation USB-C Chargers with Ultra-High Power Density and Wide Output Voltage Range

Dr. Matthias J. Kasper, Dr. Jon Azurza & Dr. Gerald Deboy
APEC Industry Session 7.3
23 March 2022

Outline

1

Introduction

2

Charger Specifications

3

Topology Selection

4

Multi-Objective Optimization Results

5

Hardware Details and Measurement Results


6

Conclusion

Introduction: CoolGaN™ technology – Infineon well positioned to address key markets

GaN market forecast¹


[USD m]

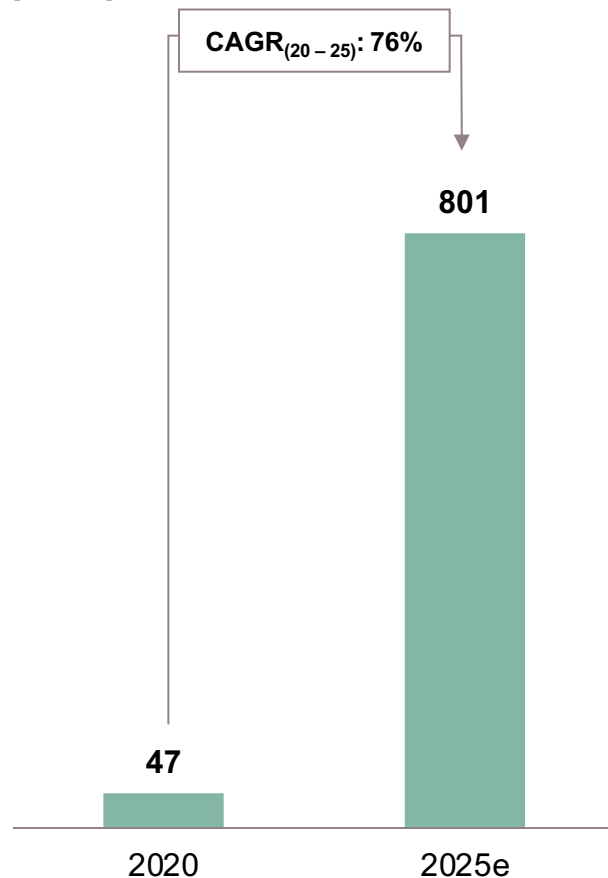


¹ GaN power devices market forecast. Yole Développement (Yole): *Compound Semiconductor Quarterly Market Monitor: From technologies to markets; Quarterly Update Module 1*. Q3 2021

Key values of GaN vs Si

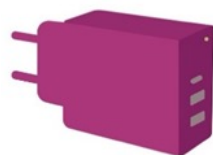
Higher power density in adapters and chargers



More power, same size

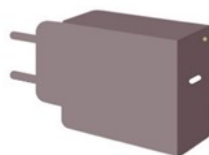

Current adapter

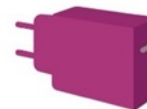

Same power, smaller size

10x

switching
frequency

> 2%

more power
efficiency

20%

lower
System Cost

25%

higher
power
density

3x




less
weight

We combine leading-edge system and application understanding with additional strengths:






Broad GaN IP portfolio, large R&D force and best-in-class manufacturing landscape

Applications

Focus applications

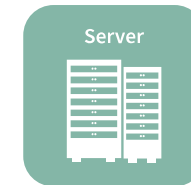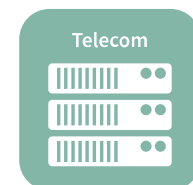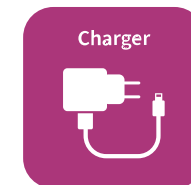


Emerging applications

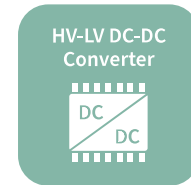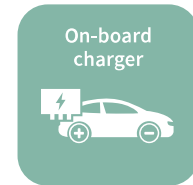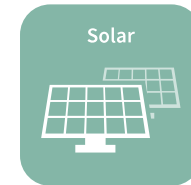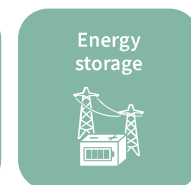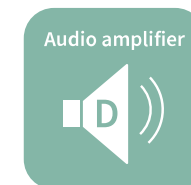

Specifications of the over-next 240W ultra-high density charger generation


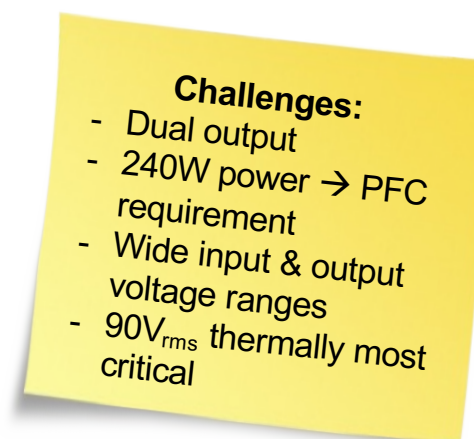
- › State-of-the-art 65W chargers soon no longer enough to charge all consumer devices → **Increase to future-proof 240W**
- › **Dual USB-C output ports** to support simultaneous charging of two mobile devices
- › Increase of **output voltage to 48V** (USB PD Rev. 3.1)



Charger specifications become more similar to other applications with 48V and >200W like SmartTVs or All-in-One PCs!


Efficiency & power density performance target for maximum case temperature

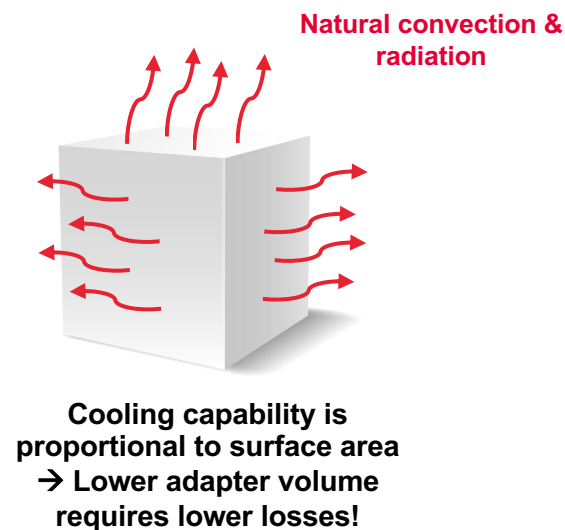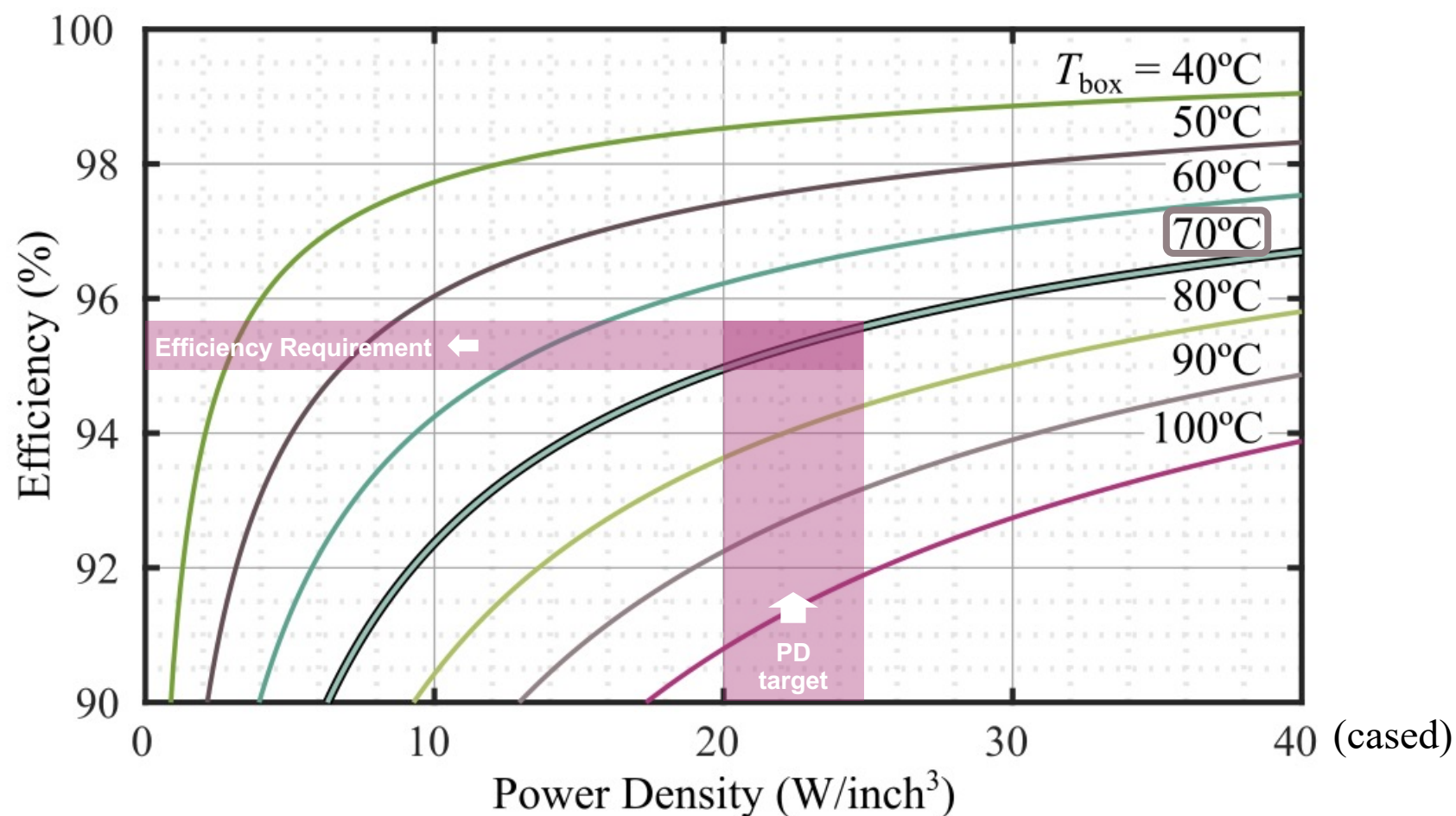- Increasing **power density** requires **higher efficiency** to keep **case temperature within limits!**




Possible topologies and system partitioning

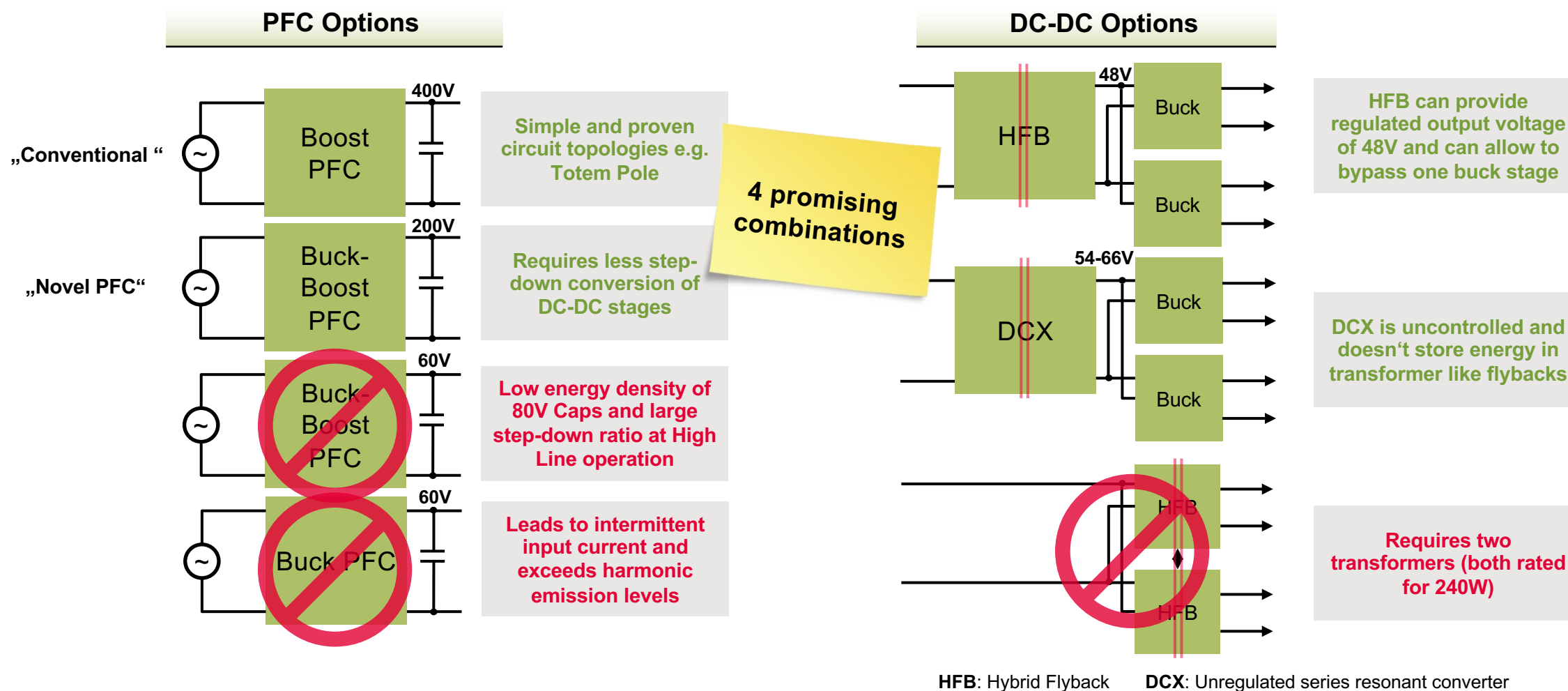- Final solution needs to have a **PFC**, **galvanic isolation**, and **two regulated output ports**.
- Based on circuit simulations and rough size/loss estimations several solutions can be ruled out for this project.



Multi-objective Pareto optimization


- › **Systematic approach** to consider all degrees of freedom
 - E.g.: Semiconductor technologies, # of HF legs in totem-pole, # of matrix transformers, switching frequencies, current/voltage ripples, magnetic component realizations, paralleling of switches
- › Comprehensive and **detailed modeling** of **components** and **systems behavior**
- › Finding **trade-offs** („Pareto-Front“) between **Efficiency, Power Density, and Costs**

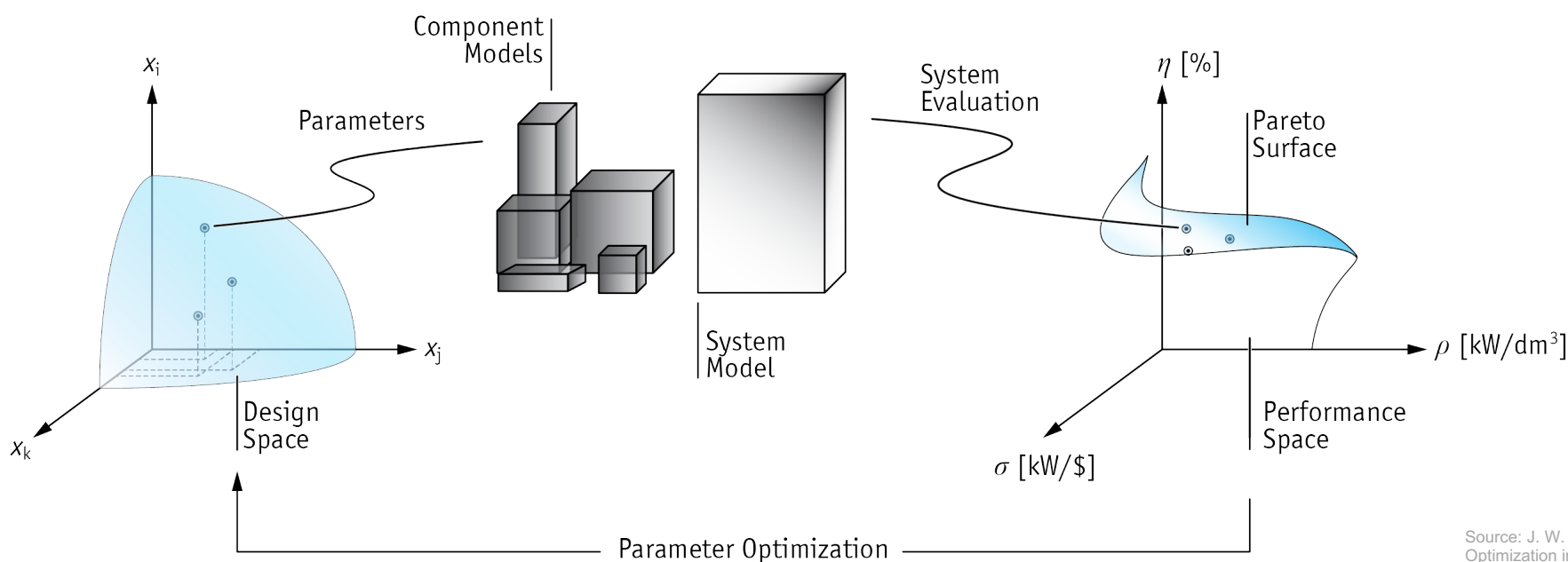

Source: J. W. Kolar, "Multi-Objective Optimization in Power Electronics", Plenary Presentation SPEC, 2016

Pareto optimization of 4 remaining converter options for the most challenging operating point

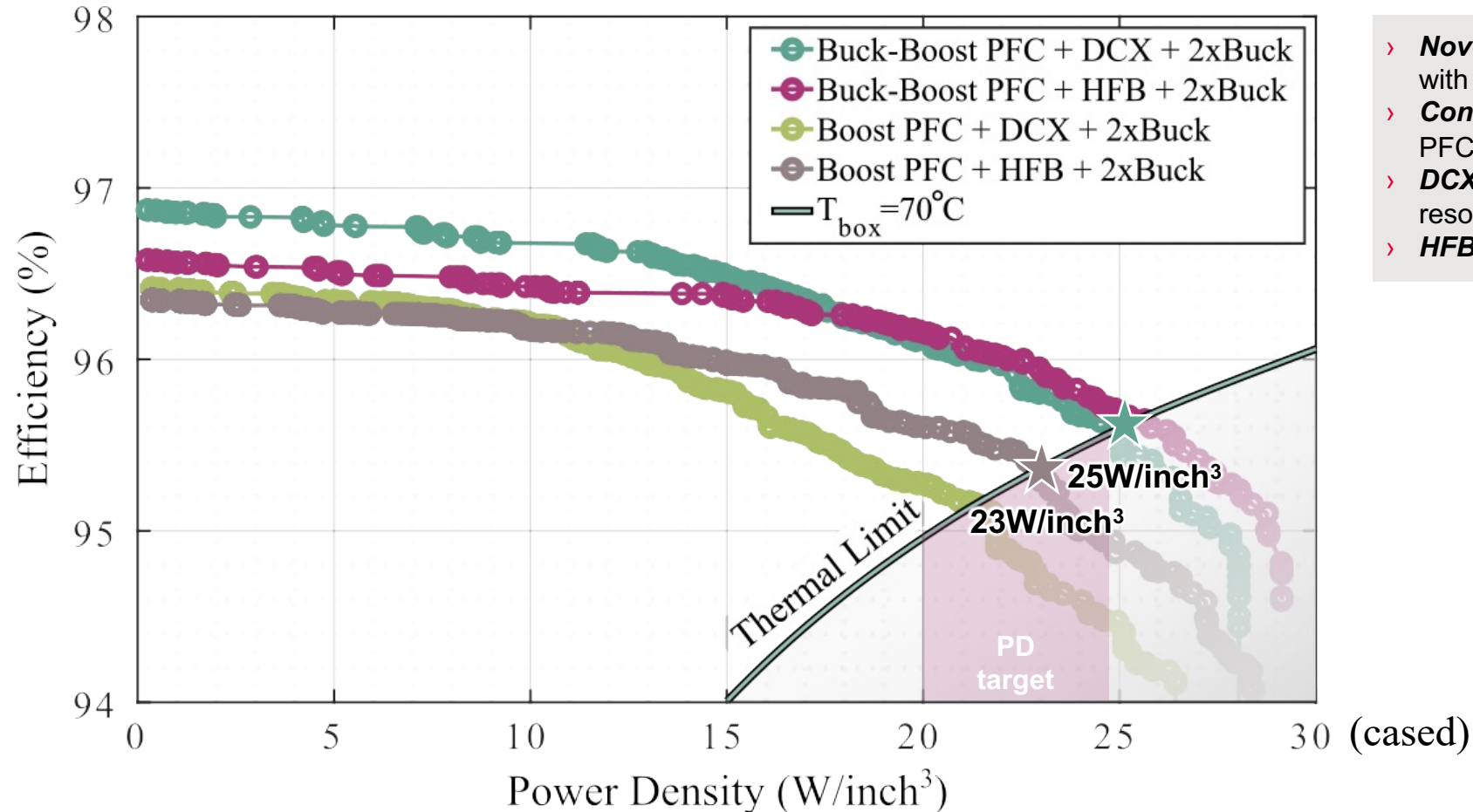- › Optimization results for **full load (240W)** and low line (**90V_{rms}**)



- › **Novel PFC**: Boost+Buck PFC with ~150V output
- › **Conventional PFC**: Totem-Pole PFC with ~400V output
- › **DCX**: unregulated series-resonant converter
- › **HFB**: Hybrid Flyback

Summary of optimization results

23 W/in³

**Conventional Solution (400V DC link):
TP + HFB + 2x Buck**

Why to use this solution:

- › Straightforward solution
- › Proven controllers
- › Explore higher frequencies (within bounds of controllers)

Risks:

- › Might miss target of 20W/in³
- › Not going to extreme power densities
- › Not learning about new topologies
- › Missing chance to go to „new territory“

25 W/in³

**Novel Solution (160V DC link):
Boost+Buck PFC + DCX or HFB + 2x Buck**

Why to use this solution:

- › Highest power density
- › Learning about new topology
- › Explore highest frequencies with proprietary control

Risks:

- › Not fulfilling requirements:
 - Standby power; Harmonics/EMI; Surge; ESD; Safety test (i.e. Short circuit)
- › Cost
 - High number of devices; controller development





Possibility to combine both solutions: „Boost Follower“ Totem-Pole which is a conventional Totem-Pole that is operated with lower DC-link voltage depending on line voltage



Boost-Follower PFC operation to maximize efficiency at low-line operation

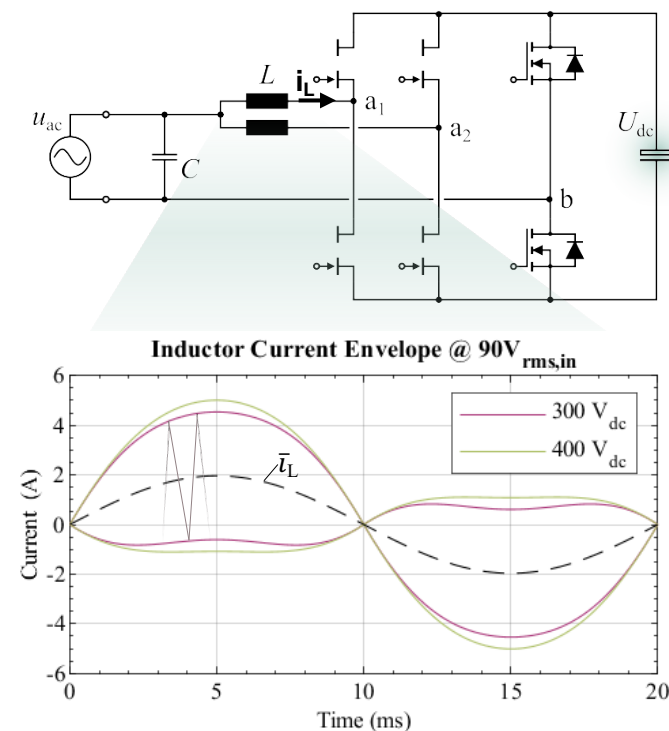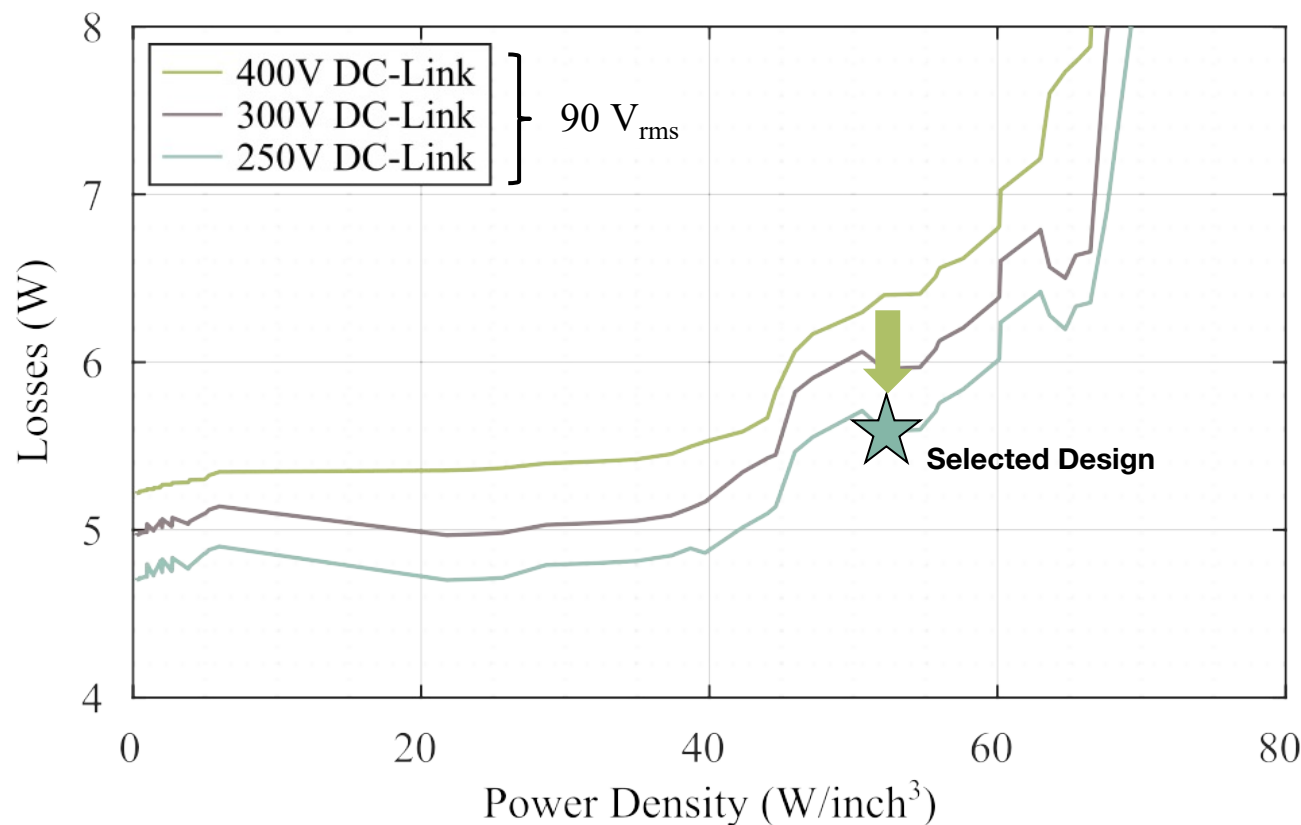- › Optimization of **Boost-Follower Totem-Pole PFC** stage at 240W and 90V_{rms} input




Novel Control Scheme: Variation of DC-link voltage for diff. line voltages to achieve ZVS at fixed f_{sw}

- › Reduction of losses at most critical 90V_{rms} operating point → High f_{sw} → Low converter volume
- › Simplified control without variation of switching frequency like in TCM control
- › Easier EMI filter design with defined noise spectrum

Hardware Demonstrator of Next-Gen 240W USB-C Charger

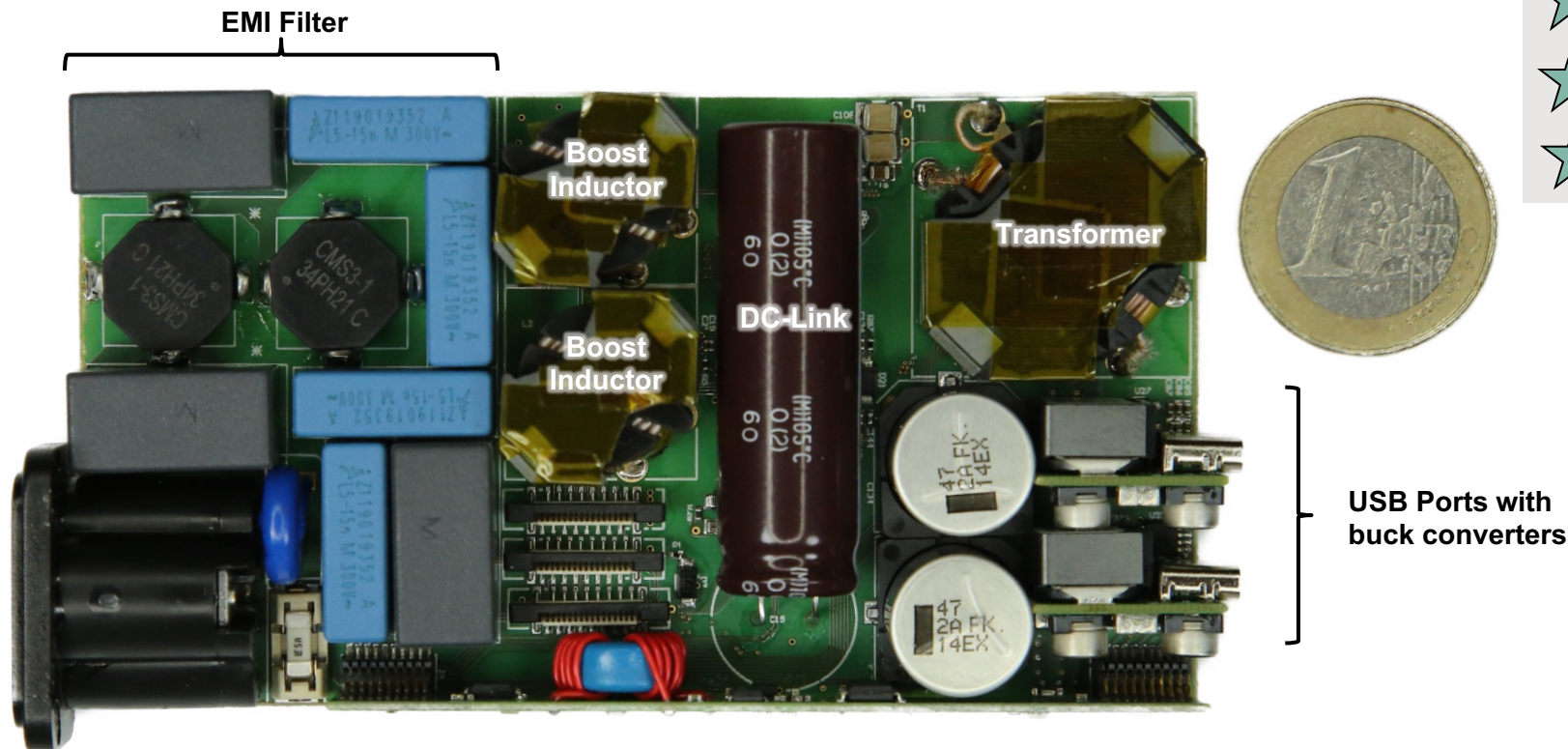
- › Dimensions: W x L x H: **100mm x 55mm x 17mm** without case



- ★ **42 W/inch³** (uncased, 24W/inch³ cased)
- ★ **113 g** (uncased)
- ★ **95.3 % Eff** (240W, 90Vrms)

Topology:

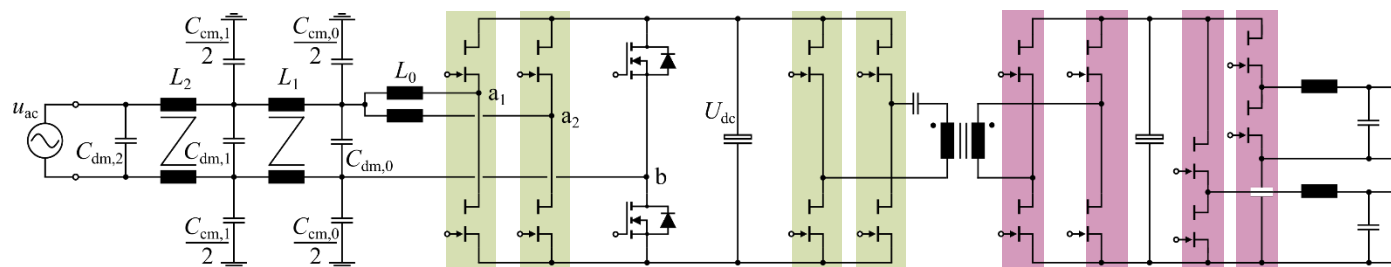- › **Interleaved Totem-Pole**
- › **DCX**
- › **ZVS Buck converter**



4x 600V 140mΩ_{typ} Integrated GaN Half-bridges

4x 100V 2.5mΩ_{typ} Discrete GaN Half-Bridges



PFC Stage – Details and Measurement Results


ZVS Totem-pole PFC with 2x interleaving

- › Fixed $f_{sw} = 400\text{kHz}$ CCM PFC
- › Effective 800kHz for EMI Filter
- › Large Δi_L ($L = 35\text{ }\mu\text{H}$, Litz Wire) for **natural ZVS** → For All Voltage Ranges
- › Operating-Point-Dependent U_{dc} variation to always achieve ZVS
- › Easy-to-Implement **Avg. Current Control**




- › CoolGaN™ GIT IPS
- › 600V 140m Ω_{typ}



- › CoolMOS™ Si-SJ
- › 600V 48m Ω_{typ}

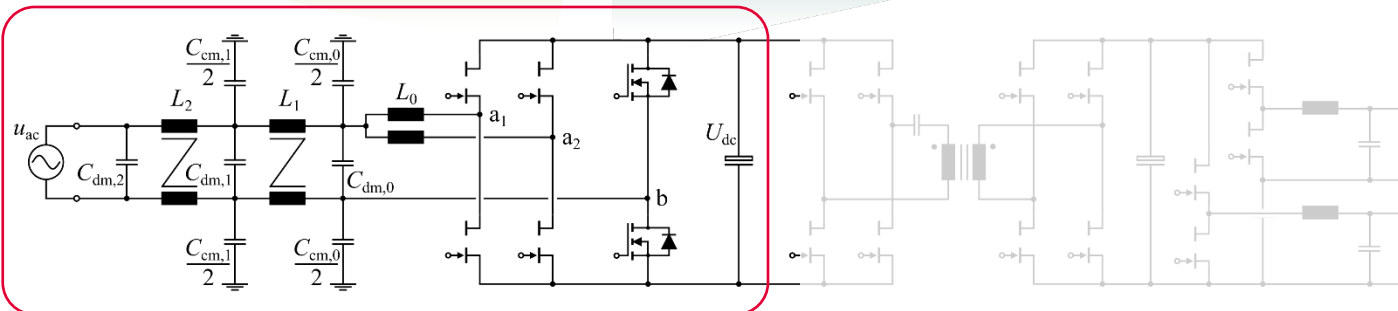

97.9% @ 240W, 120V_{in}, 300V_{out}

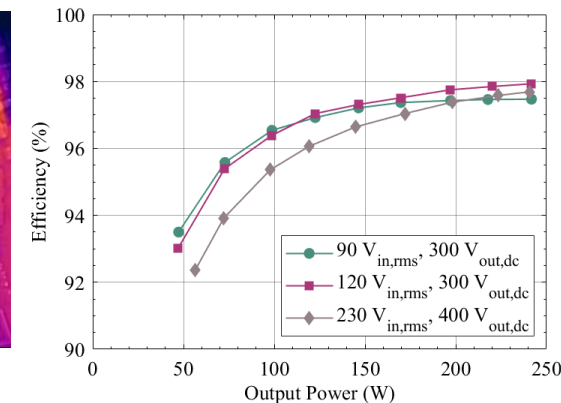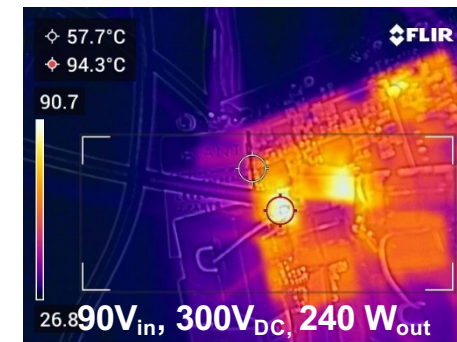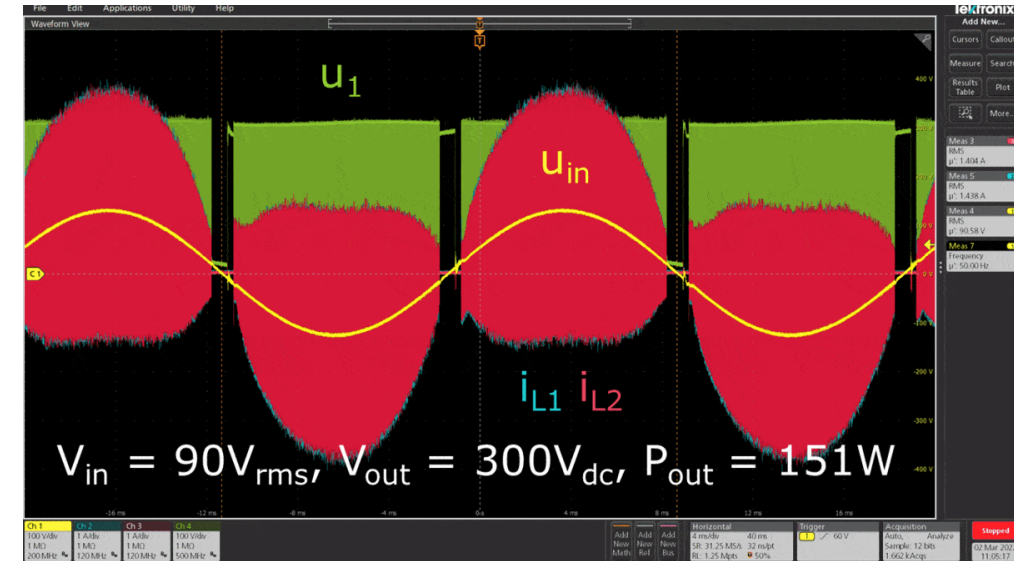


DCX stage details and measurement results

Unregulated DCX w/ Fixed Conversion Ratio ($N_1:N_2 = 28:5 = 5.6$)




- > $f_{sw} = 425\text{kHz} \rightarrow$ Very High Dynamics
- > Load independent ZVS in all operating points
- > Small overall size by utilizing leakage inductance ($L_r = 12.6\mu\text{H}$, Litz-Wire) of transformer as resonance inductor
- > Full-Bridge & Full-Bridge configuration allows to start-up with discharged output with duty-cycle modulation

> CoolGaN™ GIT IPS
 > 600V 140mΩ_{typ}

> CoolGaN™ SG
 > 100V 2.5mΩ_{typ}

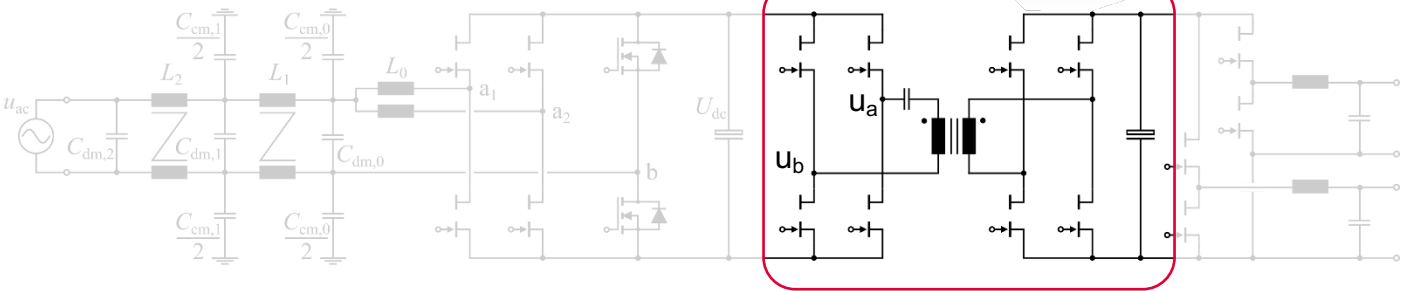

★ 98.3% @ 240W, 300V_{in}, 52V_{out}

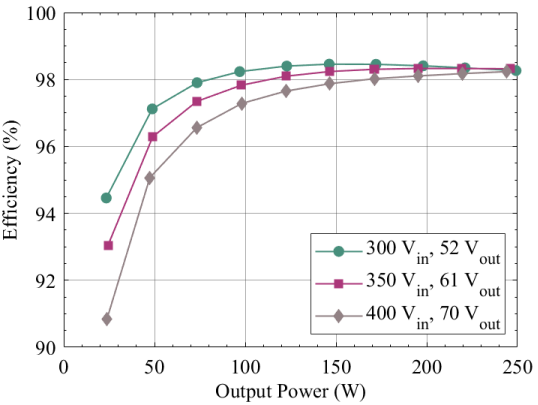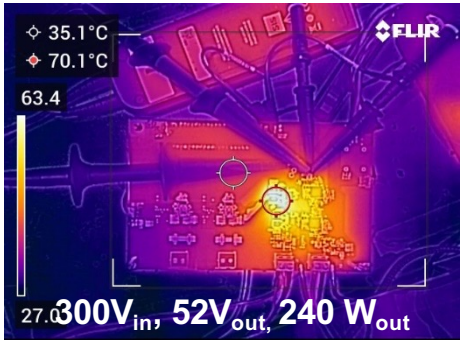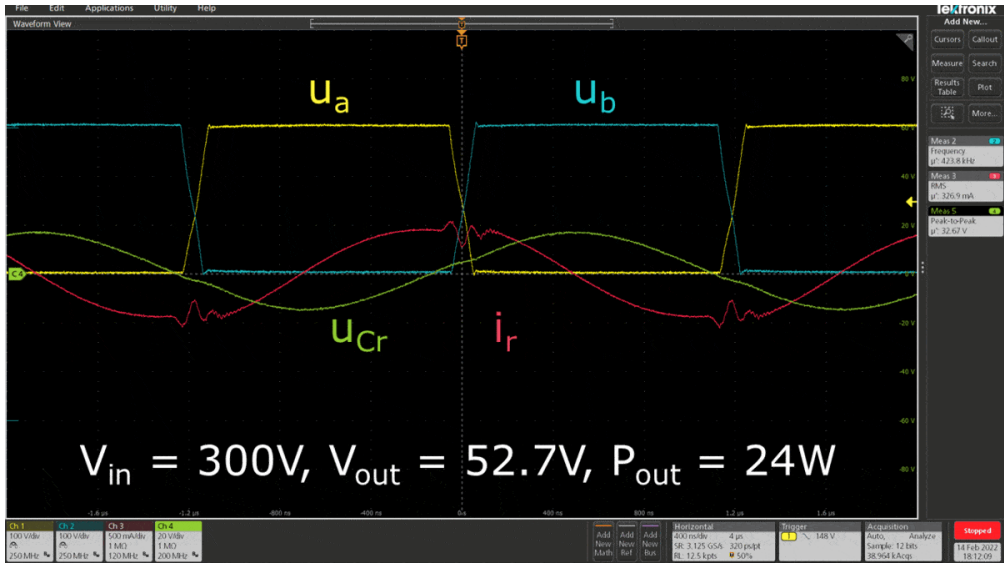


ZVS Buck Converter Stage




Full-ZVS Buck Stage

- › ZVS in All Operating Points
- › Enabled by:
 - Variable frequency: $f_{sw} = 120...420$ kHz
 - Optimal Inductor Design ($L = 3.6 \mu\text{H}$, Litz-Wire)


★ 99.3% @ 240W, 55V_{in}, 48V_{out}

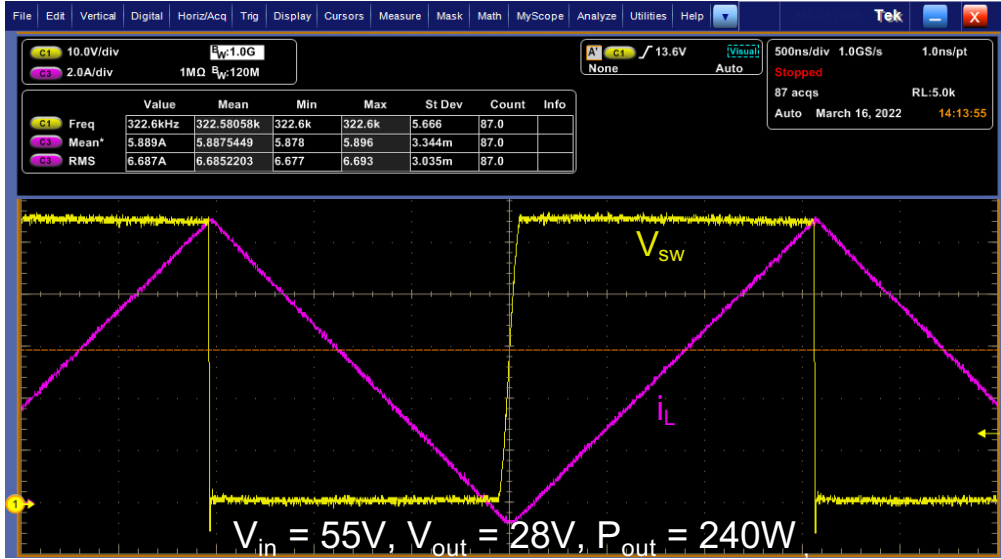

› CoolGaN™ SG
› 100V 2.5mΩ_{typ}

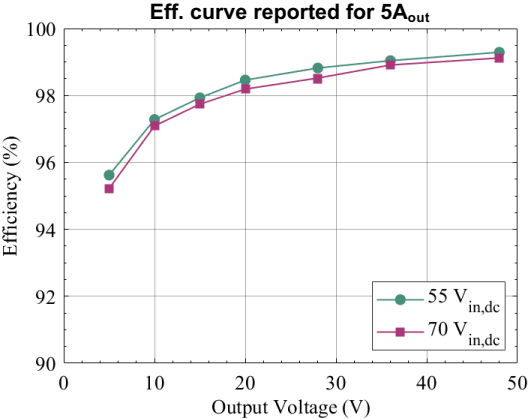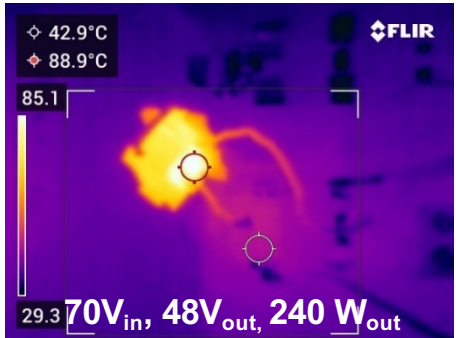
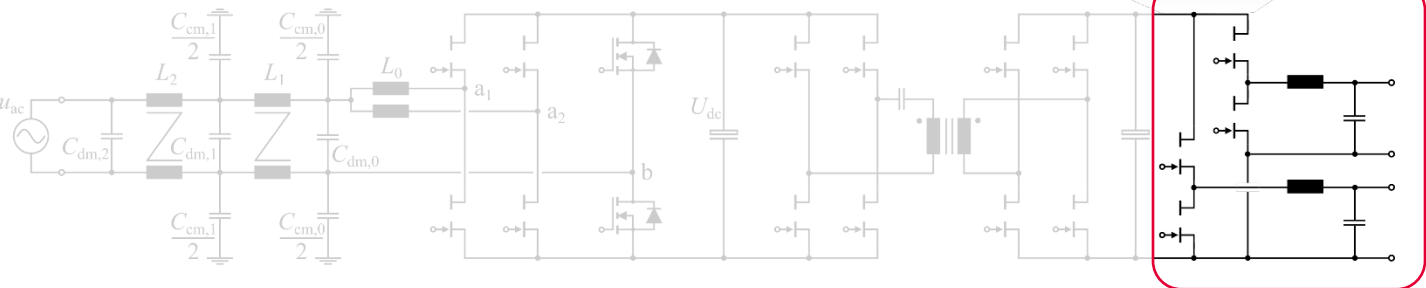


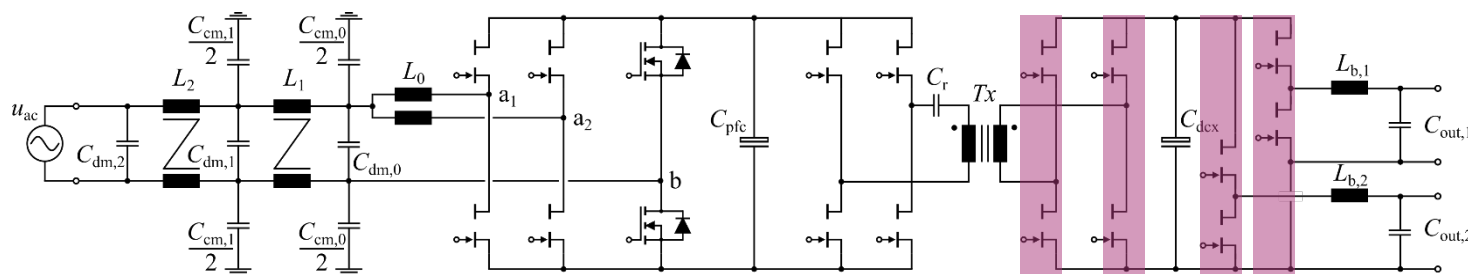Outlook: 100V CoolGaN™ SG Integrated Power Stage



Size and BOM reduction with integrated 100V power stages


- › **Half-bridge** multi-chip module (MCM) in **6x9 mm laminate package**:
 - **2x 100V 2.5mΩ_{typ} CoolGaN™ SG HEMTs** in half-bridge configuration
 - **GaN-optimized half-bridge gate driver with regulated bootstrapping supply**
 - **ALL high-frequency capacitors included!** – PCB layout has no impact on switching performance or overshoot voltages, even on a single-layer PCB
- › **Thermally optimized** package
 - Copious thermal microvias connecting to large PCB pads
 - Galvanically isolated top-side metal pad for easy heatsink attachment

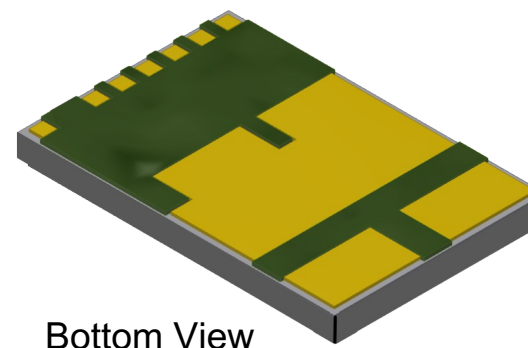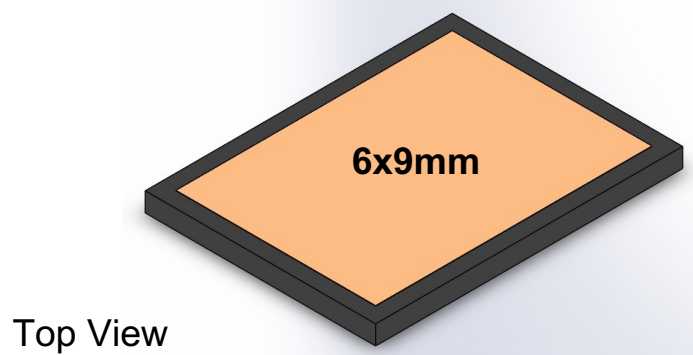

Conclusions

- › Unprecedented 240W USB-C charger power density (42 W/inch³ & 113g uncased, 24W/inch³ cased)
- › Thoroughly optimized system performance due to Infineon's comprehensive technology portfolio and system expertise:

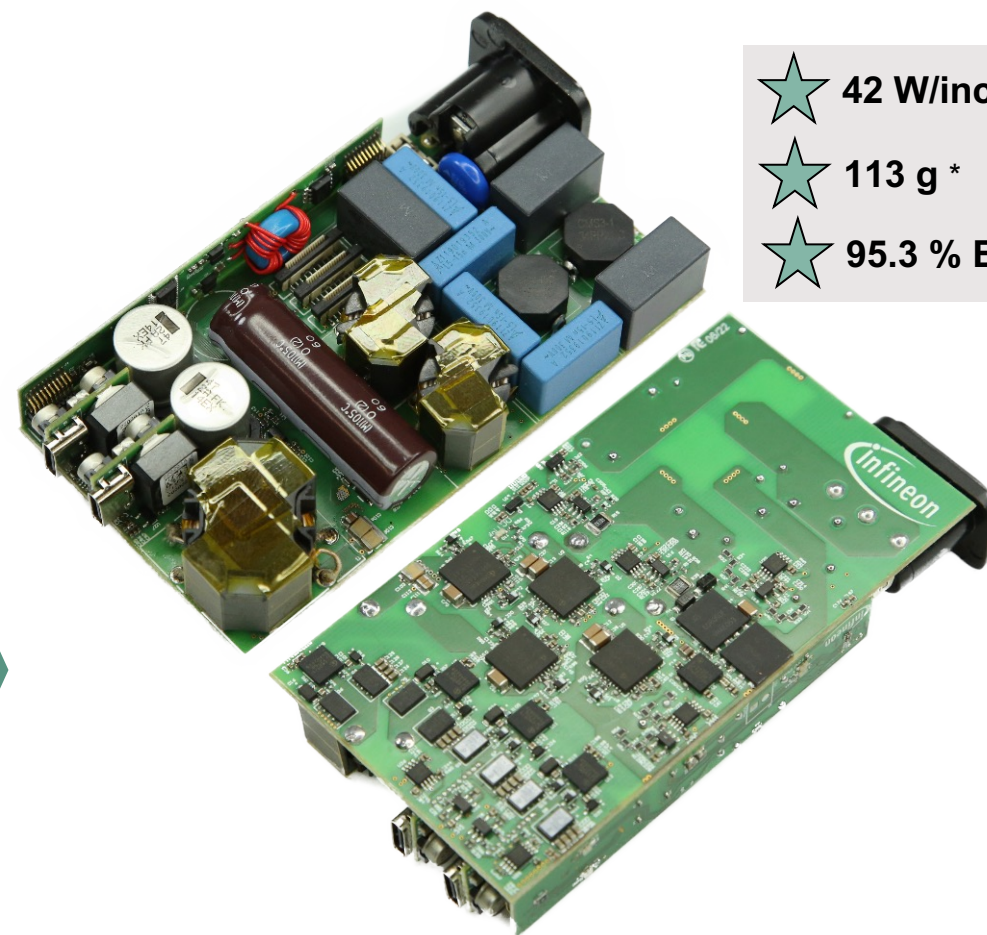- 600V CoolGaN™ GIT Integrated Power Stage
- 100V CoolGaN™ Schottky Gate HEMTs
- Matching gate drivers
- Digital control with advanced modulation methods
- Pareto multi-objective system optimization



★	42 W/inch ³ *
★	113 g *
★	95.3 % Eff (240W, 90Vrms)

* Uncased

Thank you for your interest!


Dr. Matthias J. Kasper, Dr. Jon Azurza & Dr. Gerald Deboy
Email: jon.azurza@Infineon.com



Part of your life. Part of tomorrow.

Infineon CoolGaN™ Solutions for 600V and 100V

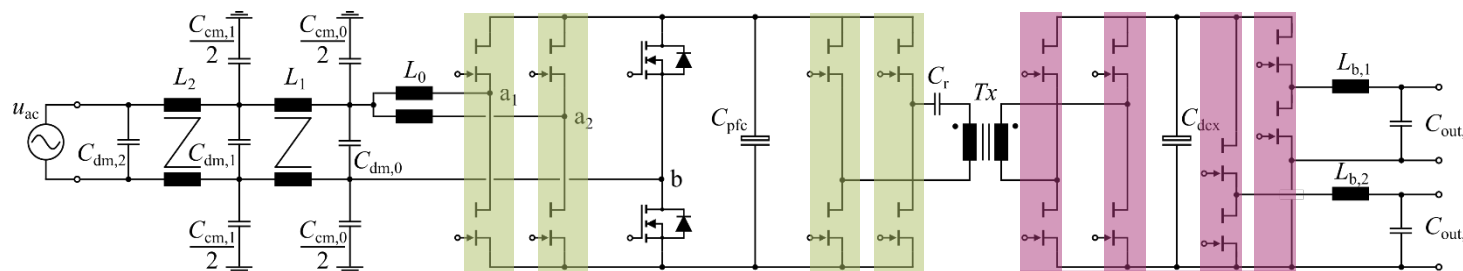Topology:
Interleaved Totem-pole &
DCX & ZVS Buck converter



4x 600V 140mΩ_{typ} Integrated
GaN Half-Bridges

4x 100V 2.5mΩ_{typ} Discrete
GaN Half-Bridges



**600V CoolGaN™ GIT Integrated
Power Stage (IPS)**

- › Isolated digital input with digital-in, power-out building block
- › Application configurable switching behavior
- › Fast, highly accurate, and stable timing
- › Thermally enhanced 8x8mm QFN-28 and 6x8mm QFN-26 packages



**100V CoolGaN™ Schottky Gate
(SG) HEMT**

- › Lower Q_{oss} & more linear C_{oss}
- › Lower Q_G and no Q_{rr}
- › 3x5 mm PQFN package with dual-sided cooling



TDI EiceDRIVER™ for SG GaN

- › Optimized driving strength – no gate resistors
- › Featuring TDI & active Miller clamp
- › 1.8x1.8mm TSNP package