


Benefits of Million Times Larger Capacitance in EDLCs: Supercapacitor Assisted Novel Circuit Topologies

Nihal Kularatna
School of Engineering
The University of Waikato
Hamilton
New Zealand




THE UNIVERSITY OF
WAIKATO
Te Whare Wānanga o Waikato

Normal capacitors and their limits

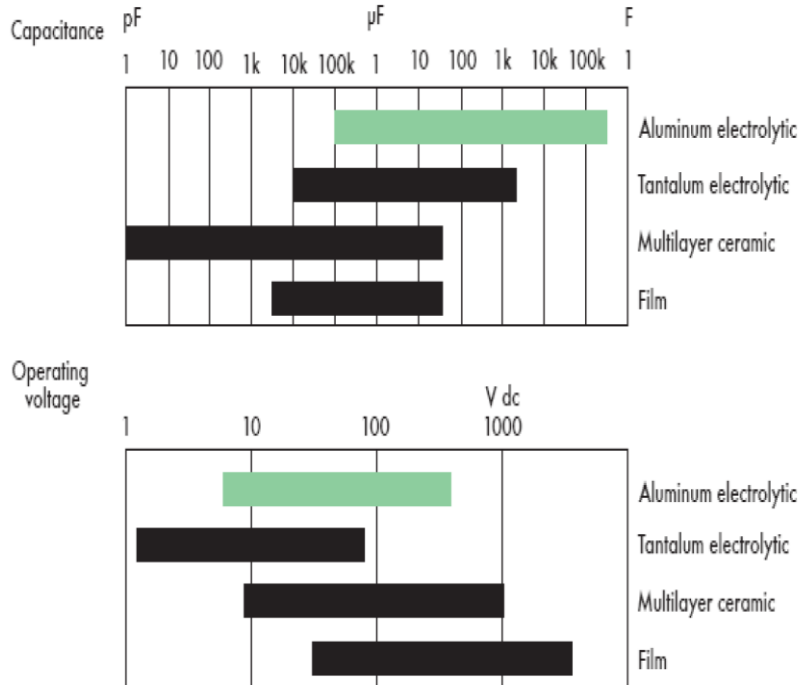

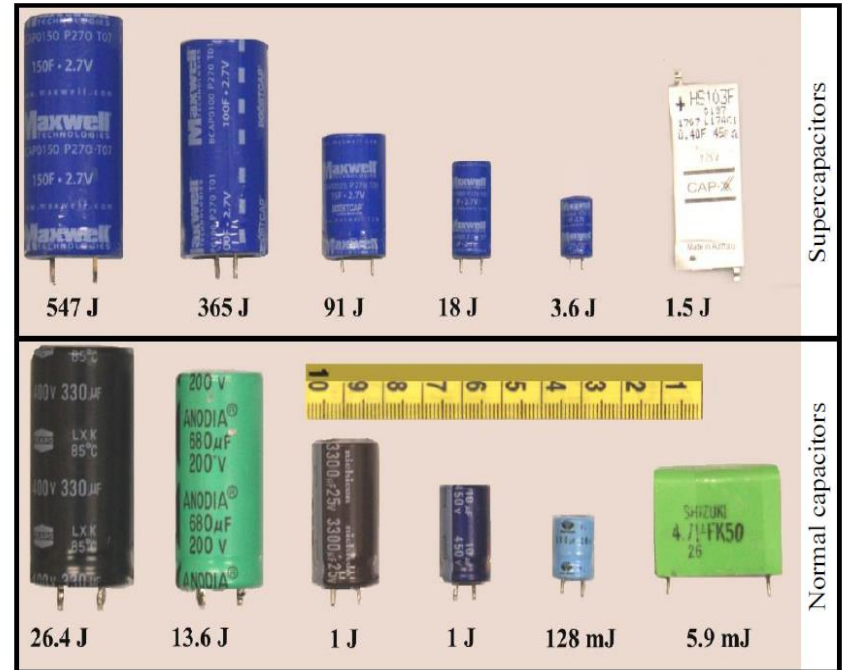Physical Comparison of Supercapacitors (SC) and Electrolytic Capacitors




2. Common dielectric materials, i.e., aluminum oxide, tantalum tetroxide, titanium oxide barium, and polyester polypropylene, also pose limits on capacitance level and operating-voltage capabilities.

Source: Dirjish,.M., Ultracapacitors branch out to wider markets, Electronic Design , On line ed, Nov 17, 2008

Typically, in SCs we get approximately one million times bigger capacitance, but at the penalty of very low DC voltage rating

Supercapacitors versus batteries

Ragone Plot

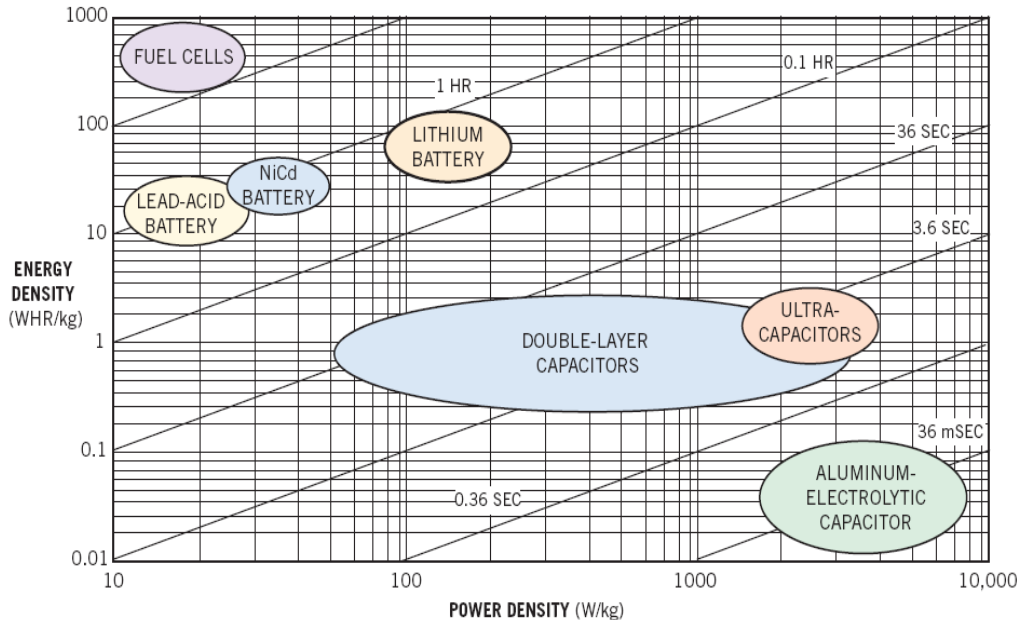

Internal resistance with depth of discharge

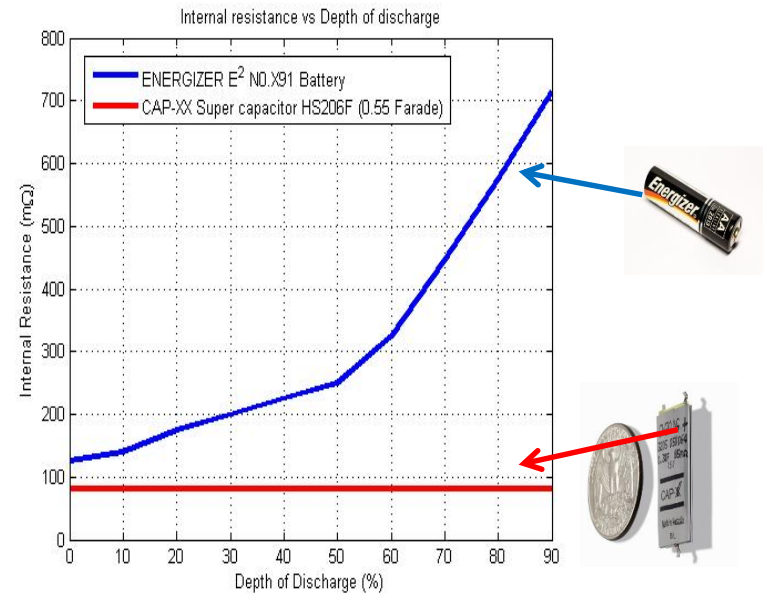


Figure 1

Graphing energy density against power density, conventional batteries occupy the top-left position, and conventional aluminum-electrolytic capacitors occupy the bottom-right. Supercapacitors bridge the space between. Diagonal lines are lines of equal discharge time into a specified load (courtesy Maxwell Technologies).

54 EDN | JANUARY 9, 2003

SCs with constant and very low ESR can deliver much higher power into a load than a electrochemical battery, where ESR keeps increasing with the discharge.

SCs versus electrolytics

TABLE 2. COMPARISON OF TYPICAL ELECTROLYTIC CAPACITORS AND SUPERCAPACITORS FOR THEIR ESR VALUES AND OTHER USEFUL SPECIFICATIONS						
ENERGY STORAGE LIMIT	CAPACITOR TYPE	MANUFACTURER	PARAMETERS			
			CAPACITANCE ($\mu\text{F}/\text{F}$)	TERMINAL VOLTAGE (V)	SHORT CIRCUIT CURRENT (A)	ESR ($\text{m}\Omega$)
Less than 1J	Electrolytic	RSS	2200 μF	16	104	153
1-5 J	Supercap	Maxwell	1 F	2.7	3.85	700
		Cap-xx	2.4 F	2.3	115	20
	Electrolytic	Cornell Dubilier	2200 μF	50	704	71
5-50 J	Supercap	Maxwell	10 F	2.5	14	180
		Cap-xx	1.2 F	4.5	112.5	40
		Nesscap	10 F	2.3	33	70
	Electrolytic	Cornell Dubilier	82,000 μF	16	1441	11.1
		VICOR	270 μF	200	325	614
Above 50 J	Supercap	Maxwell	350 F	2.7	840	3.2
		Nesscap	120 F	2.3	144	16

In general, SCs have lower ESR than the electrolytic capacitors, but their DC voltage rating is very low.

Traditional Applications of Supercapacitors


- In general supercapacitors have much less energy density than batteries
- But their power delivery capability (Watts/kg) is quite high compared to batteries
- Large supercapacitors have very low ESR in the range of few mΩs to fractional mΩs

Common supercapacitor applications are in

- UPS systems
 - Wind turbine systems
 - Electric vehicles/ Fork lifts/ Hybrid buses
 - Utility voltage stabilizer systems
 - Photo voltaic systems
 - Memory back up systems
-
- In many of these applications battery-supercapacitor hybrid systems are used

Capacitors used in simple DC blocking circuits

- We use electrolytics and ceramics as simple DC blocking elements in amplifiers
- When a circuit is powered, the DC blocking capacitor charges to the difference in voltages within micro to millisecond time periods
- Typical values used are from few nanofarads to tens of microfarads
- If we replace a 1 μF blocking capacitor with a 1 F capacitor the circuit will take **one million times longer to reach its steady state of blocking!**

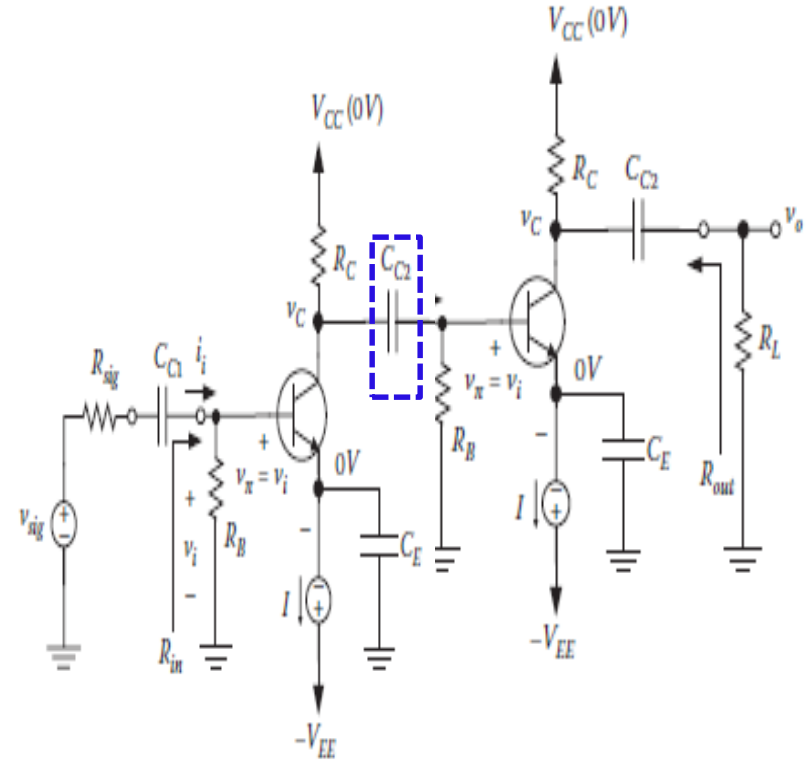

This gives you a different starting point to think of using the SCs in circuits more creatively!

Typical characteristics of SCs useful in analog and power electronic circuits

- They are approximately 20 to 100 times larger energy density than electrolytic capacitors
- Larger the SC, ESR is lower
- Typical ESR values are
 - 30 to 100 mΩ for 0.1 to 2F capacitors (such as the thin profile Cap-XX types)
 - 100 to 1000 mΩ for 1 to 100 F
 - 0.3 to 2 mΩ for 600 to 5000 F devices




Smaller ESR of SCs allow them to be used for short term high power delivery

Supercapacitors as lossless voltage droppers in linear power converters


- A capacitor carrying a charge or discharge current of I_L for a time period of Δt changes the voltage across the capacitor by

$$\frac{I_L \Delta t}{C}$$

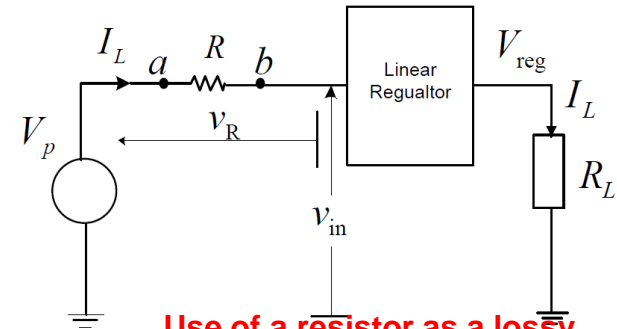- If the capacitor is very large this ΔV will be very small
- A supercapacitor (one million times larger than an electrolytic), will not be fully charged for a long time to block the circuit
- In supercaps, ESR is very small and this causes only a negligible voltage drop across ESR
- In larger SCs ESR can be significantly lower than the on resistance of commonly used MOSFETs



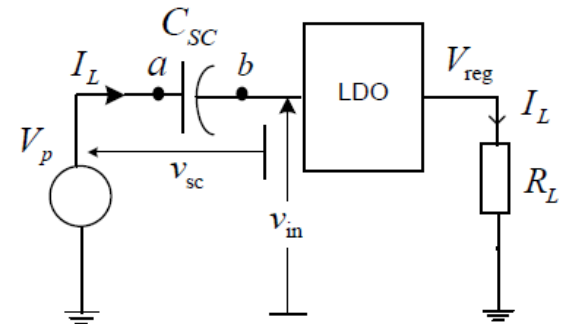Use of a resistor as a lossy dropper with a linear regulator




Use of a supercap as a lossless dropper with an LDO

This allows us to use SCs as lossless droppers in linear power converters

How SCs help increasing the efficiency of linear DC-DC converters

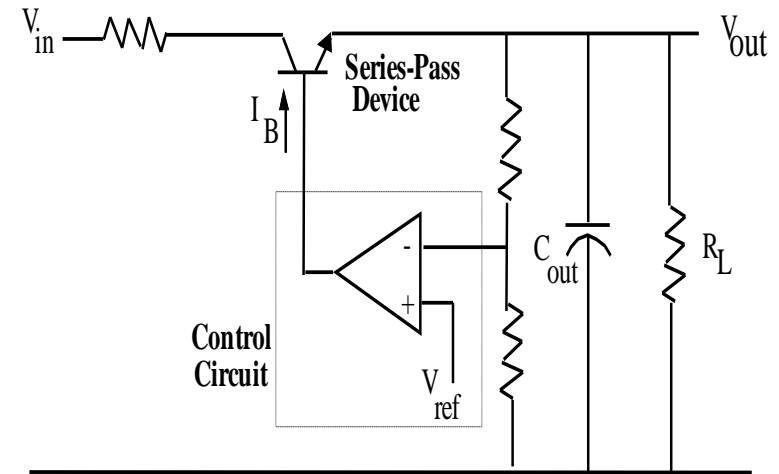- Linear DC-DC converters have low noise RFI/EMI free DC output
- However, they are very inefficient
 - 12-5V converter has a theoretical maximum efficiency of 42%
 - 5-3.3 V converter gives you only 66% efficiency
 - Efficiency is given by $\frac{V_o}{V_{in}}$




In a typical linear regulator series pass transistor wastes energy

- Higher the voltage difference between the input and output side the loss is higher
- In low dropout regulators (LDO) efficiency is high due to smaller input-output voltage difference
- If we can insert a lossless voltage dropper in the series path we can reduce the waste of energy
- A capacitor in series can help here, as far as it does not block the circuit

SC assisted low dropout regulator (SCALDO) technique makes use of a supercapacitor to achieve a lower input-output voltage difference


Basic concept of the SCALDO technique

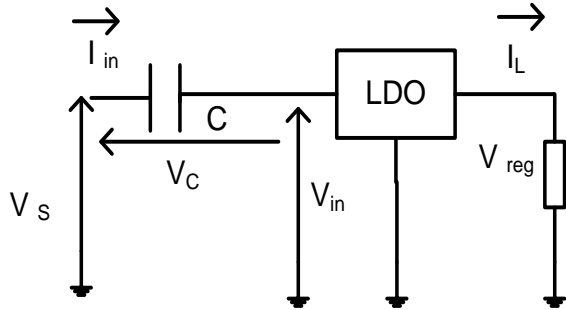Use a very large capacitor in series with LDO



- Series SC charges until it reaches the minimum input voltage of LDO $V_{in,(min)}$
- At the end of the charging time voltage across the SC reaches $(V_s - V_{in,(min)})$
- This supercapacitor will be discharged later up to $V_{in,(min)}$, $V_s > 2V_{in,(min)}$

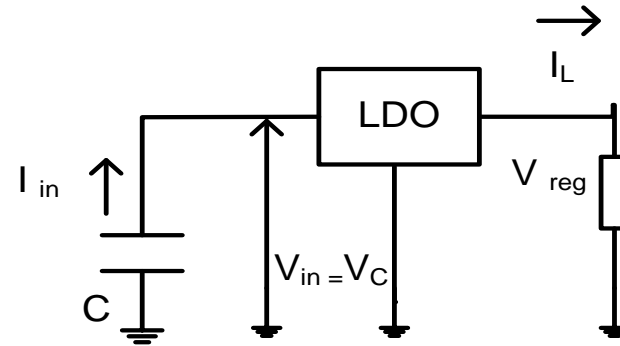Reuse of energy stored in the first part of the cycle



- Series SC charges until reaches min. input voltage of LDO $V_{in,(min)}$
- At the end of the charging time voltage across the SC reaches $(V_s - V_{in,(min)})$
- To discharge this supercapacitor later up to $V_{in,(min)}$, $V_s > 2V_{in,(min)}$

The above approach allows us to develop a linear DC output converter with a energy re-circulation frequency, typically in the range of millihertz to fractional hertz

Practical implementation of the SCALDO technique

- SCALDO technique allows you to build very high efficiency linear regulators

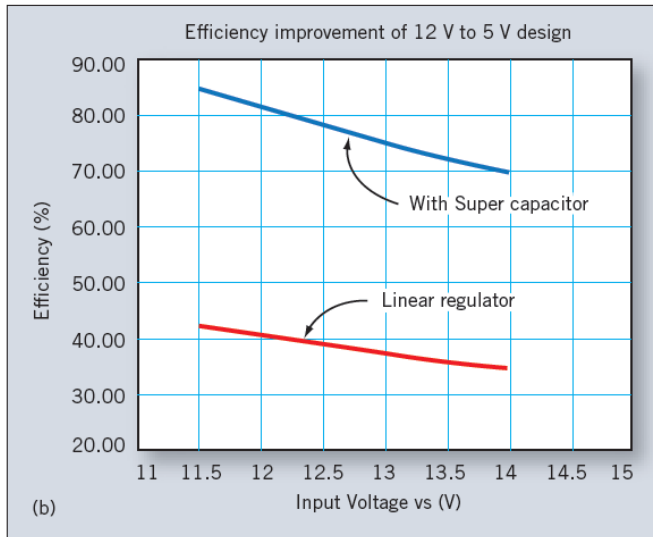
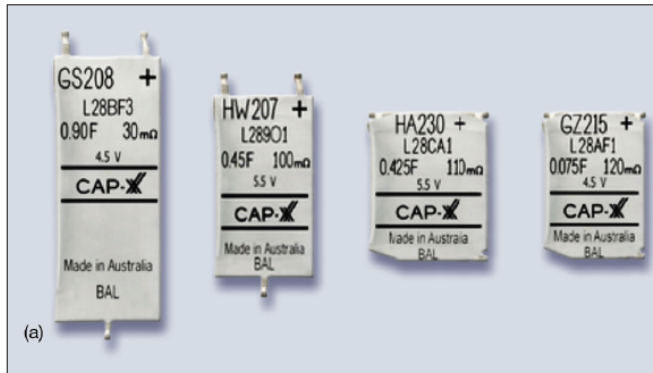


Fig. 3(a) Capacitor size reductions in an early prototype for 12-5V regulator supercaps used. (b) Shows efficiency improvements in 12-5 V regulator supercaps.

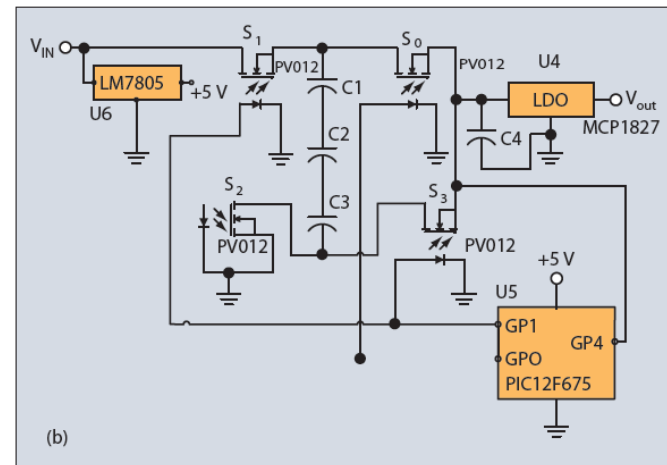
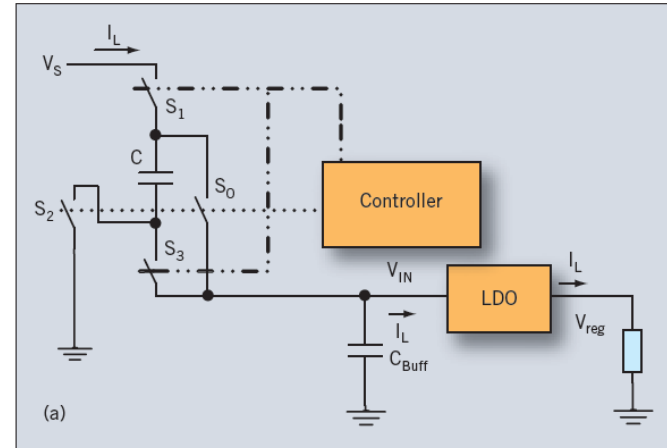






Fig. 4(a) The 12 V to 5V circuit to achieve efficiency improvements shown in Fig. 4(b). The implementation in Fig. 4(b) is shown using a PIC microcontroller.

In a typical SCALDO circuit such as this 12-5V converter we get an efficiency improvement factor of 2

SCALDO Applications and Advantages

- SCALDO uses the low ESR advantage and the large capacitance of the device
- Topology runs at very low frequency (milli-hertz to few 10s of Hz)- No RFI/EMI issues
- Load always see the high quality output of a linear regulator
- **It helps with an efficiency multiplication factor in the range of 1.33 to 3**
 - For a 12-5V converter it is a factor of 2 (giving 84% theoretical efficiency)
 - For a 5-3.3 converter this factor is 1.33 (88% theoretical efficiency)
 - For a 5-1.5V converter this factor is 3 (90% theoretical efficiency)

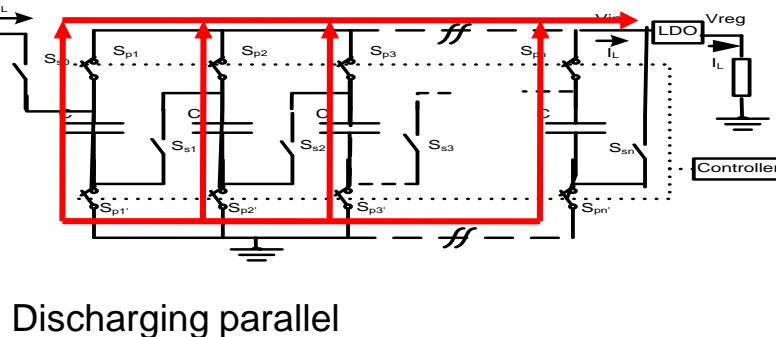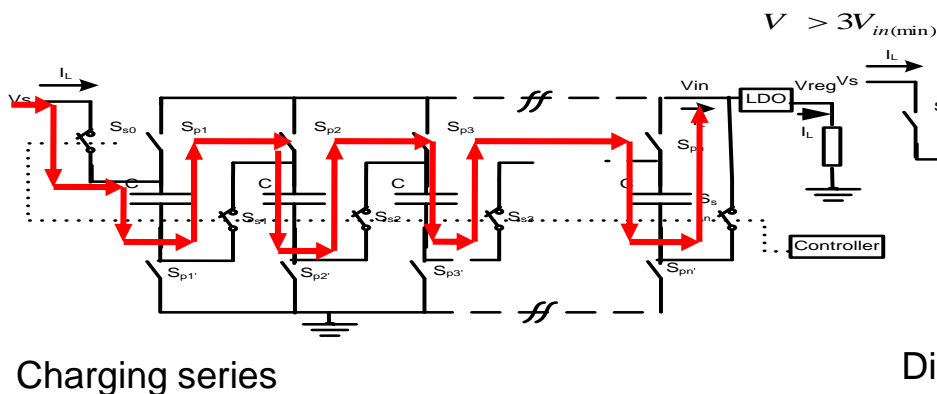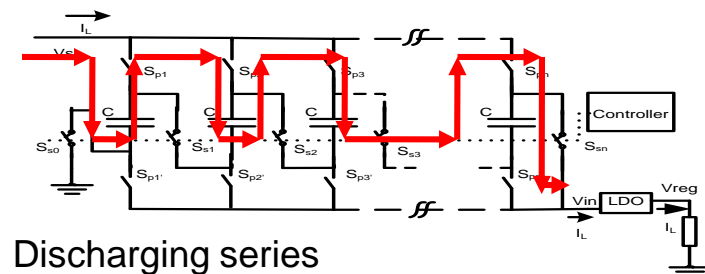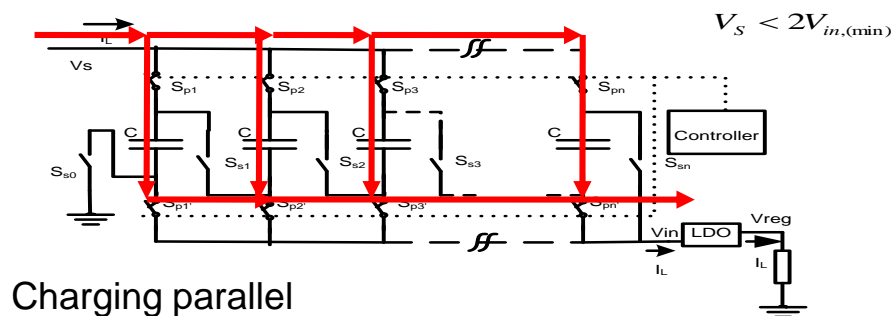SCALDO Configurations for 5-3.3V and 5-1.5V requirements



SCALDO variations

RS-SCALDO technique for high current converters

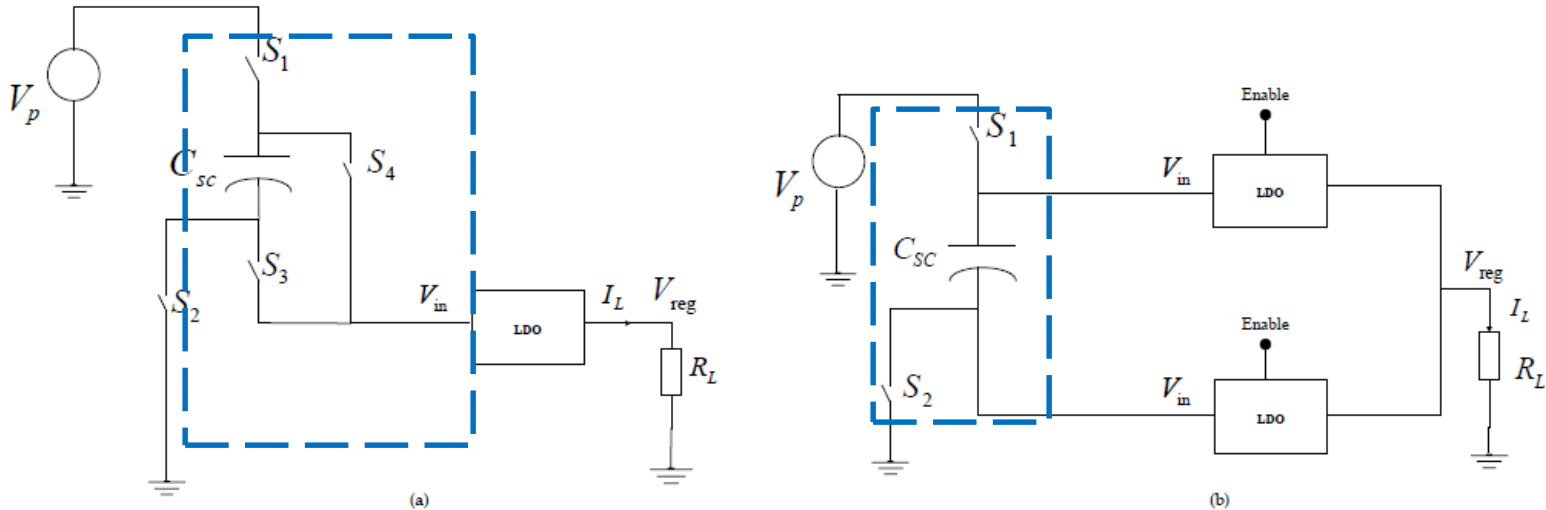


Figure 1.1: (a) Basic SCALDO configuration with single LDO and 4 switches (b) Modified RS-SCALDO (Reduced switches) configuration with two identical LDOs and two switches


By splitting the LDO into two half size LDOs we can reduce the number of powers switches

Basis for linear VRM systems!

**Surge protectors based on supercapacitors:
SC Assisted Surge Absorber (SCASA)
Technique**

Despite their low DC voltage rating, supercapacitors are large time constant circuits

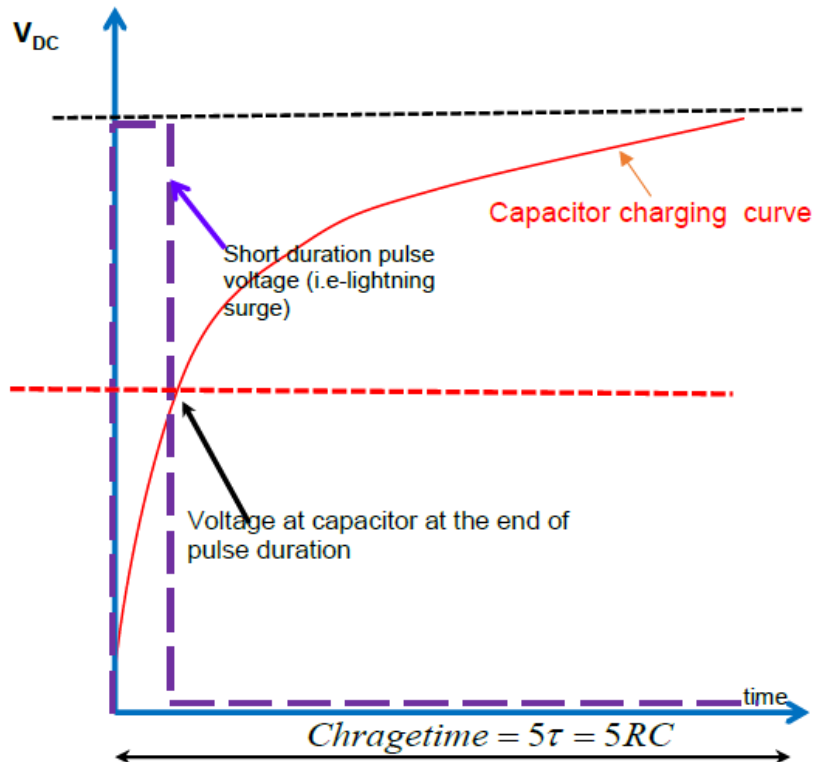Large time constant circuit excited by a short duration step-voltage



- A typical SC circuit has a time constant from milliseconds to seconds
- 1 F SC with an ESR of 100 m Ω will have a time constant of 100 ms
- Such a circuit will take about 0.5 seconds to charge the capacitor to DC source voltage
- However, if the source voltage lasts only 10-100 μ s (as in a case of a lightning induced case) capacitor will not charge to a significant voltage

Can SCs absorb high voltage transients like lightning surges/inductive energy dumps induced on power rails?

Due to their long time constant circuits SCs can absorb kilovolts order surges!

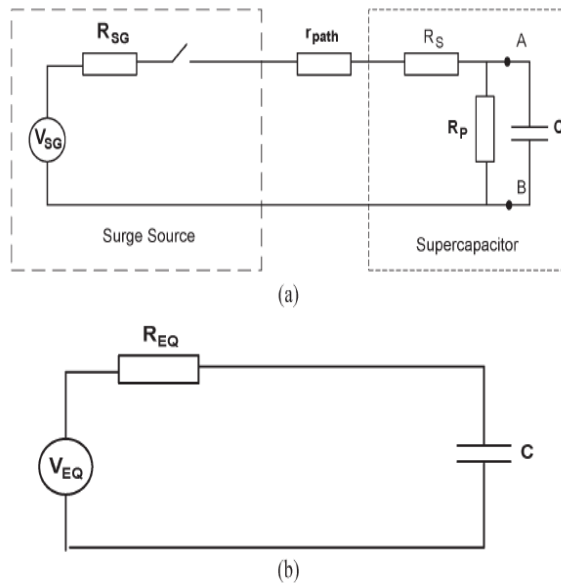


Fig. 5. Surge source connected to an SC. (a) Case with a simplified equivalent circuit of an SC. (b) Simplified Thevenin equivalent circuit.


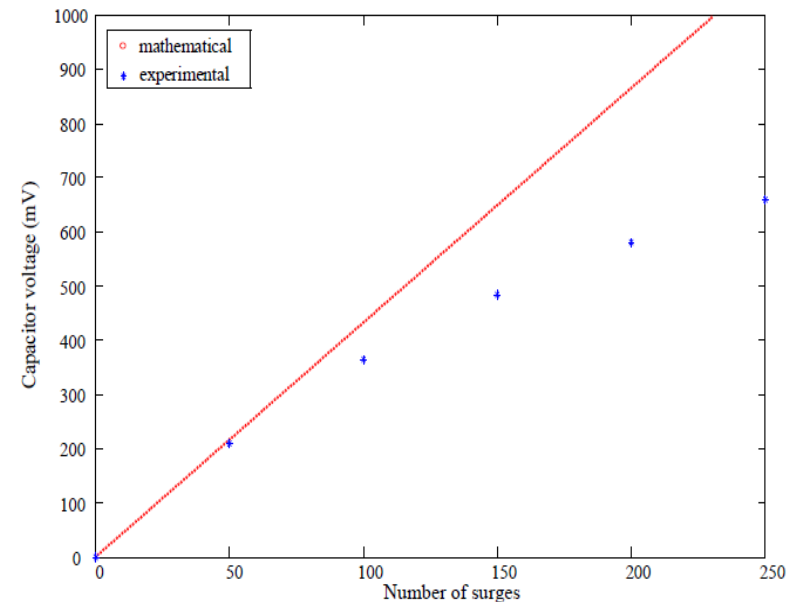


Figure 4.6: Applying consecutive surges to a 1 F supercapacitor; experimental vs simulated data


- This indicates that due to very long time constants, SC can't be destroyed by short duration transient surge voltages
- We tested three different commercial families of SCs and reconfirmed this practically

Surge Capability Testing of Supercapacitor Families Using a Lightning Surge Simulator

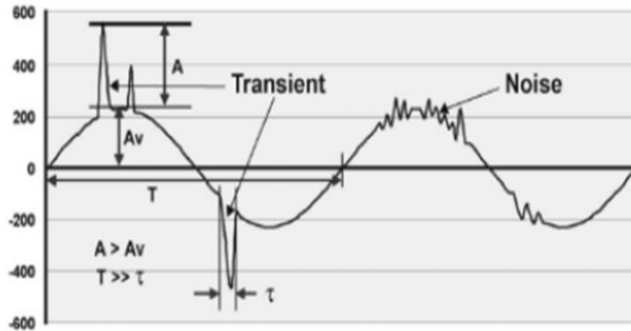
Typical surge protector circuits and power line transients



Power line suraes

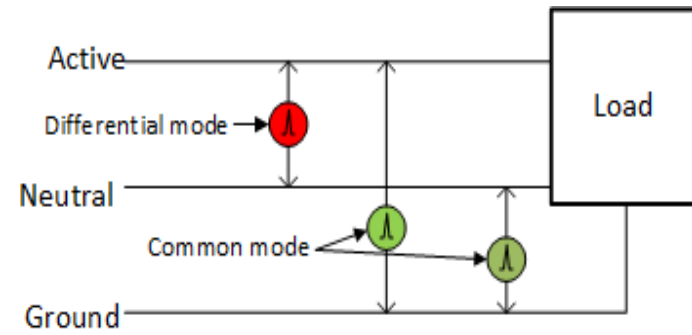


Differential and common mode surges

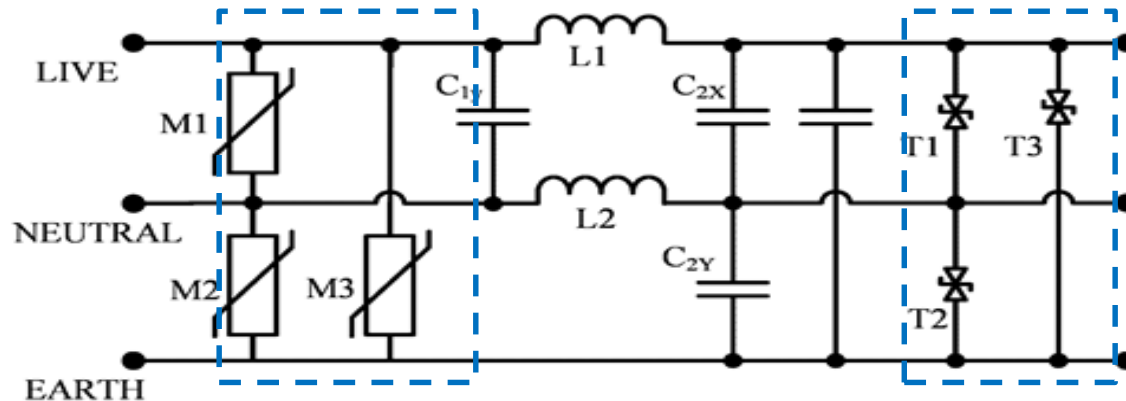

Typical surge protection circuit

Typical surge protectors use MOVs and BBDs to absorb surge energy. However, they are transient rated devices, and if repeated surges occur they tend to get destroyed.

SCASA Technique

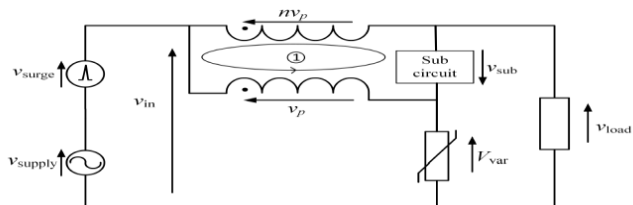

SCASA Technique with a SC sub-circuit for better surge absorption

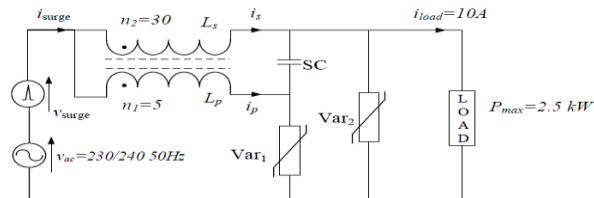


Figure 5.16: The SCASA technique with an additional second varistor for further protection

Practical implementation in a commercial design




Commercial product based on SCASA technique

SCASA advantage over well-known surge absorber techniques

Table 5.4: Component count comparison for differential-mode section in commercial surge protectors vs SCASA

Component type	High end	Low end	SCASA
MOVs	4	1	2
Inductors	2	0	1
X-type capacitors	5	1	0
Supercapacitors	0	0	1

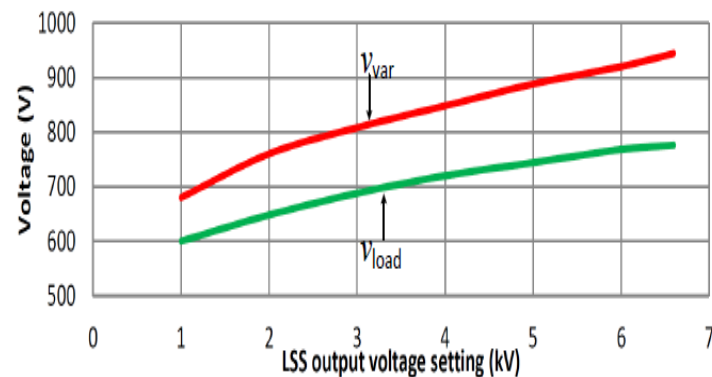

In SCASA, number of components are less and the transient related voltage at the protected load is less than the clamping voltage at the MOV

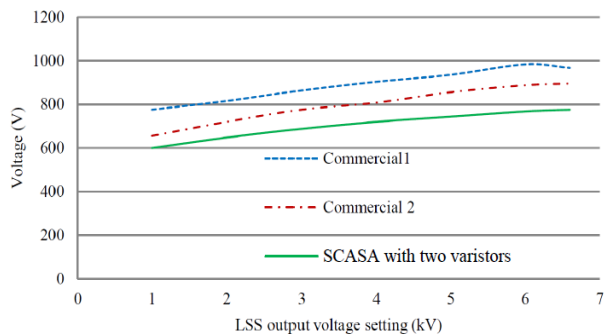


Figure 5.19: Performance comparison of SCASA with two commercial surge protectors

**Supercapacitor Assisted Temperature
Modification Apparatus (SCATMA) : A SC
based solution to hot water delay issue**


Well-known problem at water faucets

- In our home environments central water heater is at a distant location from individual faucets
- This makes cold water storage between the central heater and the faucet
- Result is delayed hot water at the faucet
- Delay can be anything from about 10 seconds to a minute depending on the length of the buried pipes
- This creates a huge waste of water, every day

Why it is not easy to solve the problem

- Maximum power we can draw from a wall socket is about 2.3 kW
- Water is not stationery and hence heating power deliverable into water should be at a value much larger than 2.5 kW maximum
- Building heaters and tanks to do this is complex and costly
- Safety/ regulatory issues




Instant water heating : SCATMA

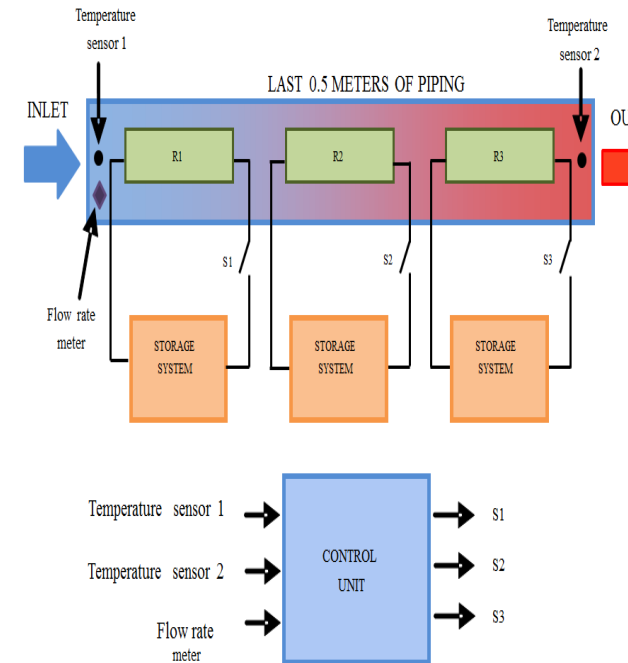

Flow Rate ($L \min^{-1}$)	4			6		
Temperature Rise ($^{\circ}C$)	20	30	50	20	30	50
Total Energy (W h)	46	70	116	70	105	175
Average Power (kW)	5.6	8.4	14	8.4	12.6	21
Average Current at 50 V (A)	112	168	280	168	252	420

Design Approach and Implementation

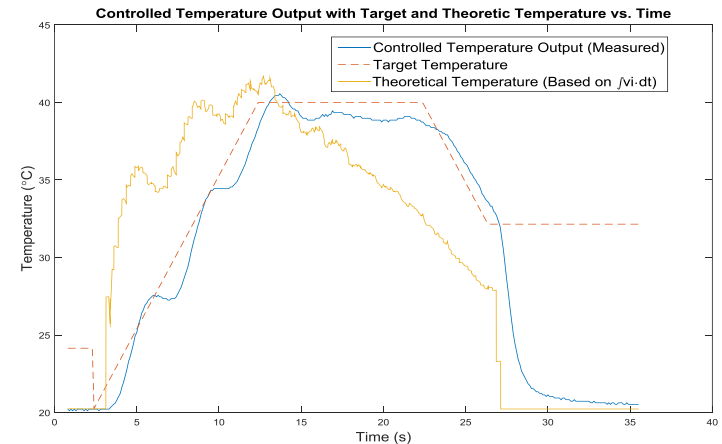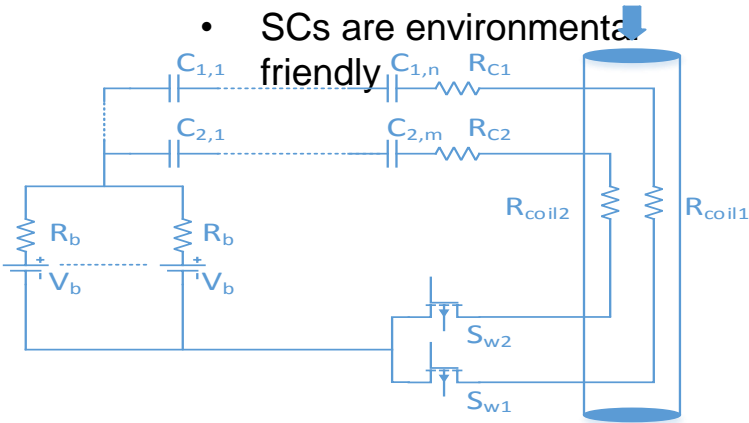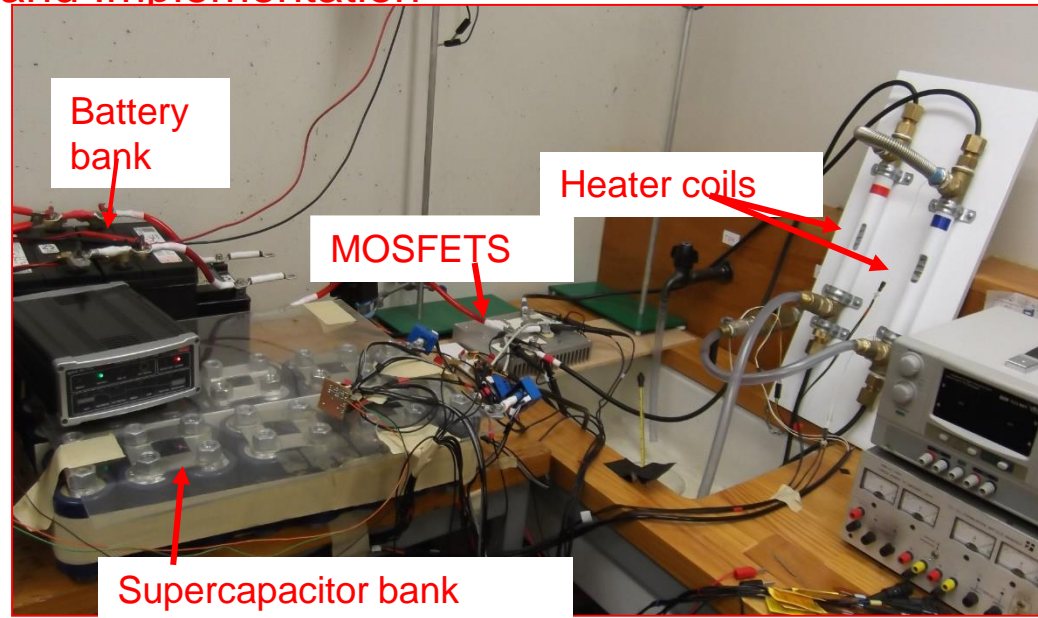- Energy Storage System
 - Supercapacitors (SC) vs. Batteries
 - Neither media has both high energy density and power density
 - Superior cycling capability of SC- but with low power density
 - Constant lower ESR of SCs allow high currents at lower depth of discharge



In first prototypes, to lower the cost, a battery-SC hybrid solution had to be used. However with new hybrid SCs SC only solution is feasible.

More SC assisted circuit topologies under development

Early developments and achievements


- Development of the SCALDO technique indicates the power of very large capacitors
- SCALDO is based on circumventing the capacitor charging losses and a large time constant circuit combined
- SCASA was making use of large time constant property of SCs and SCATMA was based on the very low ESR of large SCs

The above work opened up the potential of additional SC assisted topologies


- SC assisted high density inverter- SCAHDI (Inspired by Google's the Little Box Challenge)
- For DC Microgrid area with 12 V LED lighting SC assisted LED systems (SCALED)

In both cases, capacitor charging loss in a resistive charging loop is circumvented by inserting a useful load such as a LED lamp load or a inverter

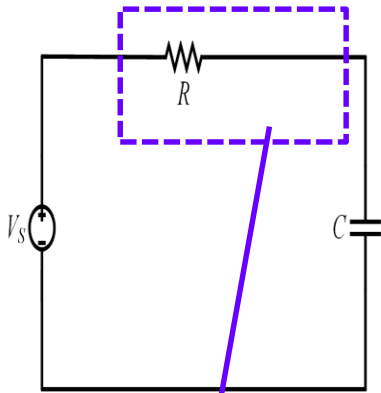Inserting a useful resistive load in the charging path to circumvent the loss



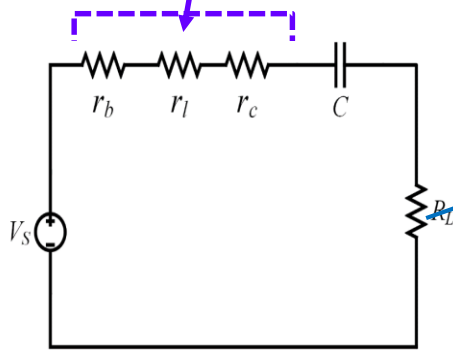Simple RC circuit where resistive losses could waste energy up to a 50%



Inserting useful resistive load in the charging loop

This concept was used in the SCALDO technique, where R_L was the loaded LDO

- The useful resistive load (R_L) can be;
 - Lighting load
 - Inverter
 - Any resistive load
- Losses in each resistive element ;

$$E_{r_b} = \left(\frac{r_b}{r_b+r_l+r_c+R_L} \right) \cdot E_{Loss}$$

$$E_{r_l} = \left(\frac{r_l}{r_b+r_l+r_c+R_L} \right) \cdot E_{Loss}$$


$$E_{r_c} = \left(\frac{r_c}{r_b+r_l+r_c+R_L} \right) \cdot E_{Loss}$$

$$E_{R_L} = \left(\frac{R_L}{r_b+r_l+r_c+R_L} \right) \cdot E_{Loss}$$
- The R_L utilizes the wasted energy;

$$E_{Loss} = \frac{r_b+r_l+r_c}{(r_b+r_c+r_l)+R_L} \times 50\%$$

SC assisted high density inverter(SCHADI) technique

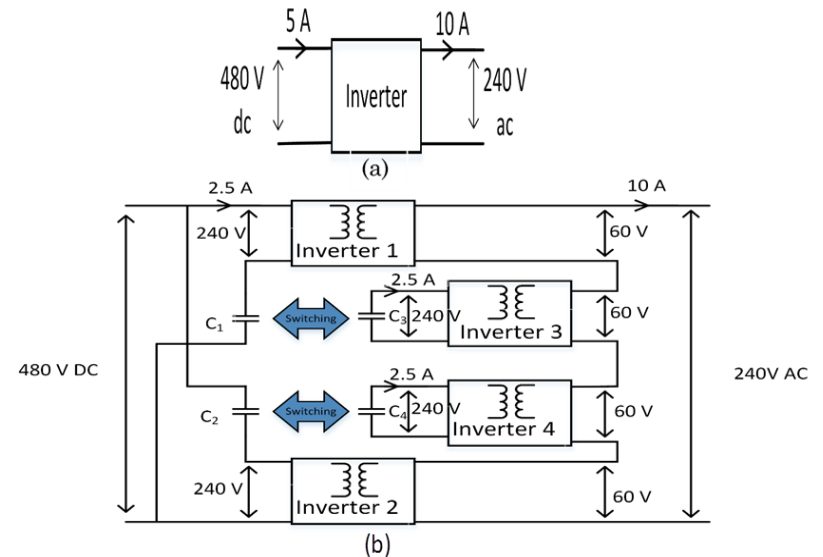- A loaded inverter is used in the charging path of a SC bank in an inverter system
- The overall inverter is divided into several micro-inverters
- Outputs are series connected to get the required AC voltage
- SC banks keep powering half the micro-inverters
- Other half are directly powered through the charging loop



In SCAHDI also we use a SC and a useful resistor to circumvent losses

Conclusion

- When a capacitor becomes almost a million times larger it can be creatively used for very new circuit topologies and techniques
- These new techniques can help in
 - Reducing lost energy in power converters
 - Developing new surge protectors with low component count and better performance
 - Low voltage rapid energy transfer into flowing liquids
 - High density inverters
 - DC Microgrid applications for energy efficiency

What was presented is only the tip of the ice burg... Creative circuit designers can make us of commercial EDLCs in many more applications and much more versatile than in simple energy storage systems....

Thank you.....

Question Time...



THE UNIVERSITY OF
WAIKATO
Te Whare Hāmau o Waikato