


7. A Spice Model for Windings

Dr. Ray Ridley

www.ridleyengineering.com

**APEC Magnetics Industry Session
Tuesday March 6, 2018**


Semiconductor Devices and Models

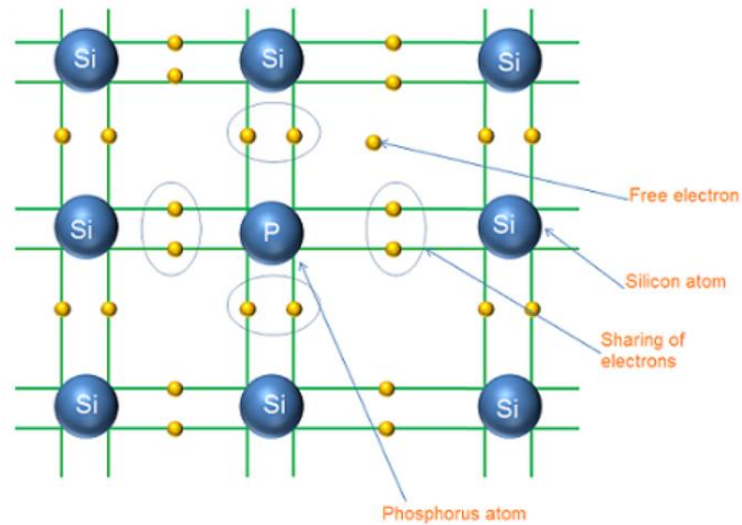

$$\frac{\lambda^2 (1-y^2)}{2} \left\{ \left[n \left(y + \frac{v-\mu}{2n+\mu+v} \right) \left(\frac{\mu-2\beta}{1-y} - \frac{v-2\alpha}{1+y} \right) + n(n+\mu+v+1) + (2\alpha\beta + \alpha + \beta) \right. \right. \\ \left. \left. - \alpha^2 \frac{1-y}{1+y} - \beta^2 \frac{1+y}{1-y} + \frac{2}{\lambda^2 (1-y^2)} \right] \times \left[\frac{V_0}{q} (y+\gamma) (1-y^2) - E \right] \varphi_n \right. \\ \left. - 2 \frac{(n+\mu)(n+v)}{2n+\mu+v} \left(\frac{\mu-2\beta}{1-x} - \frac{v-2\alpha}{1+x} \right) \frac{A_n - \varphi_{n-1}}{A_{n-1}} \right\} = 0.$$

These are impossibly complex structures to build and understand.

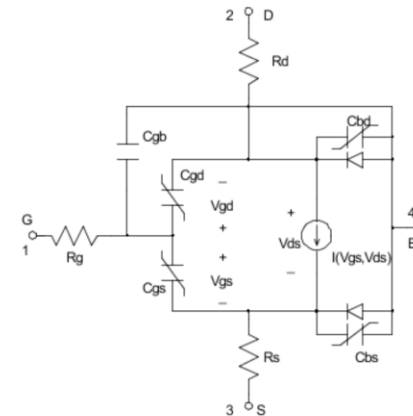Yet they come with a spice model that's pretty useful and accurate



Magnetics Devices and Models



Not so hard to build, although maybe hard to understand.

Doesn't compare to Schroedinger's equations.....


Where is the Spice model ?

The Biggest Problem with Magnetics Design

The magnetics get too **HOT!**

99.9% of designs don't apply proximity loss properly

Example: Forward converter transformer

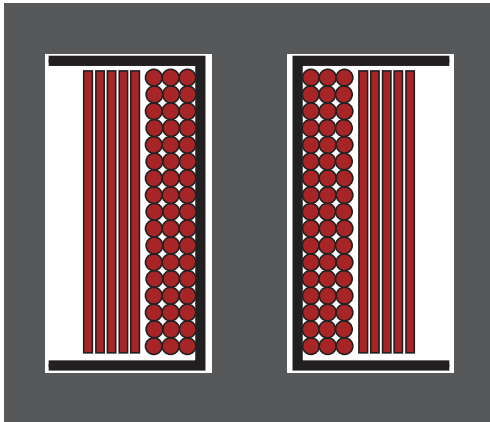


Winding loss if you don't do proximity analysis:

1.04 W

Winding loss with **full harmonic** proximity analysis

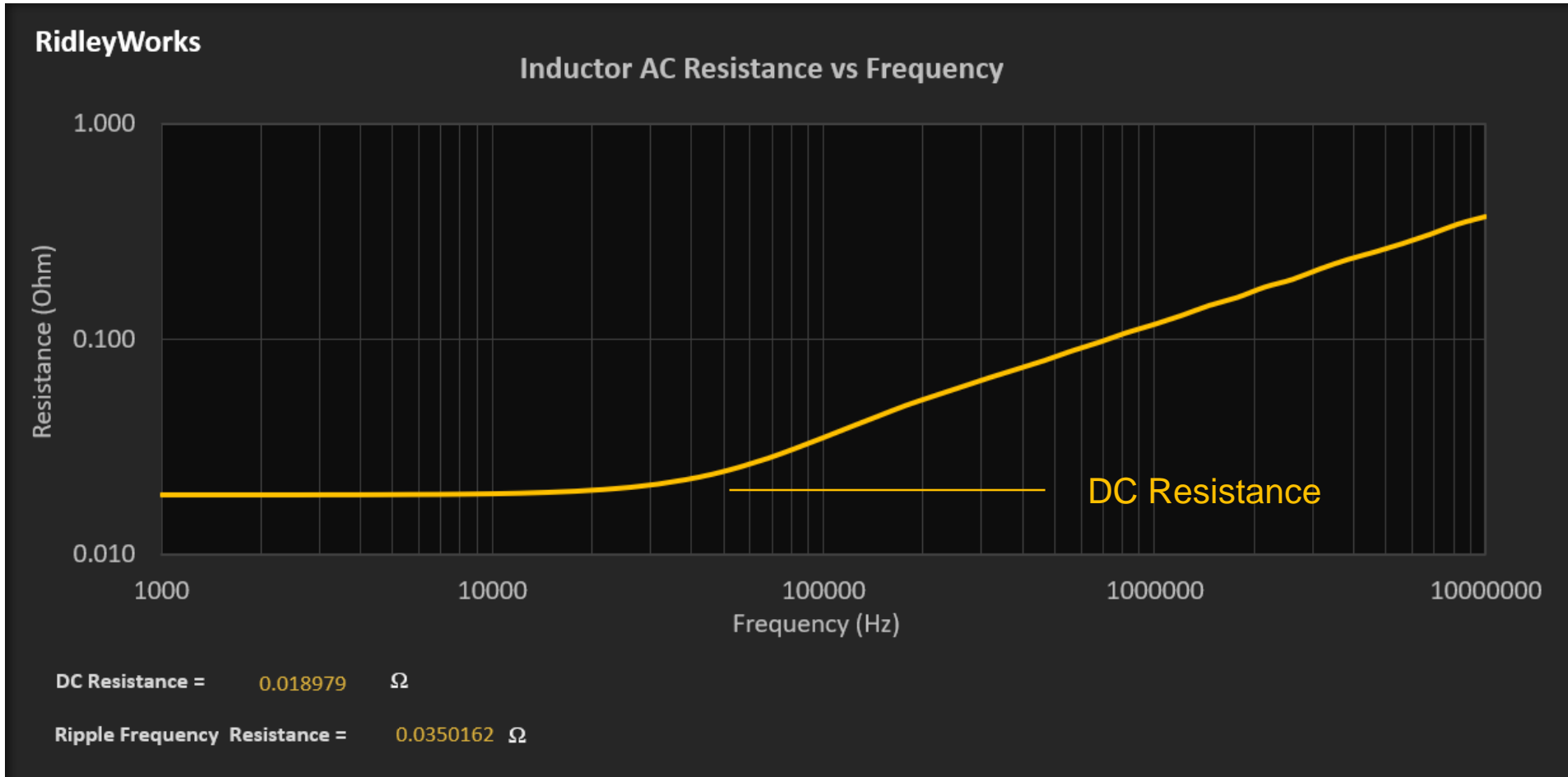10.77 W


Every Magnetic Has a Unique Frequency-Dependent Resistance



Single Layer AC Resistance with Different Thickness

RidleyWorks


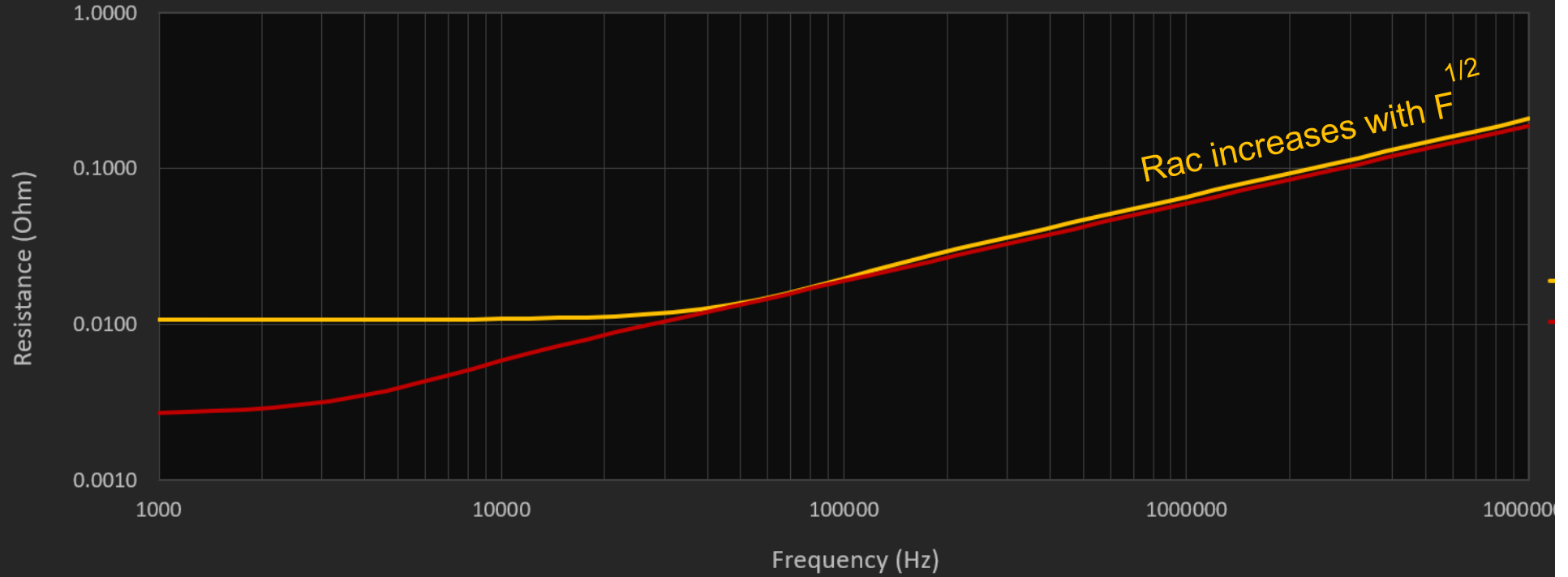
Transformer Single Layer Winding with Different Thickness




DC Resistance = 0.0106987 Ω

Ripple Frequency Resistance = 0.019739 Ω

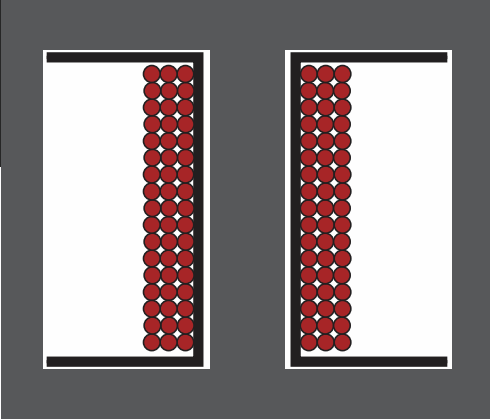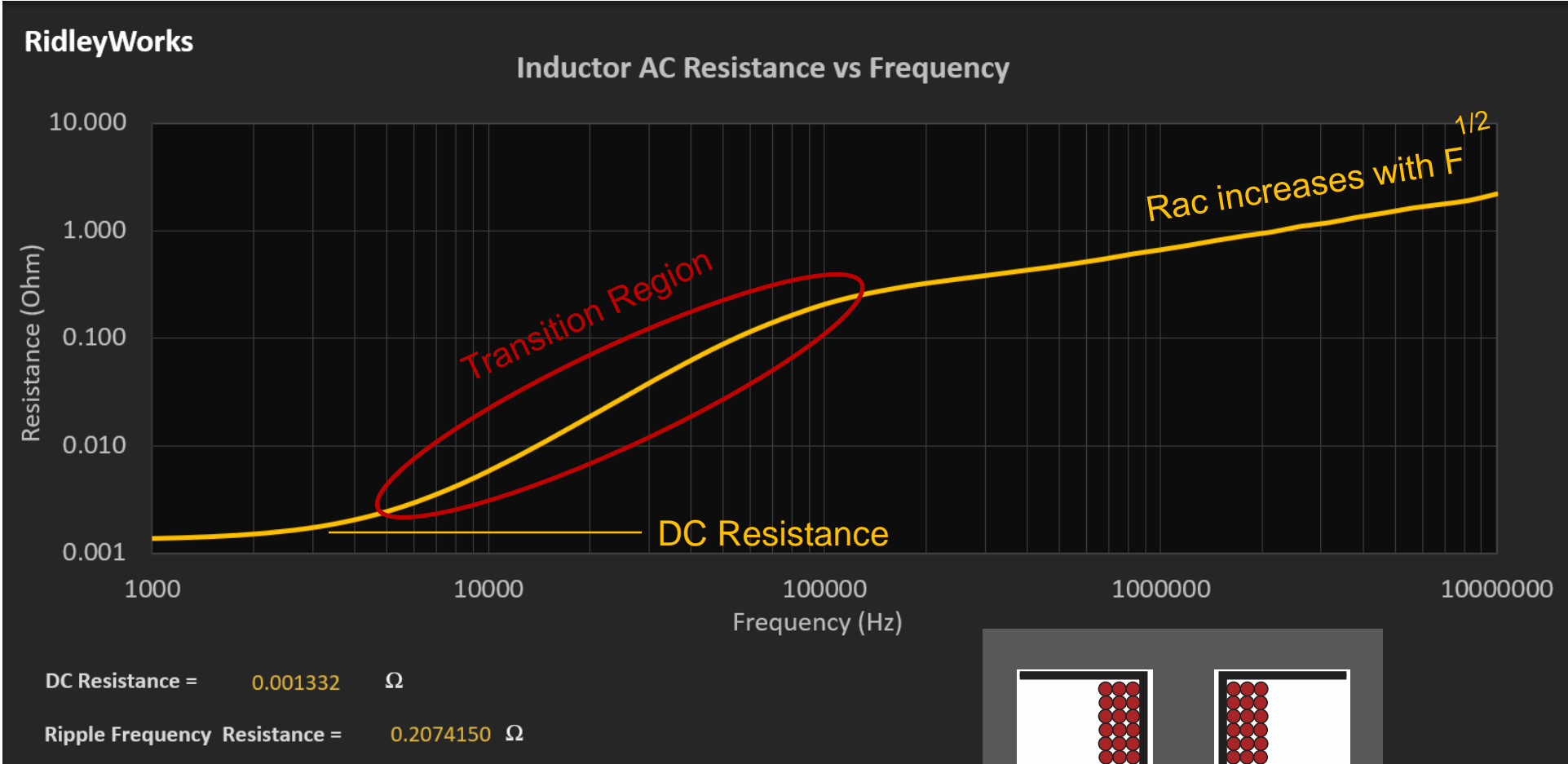Multilayer Winding AC Resistance Characteristic Curve



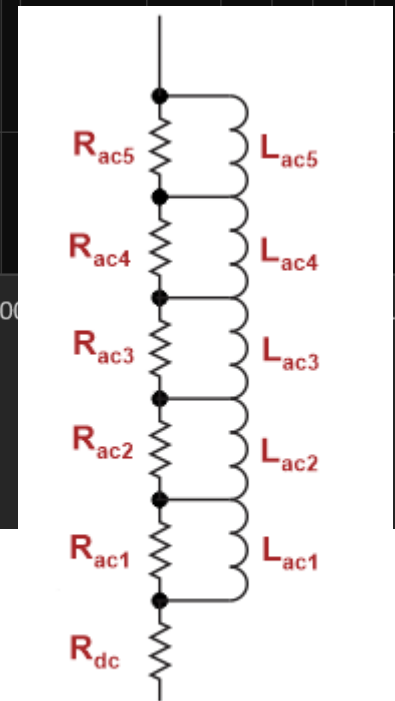
Next Step – Generate a Spice Model to Match the Resistance




Set each R_{ac} to be incremental resistance between sample frequencies multiplied by 1.4142

New Rac Model

Primary Proximity Loss Example

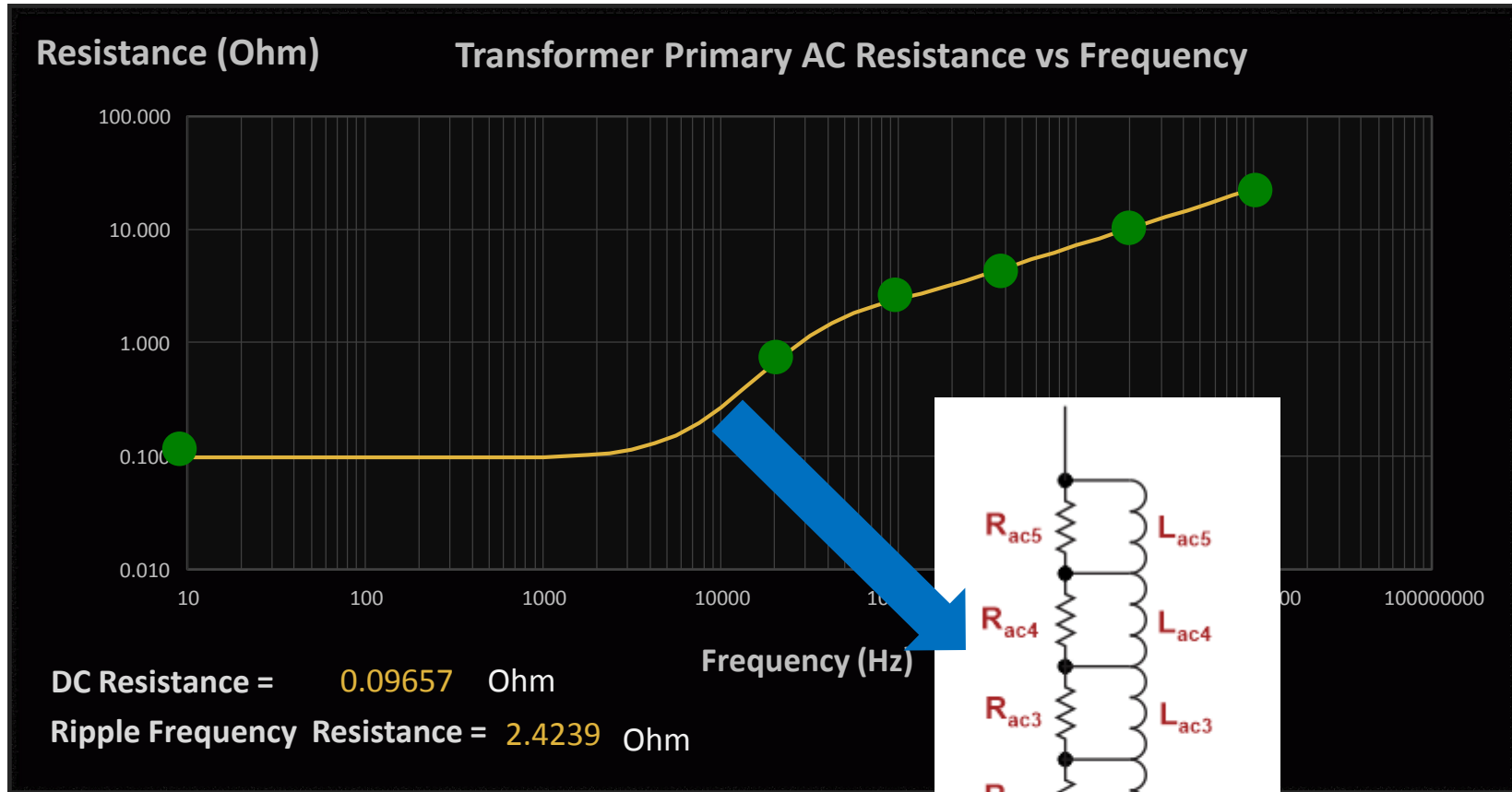


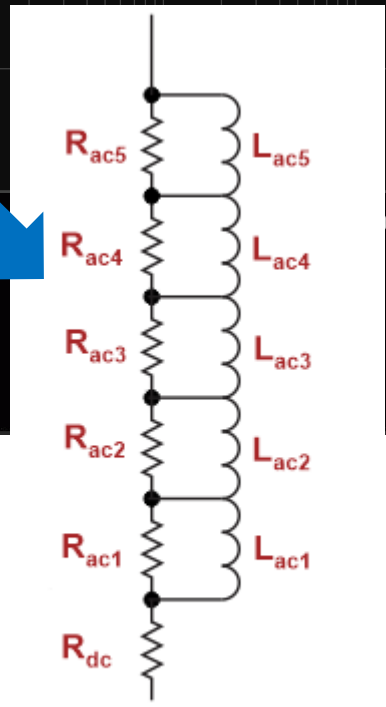
DC Resistance = 0.09657 Ohm
Ripple Frequency Resistance = 2.4239 Ohm




New Rac Model

Clear

Primary Proximity Loss

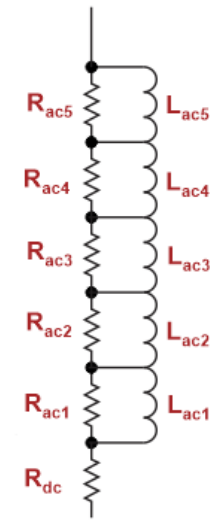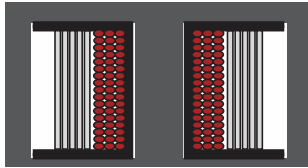


New Rac Model

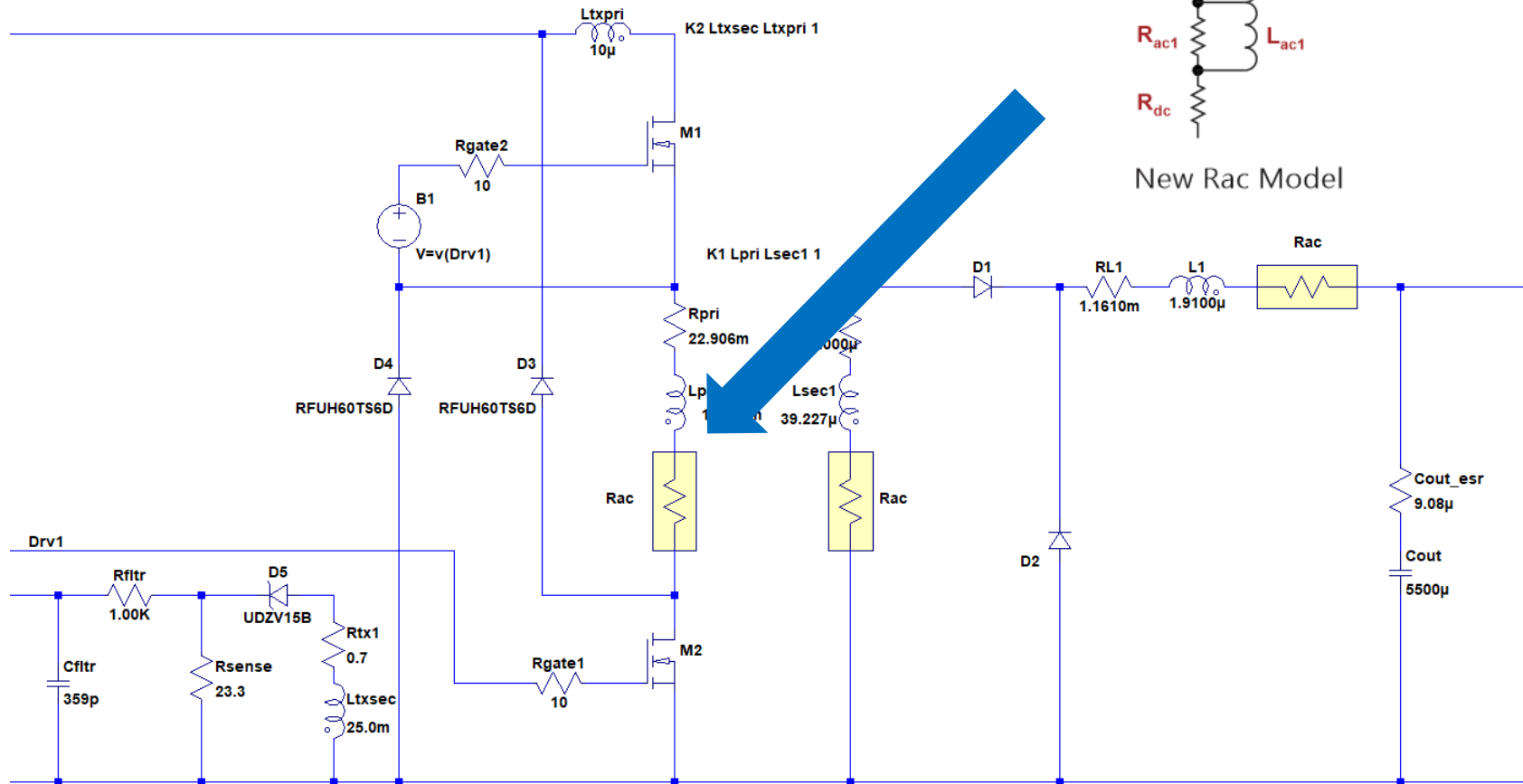

Clea

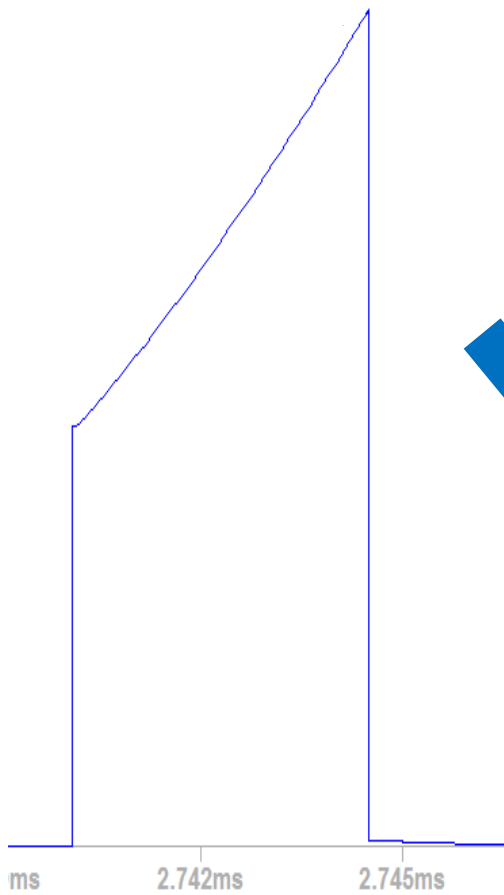Primary Loss RMS Current and DC Resistance




Waveform: V(N009,N019)*I(Rpri) [Close]

Interval Start:


Interval End:

Average:

Integral:

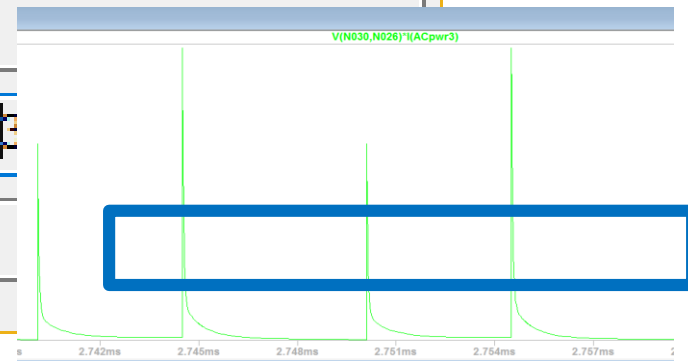

Primary Proximity Loss

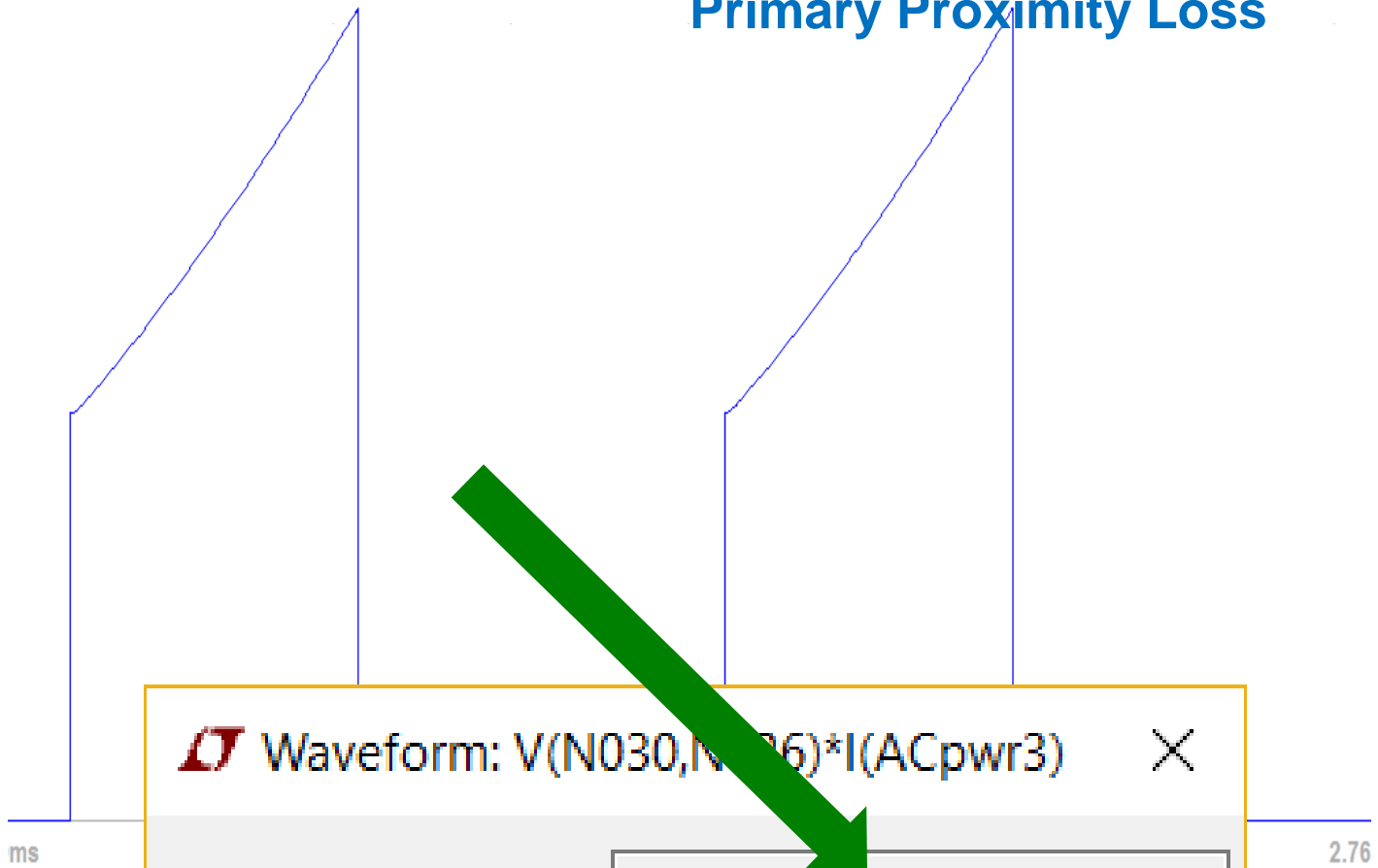

Waveform: V(N030,N026)*I(ACpwr3) X

Interval Start:	2.736ms
Interval End:	2.766ms
Average:	7.4832W
Integral:	224.5μJ

Waveform: V(N030,N026)*I(ACpwr3) X


Interval Start:	2.736ms
Interval End:	2.766ms
Average:	7.4832W
Integral:	224.5μJ

Magnetics Winding Spice Model Summary



A simple spice circuit will predict ac losses in a winding with arbitrary circuit waveforms

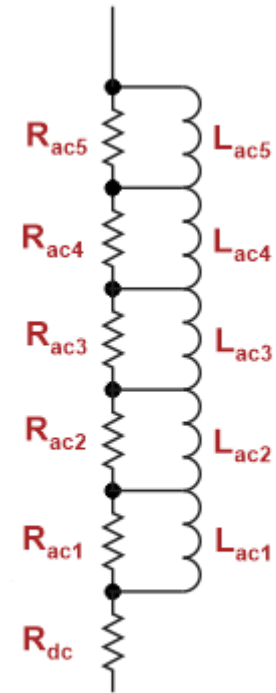Model generation is fully automatic. What used to take hours of work is now done in minutes, freeing the designer for more creative work.



New Rac Model

Magnetics Core Loss Project

We are working on similar models for the core loss

Crowd-programming project – help us with data

Download free version of RidleyWorks Buck Designer, look for the core loss
Open Programming page in next version.

Ridleyengineering.com software intro page